

Impedance Review

ME 473

Professor Sawyer B. Fuller

Technically, “mechanical impedance” is $1/Z(s)$. Therefore, in the mechanical domain, we must refer to our definition of $Z(s)$ as “generalized impedance,” or “mobility.” This convention for $Z(s)$ has the benefit that it preserves circuit topology.

Generalized impedances are an extension of the concept of electrical impedances to systems of other domains. The table below lists the corresponding driving-point impedance definitions for five different energy modalities.




		Mechanical Translational	Mechanical Rotational	Electrical	Fluid	Thermal
Across Variable		v , velocity	ω , angular velocity	v , voltage	p , pressure	T , temperature
Through Variable		f , force	T , torque	i , current	q , volumetric flow	q , heat flow rate
Impedance $Z(s)$ Admittance $Y(s) = \frac{1}{Z(s)}$		$Z(s) = \frac{V(s)}{F(s)}$	$Z(s) = \frac{\Omega(s)}{T(s)}$	$Z(s) = \frac{V(s)}{I(s)}$	$Z(s) = \frac{P(s)}{Q(s)}$	$Z(s) = \frac{T(s)}{Q(s)}$
Impedance $Z(s)$	A-Type	mass, M : $\frac{1}{Ms}$	inertia, J : $\frac{1}{Js}$	capacitor, C $\frac{1}{Cs}$	fluid capacitor, C $\frac{1}{Cs}$	thermal capacitor, C $\frac{1}{Cs}$
	D-Type	damper, B $\frac{1}{B}$	r. damper, B $\frac{1}{B}$	resistor, R R	fluid resistor, R R	thermal resistor, R R
	T-Type	spring, K $\frac{s}{K}$	r. spring, K_r $\frac{s}{K_r}$	inductor, L Ls	fluid inductor, L Ls	—

$$\text{Impedance} \triangleq \frac{\text{Across Power Variable}}{\text{Through Power Variable}}$$



$$\text{Admittance} \triangleq \frac{\text{Through Power Variable}}{\text{Across Power Variable}}$$

Reference: Chapter 13 of Rowell & Wormley's *System Dynamics an Introduction*
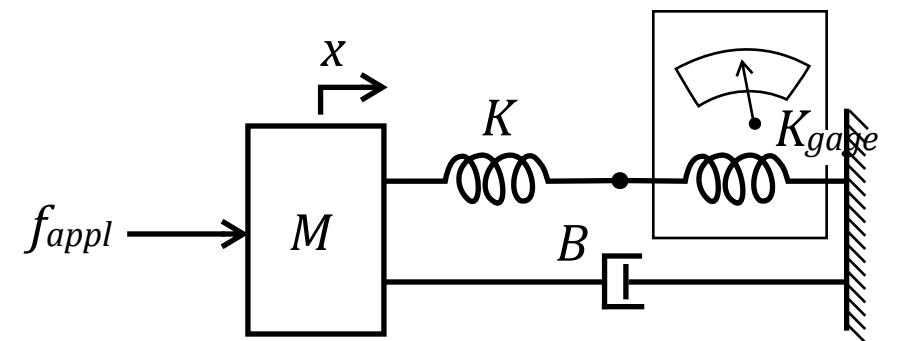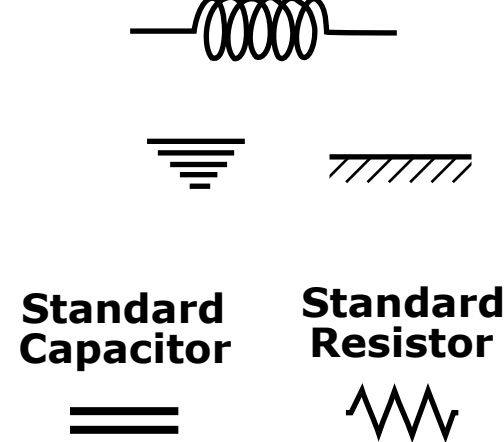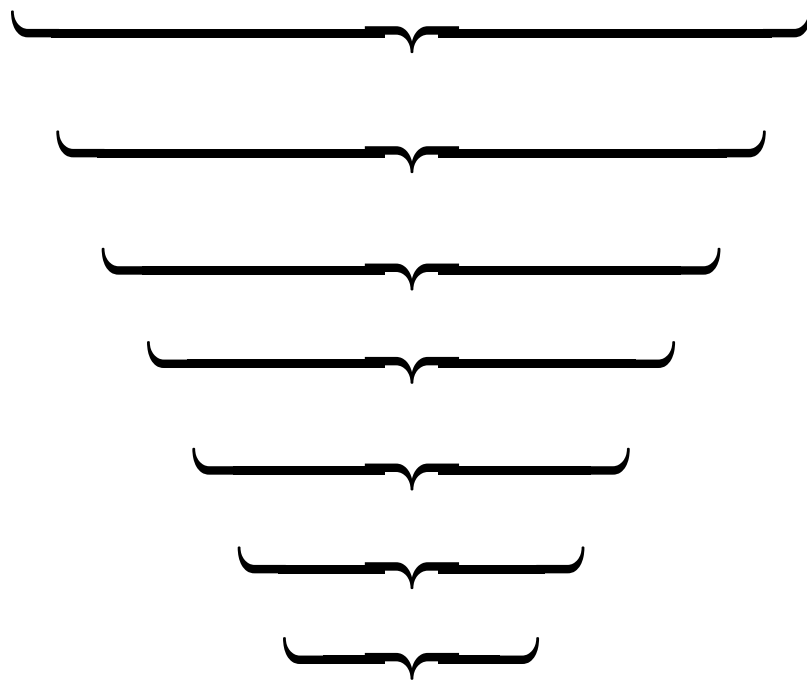
$$\text{Power} \triangleq \text{Through Var.} \times \text{Across Var.}$$



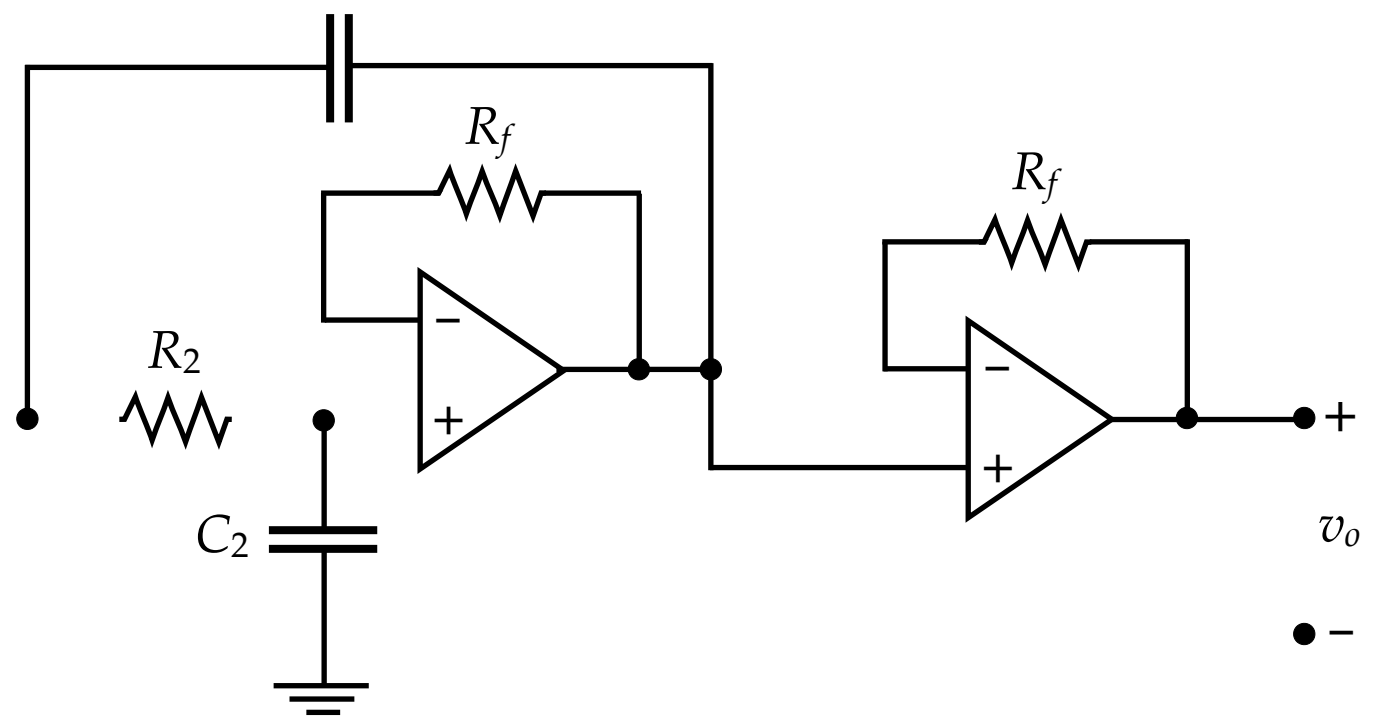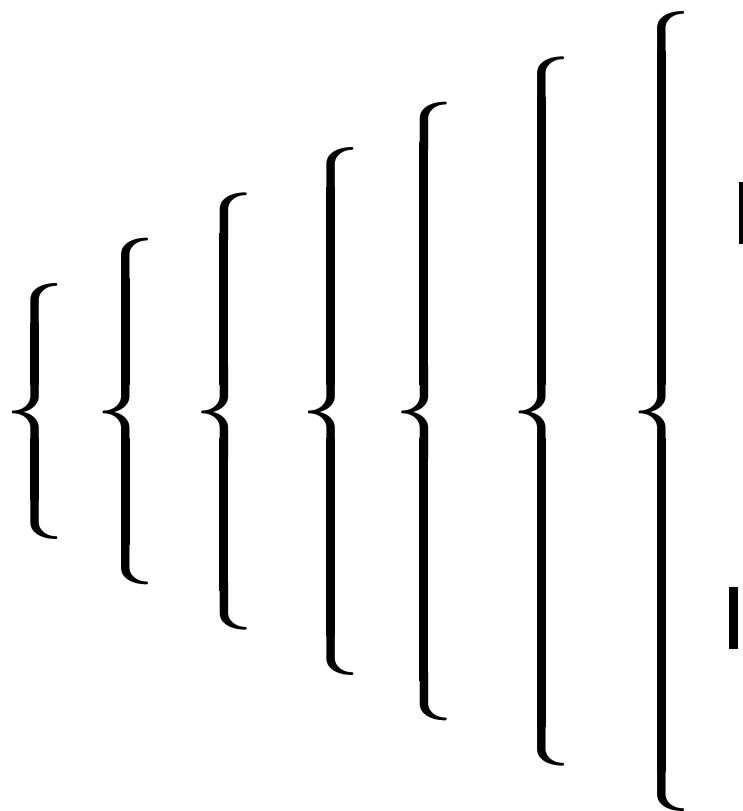*This box has Inset
Margin=6pt,
Shadow=6px, Blur=10px
and Opacity=50%*




Generalized impedances are an extension of the concept of electrical impedances to systems of other domains.
The table below lists the corresponding driving-point impedance definitions for five different energy modalities.

		Mechanical Translational	Mechanical Rotational	Electrical	Fluid	Thermal
Across Variable		v , velocity	ω , angular velocity	v , voltage	p , pressure	T , temperature
Through Variable		f , force	T , torque	i , current	q , volumetric flow	q , heat flow rate
Impedance $Z(s)$ Admittance $Y(s) = \frac{1}{Z(s)}$		$Z(s) = \frac{V(s)}{F(s)}$	$Z(s) = \frac{\Omega(s)}{T(s)}$	$Z(s) = \frac{V(s)}{I(s)}$	$Z(s) = \frac{P(s)}{Q(s)}$	$Z(s) = \frac{T(s)}{Q(s)}$
Impedance $Z(s)$	A-Type	mass, M : $\frac{1}{Ms}$	inertia, J : $\frac{1}{Js}$	capacitor, C $\frac{1}{Cs}$	fluid capacitor, C $\frac{1}{Cs}$	thermal capacitor, C $\frac{1}{Cs}$
	D-Type	damper, B $\frac{1}{B}$	r. damper, B $\frac{1}{B}$	resistor, R R	fluid resistor, R R	thermal resistor, R R
	T-Type	spring, K $\frac{s}{K}$	r. spring, K_r $\frac{s}{K_r}$	inductor, L Ls	fluid inductor, L Ls	—

Following slides apply to all
domains but use symbols
from this domain

What about the impedance/admittance of a *connection* of passive elements?

Impedances Sum in Series

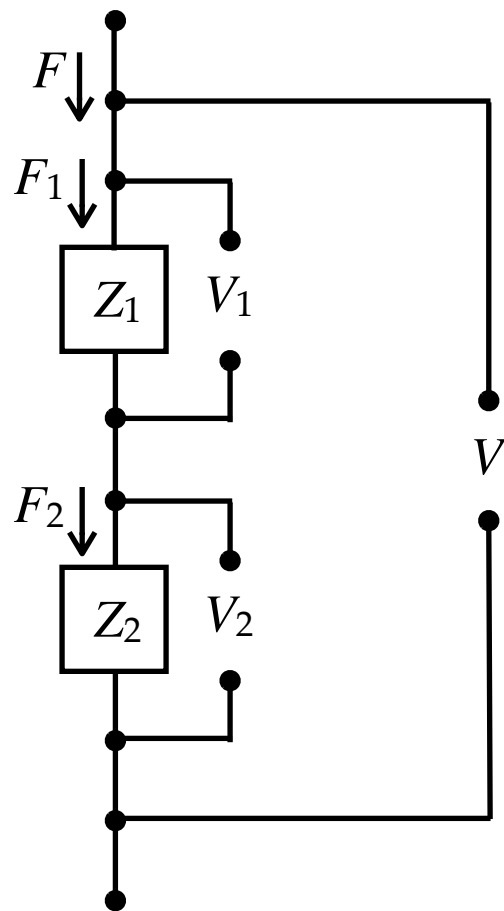


$$V = V_1 + V_2$$

$$F = F_1 = F_2$$

$$Z = \frac{V}{F} = \frac{V_1 + V_2}{F} = \frac{V_1}{F} + \frac{V_2}{F} = \frac{V_1}{F_1} + \frac{V_2}{F_2} = Z_1 + Z_2$$

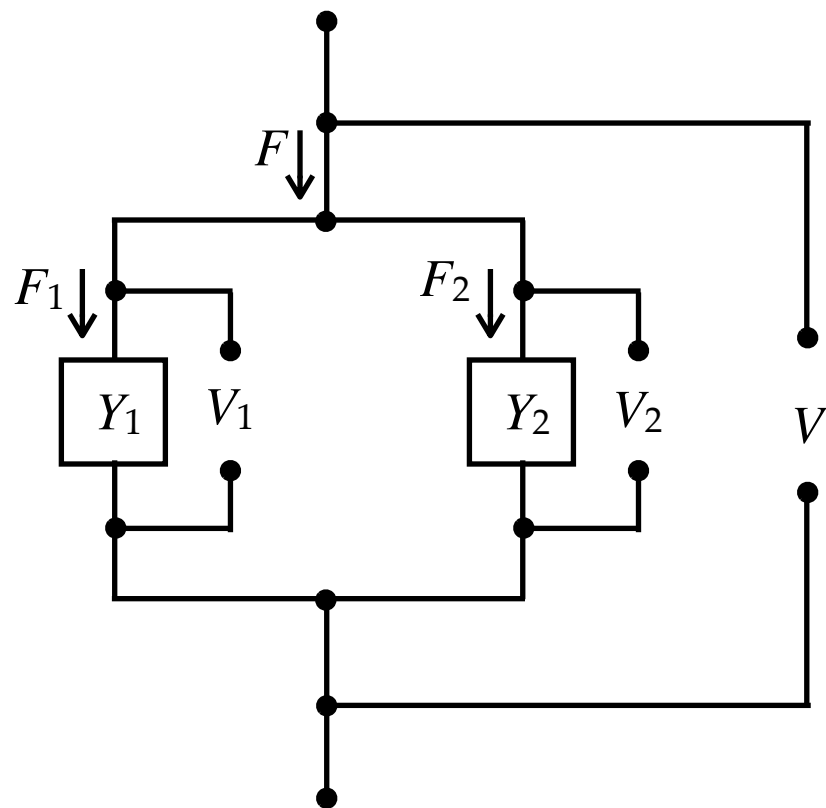admittances sum when they are in parallel





$$F = F_1 + F_2$$

$$V = V_1 = V_2$$



$$Y = \frac{F}{V} = \frac{F_1 + F_2}{V} = \frac{F_1}{V} + \frac{F_2}{V} = \frac{F_1}{V_1} + \frac{F_2}{V_2} = Y_1 + Y_2$$

Series and parallel combinations of impedances and admittances can be combined. In the following V and F represent the across and through variables respectively of any physical domain.

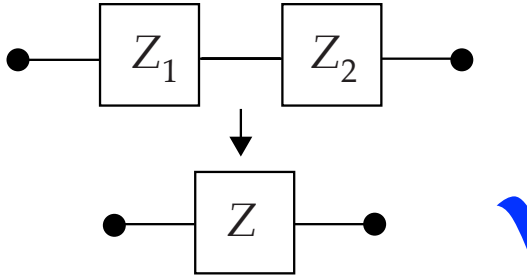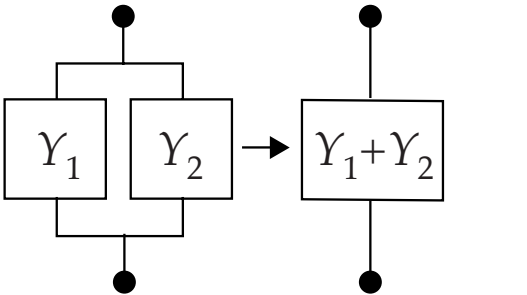Series Combination	<p>Elements sharing a common <i>through</i> variable are in <i>series</i>.</p> <p>The <i>impedance</i> of elements connected in <i>series</i> is the sum of the individual <i>impedances</i>.</p>  <p>$Z = Z_1 + Z_2$</p>	<p>Parallel Combination</p> <p>Elements sharing a common <i>across</i> variable are in <i>parallel</i>.</p> <p>The <i>admittance</i> of elements connected in <i>parallel</i> is the sum of the individual <i>admittances</i>.</p>  <p>$Y = Y_1 + Y_2$</p> <p>$Z = \frac{1}{Y} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2}} = \frac{Z_1 Z_2}{Z_1 + Z_2}$</p>
--------------------	--	--


$$Y = \frac{1}{Z} = \frac{1}{Z_1 + Z_2} = \frac{Y_1 Y_2}{Y_1 + Y_2}$$

Simple transfer functions can be determined from impedance/admittance properties.

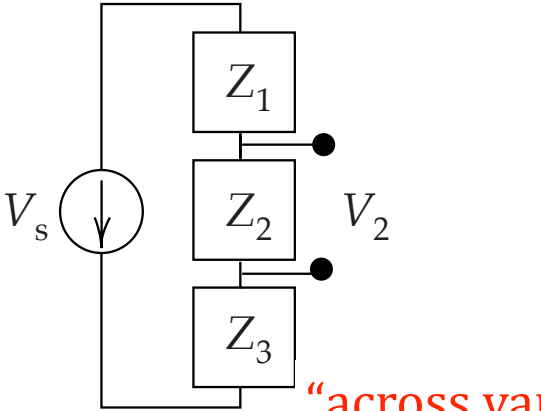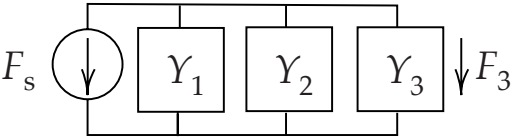Across Variable Divider	<p>The complex amplitude of the <i>across variable</i> across a set of elements in <i>series</i> is divided among the elements in proportion their <i>impedances</i>.</p>  <p>“across variable divider formula”</p> <p>$T(s) = \frac{V_2(s)}{V_s(s)} = \frac{Z_2}{Z_1 + Z_2 + Z_3}$</p>	<p>Through Variable Divider</p> <p>The complex amplitude of the <i>through variable</i> through a set of elements in <i>parallel</i> is divided among the elements in proportion their <i>admittances</i>.</p>  <p>“through variable divider formula”</p> <p>$T(s) = \frac{F_2(s)}{F_s(s)} = \frac{Y_2}{Y_1 + Y_2 + Y_3}$</p>
-------------------------	--	---

Across Variable Divider

(Across Variable = v)

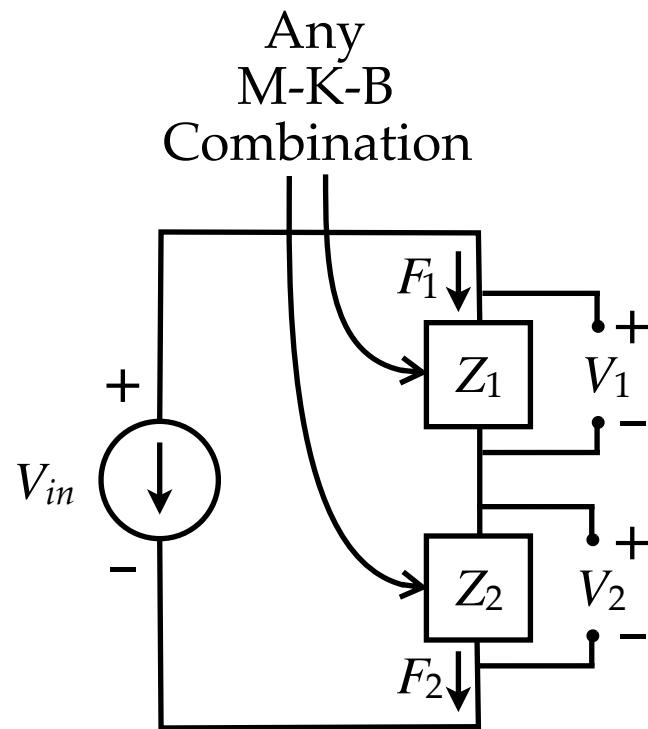

By inspection of the diagram

$$\frac{V_2(s)}{V_{in}(s)} = \frac{V_2(s)}{V_2(s) + V_1(s)} \quad (1)$$

and

$$F_1(s) = F_2(s) \quad (2)$$

Define the *impedances* $Z_1(s)$ and $Z_2(s)$ as

$$Z_1(s) = \frac{V_1(s)}{F_1(s)} \quad Z_2(s) = \frac{V_2(s)}{F_2(s)} \quad (3)$$

From (1), using (3),

$$\frac{V_2(s)}{V_{in}(s)} = \frac{Z_2(s)F_2(s)}{Z_2(s)F_2(s) + Z_1(s)F_1(s)} \quad (4)$$


From (4), using (2),

$$\frac{V_2(s)}{V_{in}(s)} = \frac{Z_2(s)}{Z_2(s) + Z_1(s)}$$

“across variable divider formula using *impedances*”

Across Variable Divider

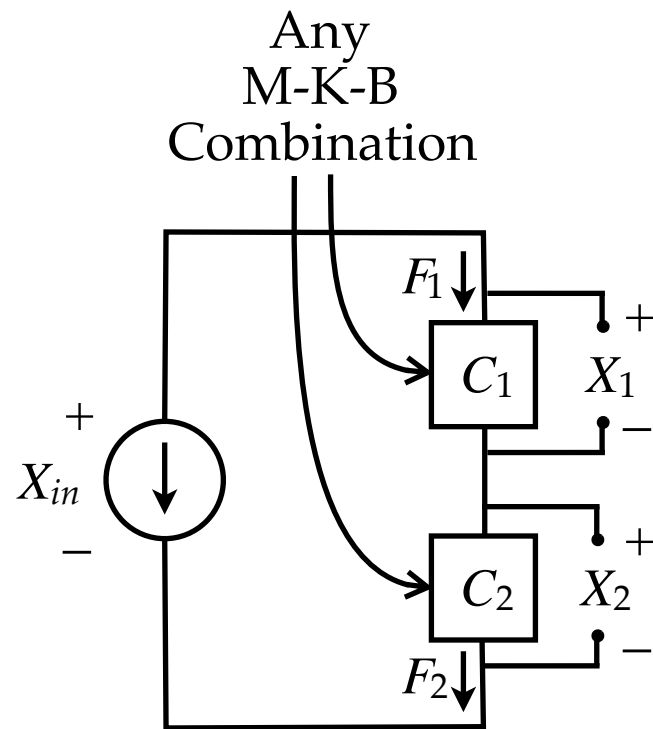(Across Variable = $x = \int v(\lambda) d\lambda$)



By inspection of the diagram

$$\frac{X_2(s)}{X_{in}(s)} = \frac{X_2(s)}{X_2(s) + X_1(s)} \quad (1)$$

and

$$F_1(s) = F_2(s) \quad (2)$$

Define the *compliances* $C_1(s)$ and $C_2(s)$ as

$$C_1(s) = \frac{X_1(s)}{F_1(s)} \quad C_2(s) = \frac{X_2(s)}{F_2(s)} \quad (3)$$

From (1), using (3),

$$\frac{X_2(s)}{X_{in}(s)} = \frac{C_2(s)F_2(s)}{C_2(s)F_2(s) + C_1(s)F_1(s)} \quad (4)$$

From (4), using (2),

$$\boxed{\frac{X_2(s)}{X_{in}(s)} = \frac{C_2(s)}{C_2(s) + C_1(s)}}$$

“across variable divider formula using *compliances*”

Through Variable Divider


(Across Variable = v)

By inspection of the diagram

$$\frac{F_2(s)}{F_{in}(s)} = \frac{F_2(s)}{F_2(s) + F_1(s)} \quad (1)$$

and

$$V_1(s) = V_2(s) \quad (2)$$

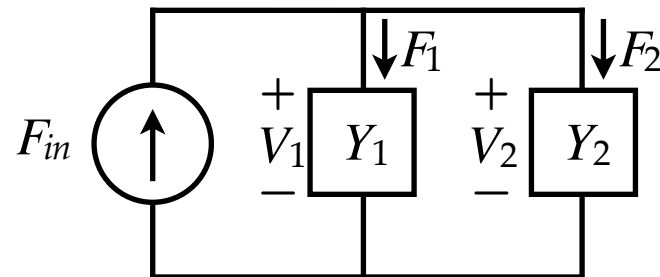

Define the *admittances* $Y_1(s)$ and $Y_2(s)$ as

$$Y_1(s) = \frac{F_1(s)}{V_1(s)} \quad Y_2(s) = \frac{F_2(s)}{V_2(s)} \quad (3)$$

From (1), using (3),

$$\frac{F_2(s)}{F_{in}(s)} = \frac{Y_2(s)V_2(s)}{Y_2(s)V_2(s) + Y_1(s)V_1(s)} \quad (4)$$


From (4), using (2),

$$\frac{F_2(s)}{F_{in}(s)} = \frac{Y_2(s)}{Y_2(s) + Y_1(s)}$$

“through variable divider formula using *admittances*”

Through Variable Divider

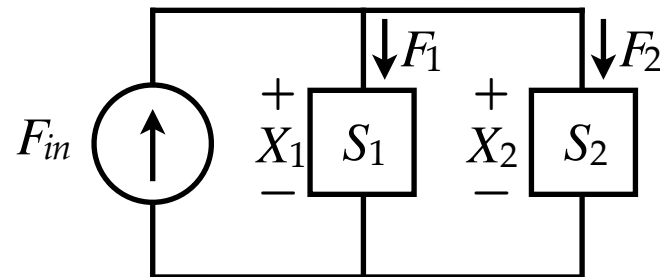(Across Variable = $x = \int v(\lambda) d\lambda$)



By inspection of the diagram

$$\frac{F_2(s)}{F_{in}(s)} = \frac{F_2(s)}{F_2(s) + F_1(s)} \quad (1)$$

and

$$X_1(s) = X_2(s) \quad (2)$$

Define the *stiffnesses* $S_1(s)$ and $S_2(s)$ as

$$S_1(s) = \frac{F_1(s)}{X_1(s)} \quad S_2(s) = \frac{F_2(s)}{X_2(s)} \quad (3)$$

From (1), using (3),



$$\frac{F_2(s)}{F_{in}(s)} = \frac{S_2(s)X_2(s)}{S_2(s)X_2(s) + S_1(s)X_1(s)} \quad (4)$$

From (4), using (2),

$$\boxed{\frac{F_2(s)}{F_{in}(s)} = \frac{S_2(s)}{S_2(s) + S_1(s)}}$$

“through variable divider formula using *stiffnesses*”

Series and parallel combinations of impedances and admittances can be combined. In the following V and F represent the across and through variables respectively of any physical domain.

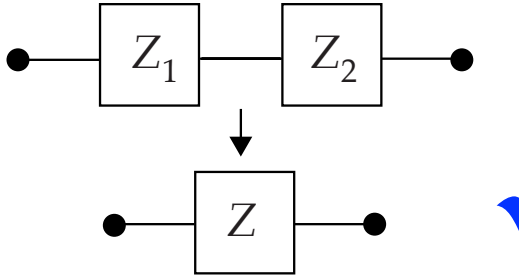
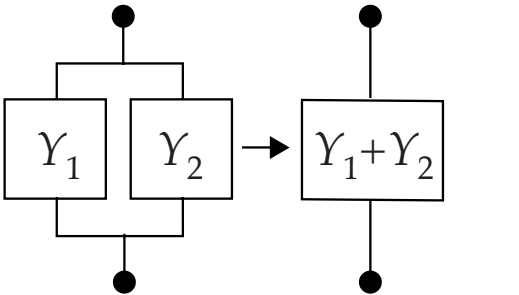
Series Combination	<p>Elements sharing a common <i>through</i> variable are in <i>series</i>.</p> <p>The <i>impedance</i> of elements connected in <i>series</i> is the sum of the individual <i>impedances</i>.</p>  $Z = Z_1 + Z_2$	<p>Parallel Combination</p> <p>Elements sharing a common <i>across</i> variable are in <i>parallel</i>.</p> <p>The <i>admittance</i> of elements connected in <i>parallel</i> is the sum of the individual <i>admittances</i>.</p>  $Y = Y_1 + Y_2$ $Z = \frac{1}{Y} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2}} = \frac{Z_1 Z_2}{Z_1 + Z_2}$
--------------------	--	--

$$Y = \frac{1}{Z} = \frac{1}{Z_1 + Z_2} = \frac{Y_1 Y_2}{Y_1 + Y_2}$$

displacements/rotations:

$Z \Rightarrow C$ (compliance)
 $\gamma \Rightarrow S$ (stiffness)

Simple transfer functions can be determined from impedance/admittance properties.

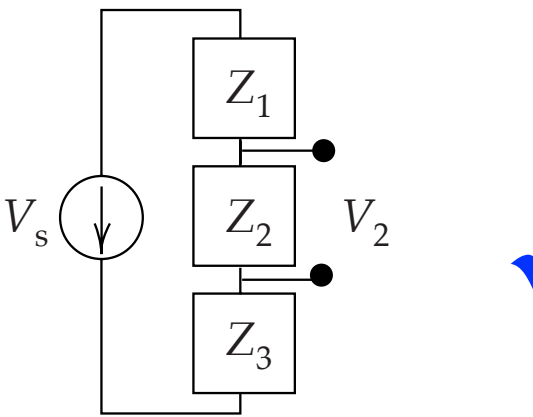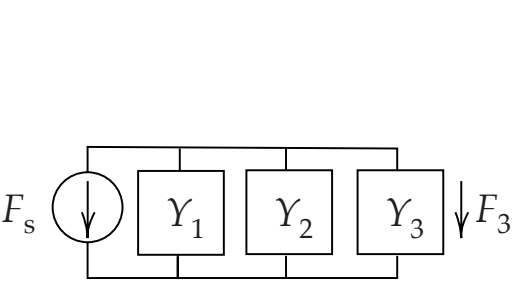Across Variable Divider	<p>The complex amplitude of the <i>across variable</i> across a set of elements in <i>series</i> is divided among the elements in proportion their <i>impedances</i>.</p>  $T(s) = \frac{V_2(s)}{V_s(s)} = \frac{Z_2}{Z_1 + Z_2 + Z_3}$	<p>Through Variable Divider</p> <p>The complex amplitude of the <i>through variable</i> through a set of elements in <i>parallel</i> is divided among the elements in proportion their <i>admittances</i>.</p>  $T(s) = \frac{F_2(s)}{F_s(s)} = \frac{Y_2}{Y_1 + Y_2 + Y_3}$
-------------------------	---	---


has mathematically identical behavior

Thevenin's Theorem

A linear two-terminal network is equivalent to an across variable source V_e in *series* with an equivalent impedance Z_e , where

Z_e = the impedance of the network with all sources set equal to zero, and

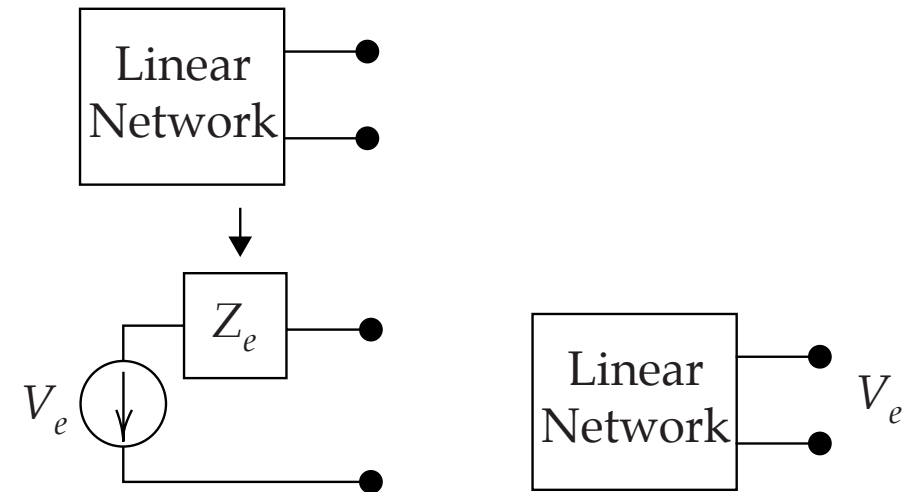V_e = an *across variable source* equal to the across variable that would appear across the *open* circuit terminals of the network.




has mathematically identical behavior

Norton's Theorem


A linear two-terminal network is equivalent to a through variable source F_e in *parallel* with an equivalent impedance Z_e , where

Z_e = the impedance of the network with all sources set equal to zero, and

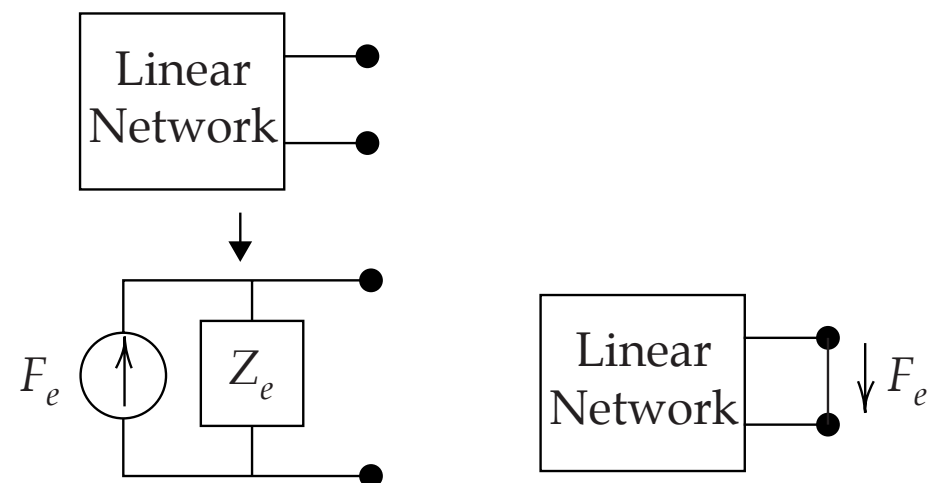F_e = a *through variable source* equal to the through variable that would flow through the *short* circuited terminals of the network.




Thevenin Equivalent Example

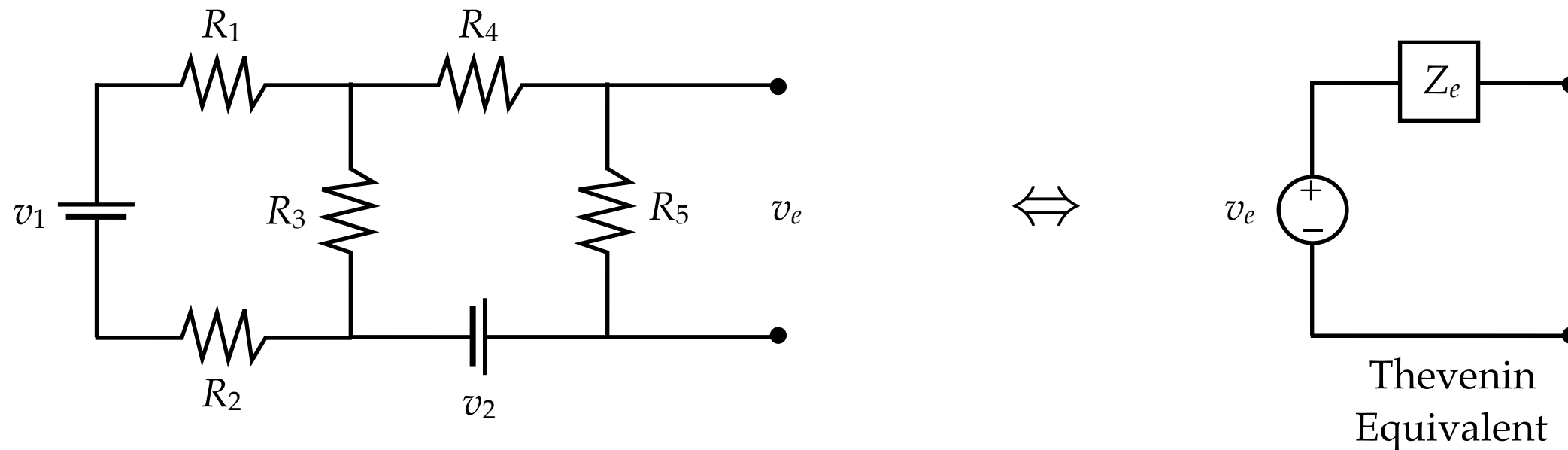

v_e = voltage that appears across the open-circuited terminals of the network

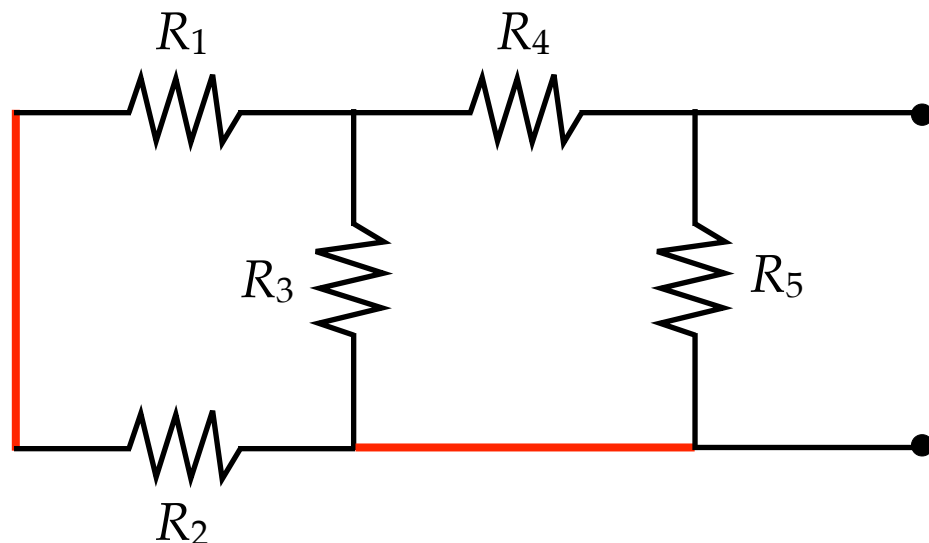
Z_e = impedance^v of the network when the voltage sources are replaced by short circuits
(seen at the output port)



\Rightarrow
Combine
Series & Parallel
Elements

$$Z_e = \frac{R_5 \left[R_4 + \frac{R_3(R_1 + R_2)}{(R_3 + R_1 + R_2)} \right]}{R_5 + \left[R_4 + \frac{R_3(R_1 + R_2)}{(R_3 + R_1 + R_2)} \right]}$$

Thevenin Equivalent Example

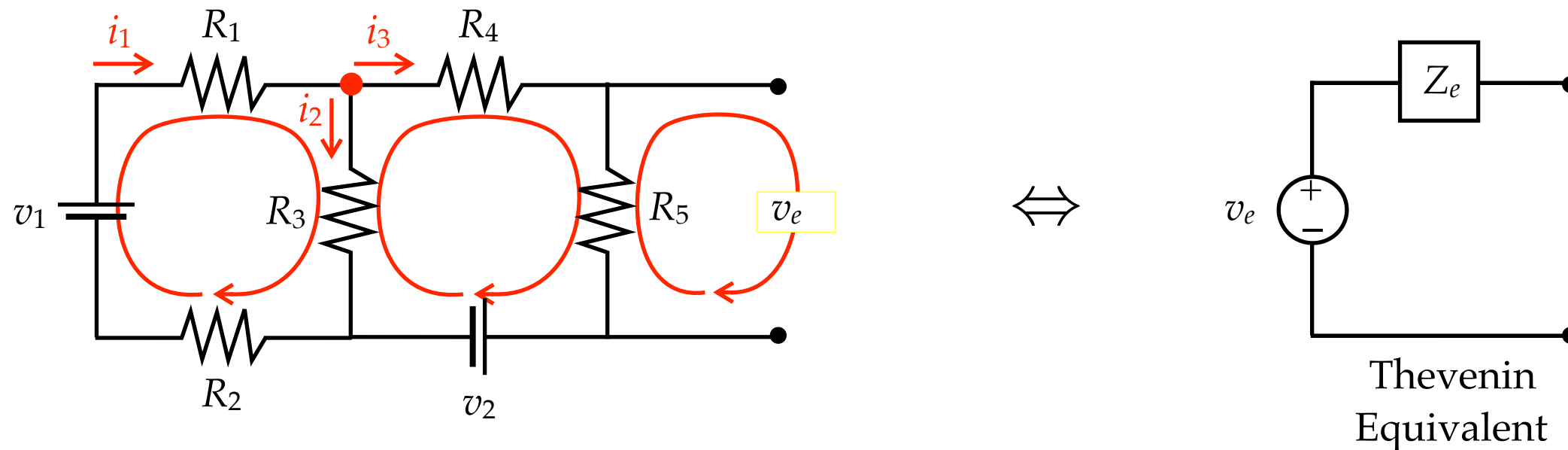

v_e = voltage that appears across the open-circuited terminals of the network

$$\left. \begin{array}{l}
 v_1 - i_1 R_1 - i_2 R_3 - i_1 R_2 = 0 \\
 i_2 R_3 - i_3 R_4 - i_3 R_5 - v_2 = 0 \\
 i_3 R_5 - v_e = 0
 \end{array} \right\} \begin{array}{l} \text{Loop Equations} \\ \\ \end{array}$$

$$i_1 = i_2 + i_3 \quad \text{Node Equation}$$

$$\left. \begin{array}{l} \text{Loop Equations} \\ \text{Node Equation} \end{array} \right\} \begin{array}{l} \text{4 independent equations in the} \\ \text{unknowns } i_1, i_2, i_3 \text{ and } v_e \end{array}$$

$$\left. \begin{aligned} v_1 - i_1 R_1 - i_2 R_3 - i_1 R_2 &= 0 \\ i_2 R_3 - i_3 R_4 - i_3 R_5 - v_2 &= 0 \\ i_3 R_5 - v_e &= 0 \end{aligned} \right\} \text{ Loop Equations}$$

$$i_1 = i_2 + i_3 \quad \text{Node Equation}$$

Mathematica solution of simultaneous equations :

In[3]:=

```
Eliminate[{v1 - i1 * R1 - i2 * R3 - i1 * R2 == 0, i2 * R3 - i3 * R4 - i3 * R5 - v2 == 0,
i3 * R5 - v_e == 0, i1 == i2 + i3}, {i1, i2, i3}]
```

Out[3]= $R_1 R_5 v_2 + R_2 R_5 v_2 + R_3 R_5 v_2 + R_1 R_3 v_e + R_2 R_3 v_e +$
 $R_1 R_4 v_e + R_2 R_4 v_e + R_3 R_4 v_e + R_1 R_5 v_e + R_2 R_5 v_e + R_3 R_5 v_e == R_3 R_5 v_1$


In[4]:= **Solve**[% , v_e]

Out[4]= $\left\{ \left\{ v_e \rightarrow \frac{R_3 R_5 v_1 - R_1 R_5 v_2 - R_2 R_5 v_2 - R_3 R_5 v_2}{R_1 R_3 + R_2 R_3 + R_1 R_4 + R_2 R_4 + R_3 R_4 + R_1 R_5 + R_2 R_5 + R_3 R_5} \right\} \right\}$

$$\Rightarrow v_e = \frac{[v_1 R_3 - v_2 (R_1 + R_2 + R_3)] R_5}{(R_1 + R_2) R_3 + (R_1 + R_2 + R_3) (R_4 + R_5)}$$

Thevenin Equivalent Example

(Summary)

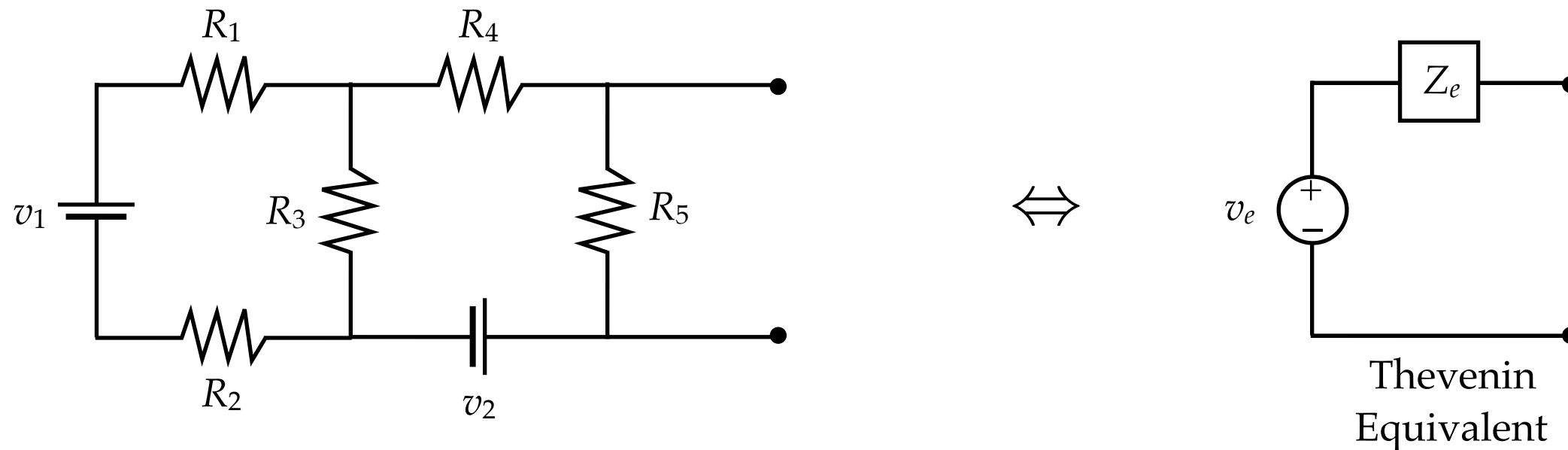

v_e = voltage that appears across the open-circuited terminals of the network

Z_e = impedance[∇] of the network when the voltage sources are replaced by short circuits
(seen at the output port)

$$v_e = \frac{[v_1 R_3 - v_2 (R_1 + R_2 + R_3)] R_5}{(R_1 + R_2) R_3 + (R_1 + R_2 + R_3)(R_4 + R_5)}$$


$$Z_e = \frac{R_5 \left[R_4 + \frac{R_3 (R_1 + R_2)}{(R_3 + R_1 + R_2)} \right]}{R_5 + \left[R_4 + \frac{R_3 (R_1 + R_2)}{(R_3 + R_1 + R_2)} \right]}$$

Thevenin's Theorem

A linear two-terminal network is equivalent to an across variable source V_e in *series* with an equivalent impedance Z_e , where

Z_e = the impedance of the network with all sources set equal to zero, and

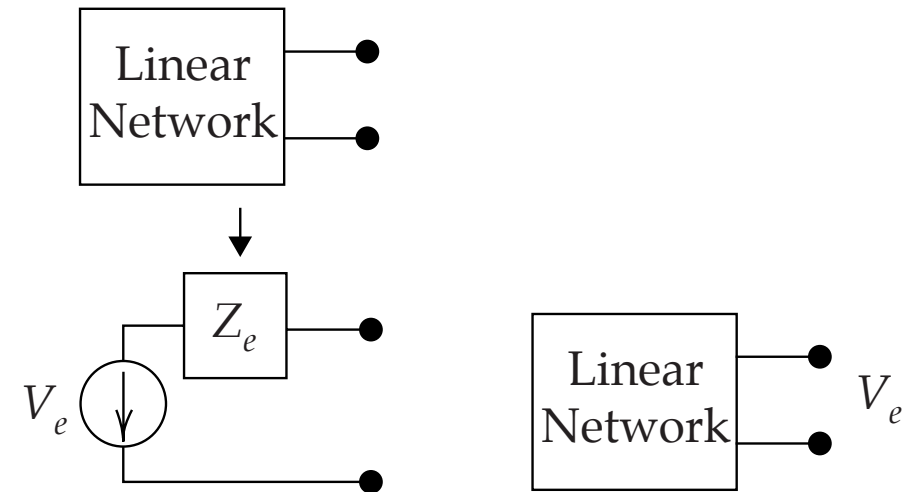V_e = an *across variable source* equal to the across variable that would appear across the *open* circuit terminals of the network.




Norton's Theorem

A linear two-terminal network is equivalent to a through variable source F_e in *parallel* with an equivalent impedance Z_e , where


Z_e = the impedance of the network with all sources set equal to zero, and

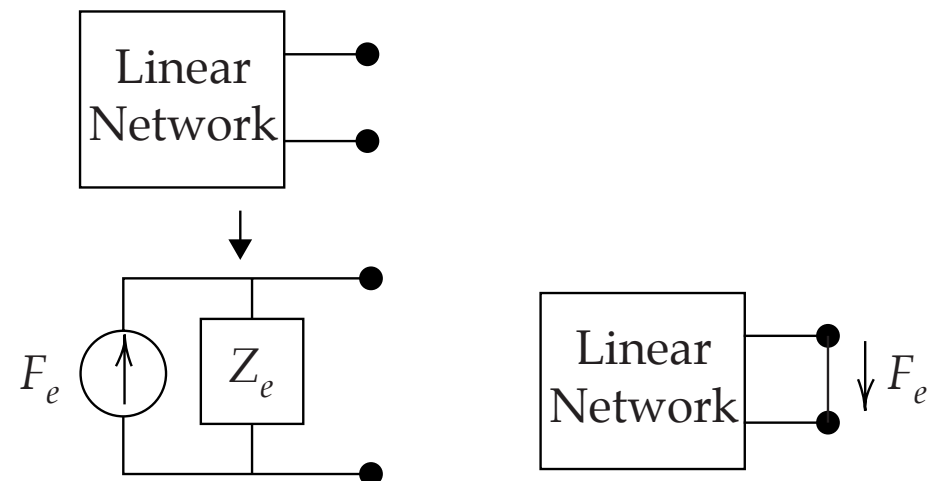F_e = a *through variable source* equal to the through variable that would flow through the *short* circuited terminals of the network.



Norton Equivalent Example

(Summary)

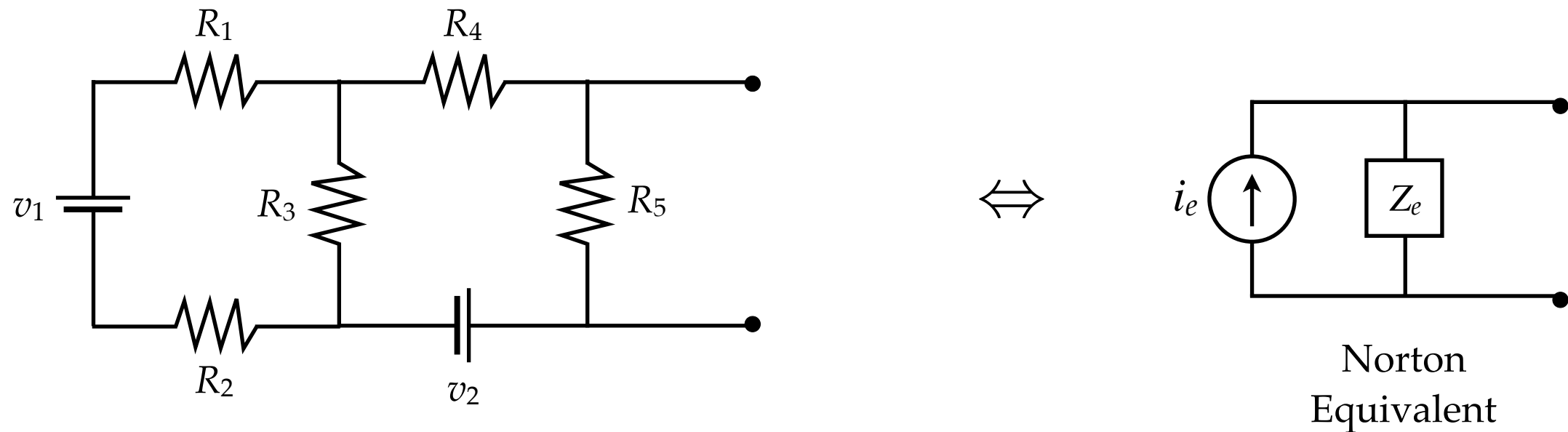

i_e = current that would flow through the short-circuited terminals of the network

Z_e = impedance^v of the network when the voltage sources are replaced by short circuits
(seen at the output port)

$$Z_e = \frac{R_5 \left[R_4 + \frac{R_3(R_1 + R_2)}{(R_3 + R_1 + R_2)} \right]}{R_5 + \left[R_4 + \frac{R_3(R_1 + R_2)}{(R_3 + R_1 + R_2)} \right]}$$


$$i_e = \frac{v_e}{Z_e} = \frac{[v_1 R_3 - v_2(R_1 + R_2 + R_3)] R_5}{(R_1 + R_2) R_3 + (R_1 + R_2 + R_3)(R_4 + R_5)} \div \frac{R_5 \left[R_4 + \frac{R_3(R_1 + R_2)}{(R_3 + R_1 + R_2)} \right]}{R_5 + \left[R_4 + \frac{R_3(R_1 + R_2)}{(R_3 + R_1 + R_2)} \right]}$$

Thevenin's Theorem

A linear two-terminal network is equivalent to an across variable source V_e in *series* with an equivalent impedance Z_e , where

Z_e = the impedance of the network with all sources set equal to zero, and

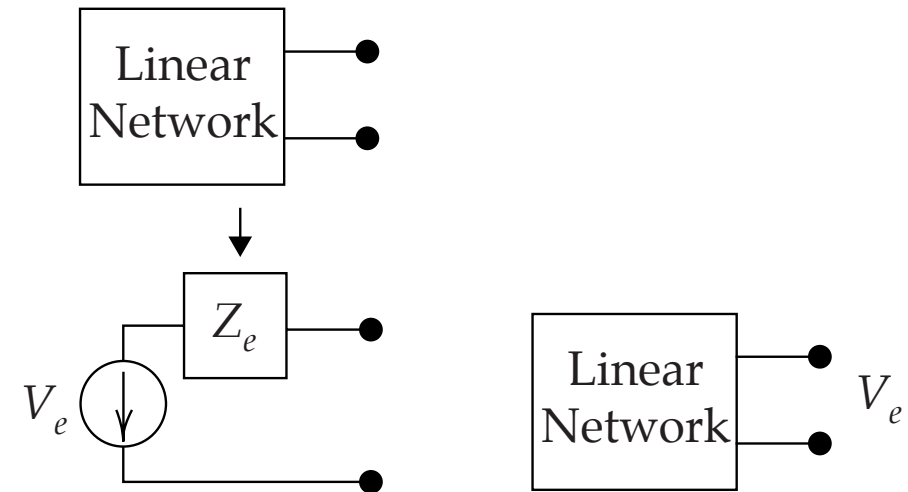V_e = an *across variable source* equal to the across variable that would appear across the *open* circuit terminals of the network.



Norton's Theorem

A linear two-terminal network is equivalent to a through variable source F_e in *parallel* with an equivalent impedance Z_e , where

Z_e = the impedance of the network with all sources set equal to zero, and

F_e = a *through variable source* equal to the through variable that would flow through the *short* circuited terminals of the network.

