

Analog Filters


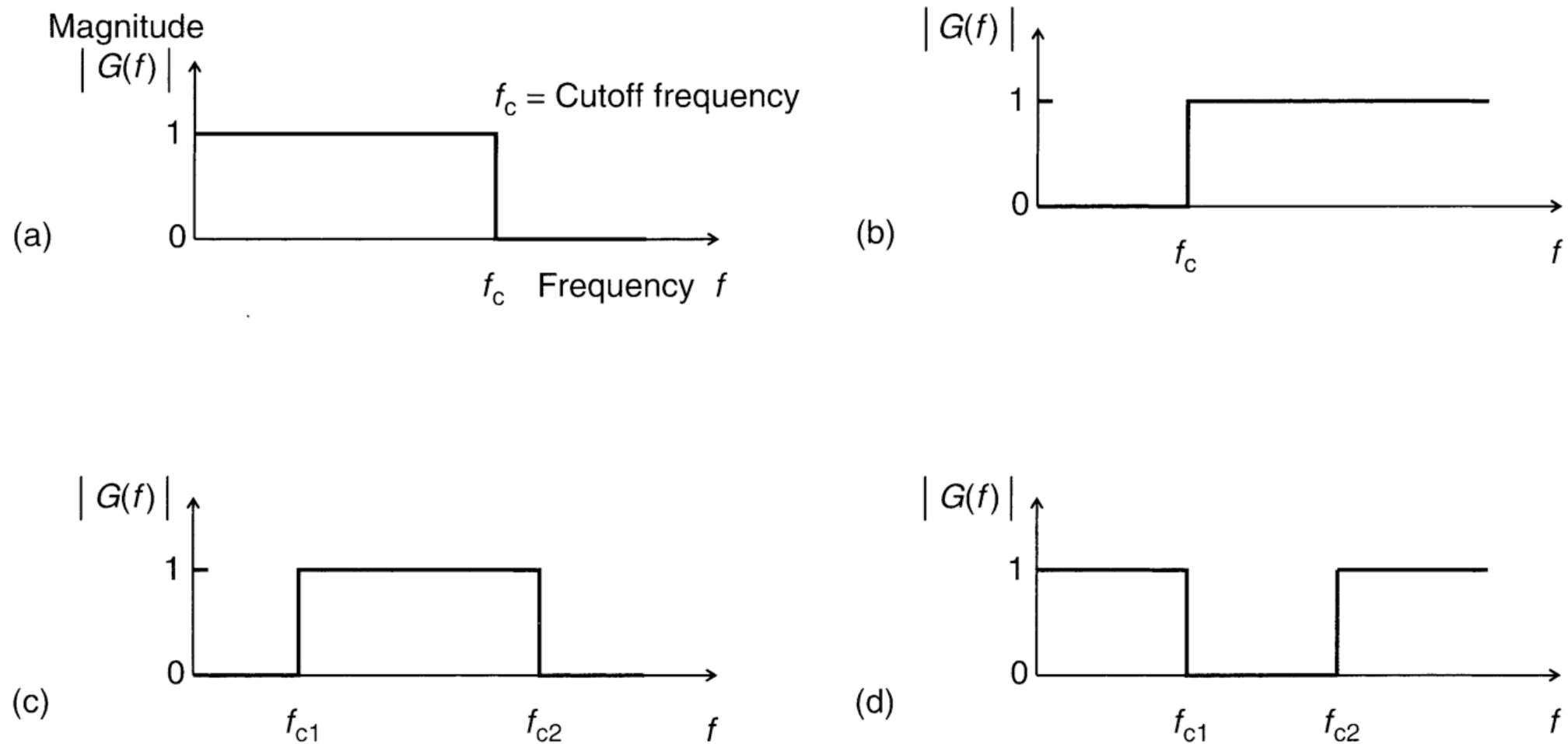


Figure 2.19

Ideal filter characteristics: (a) Low-pass filter. (b) High-pass filter. (c) Band-pass filter. (d) Band-reject (notch) filter.

passive first-order low-pass filter

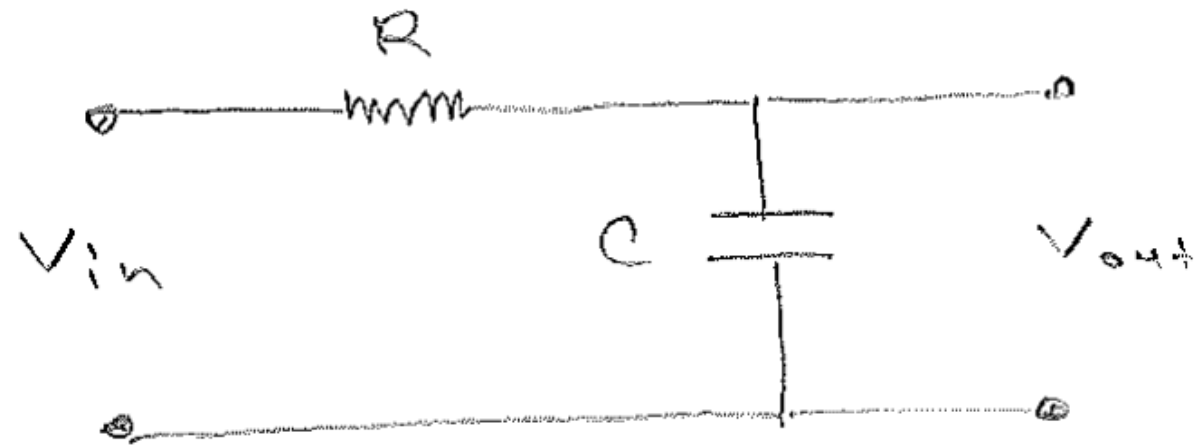


$$V_{out} = \frac{Z_c}{Z_c + Z_R} V_{in} =$$

$$= \frac{1/s}{1/s + R} V_{in} = \frac{1}{1 + RCs} V_{in}$$

$\tau = RC$ - time constant "RC time constant"

Mechanical analogy

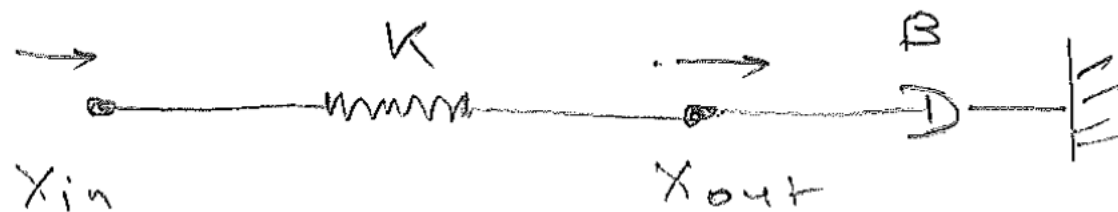

$$X_{out} = \frac{1}{1 + \tau s} X_{in}$$

$$\tau = \frac{B}{K}$$


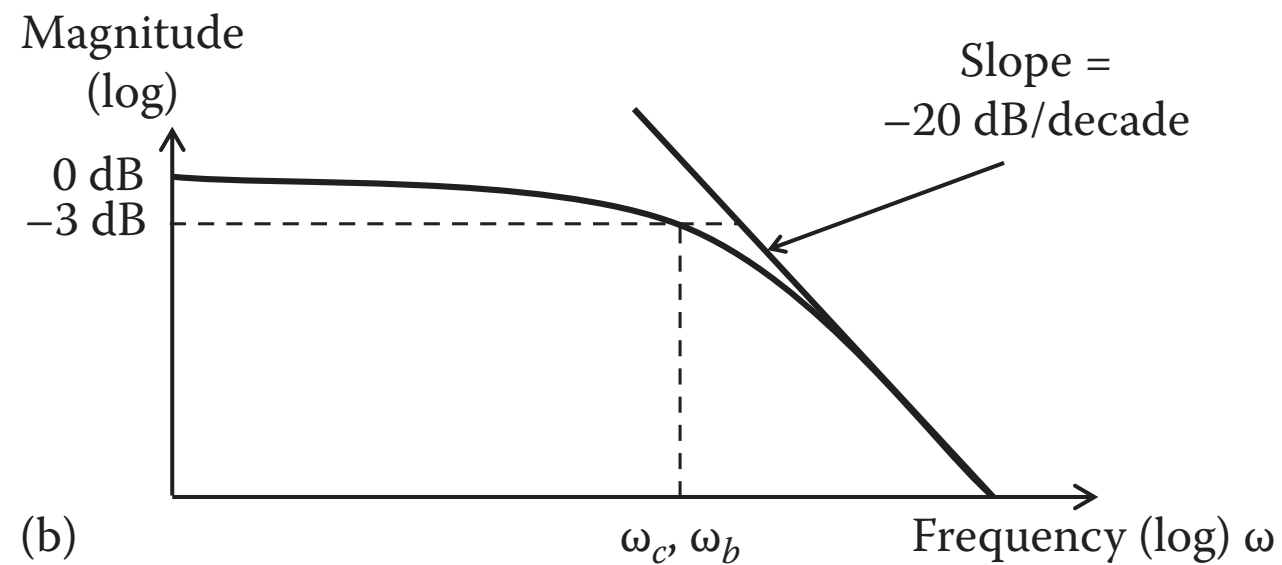
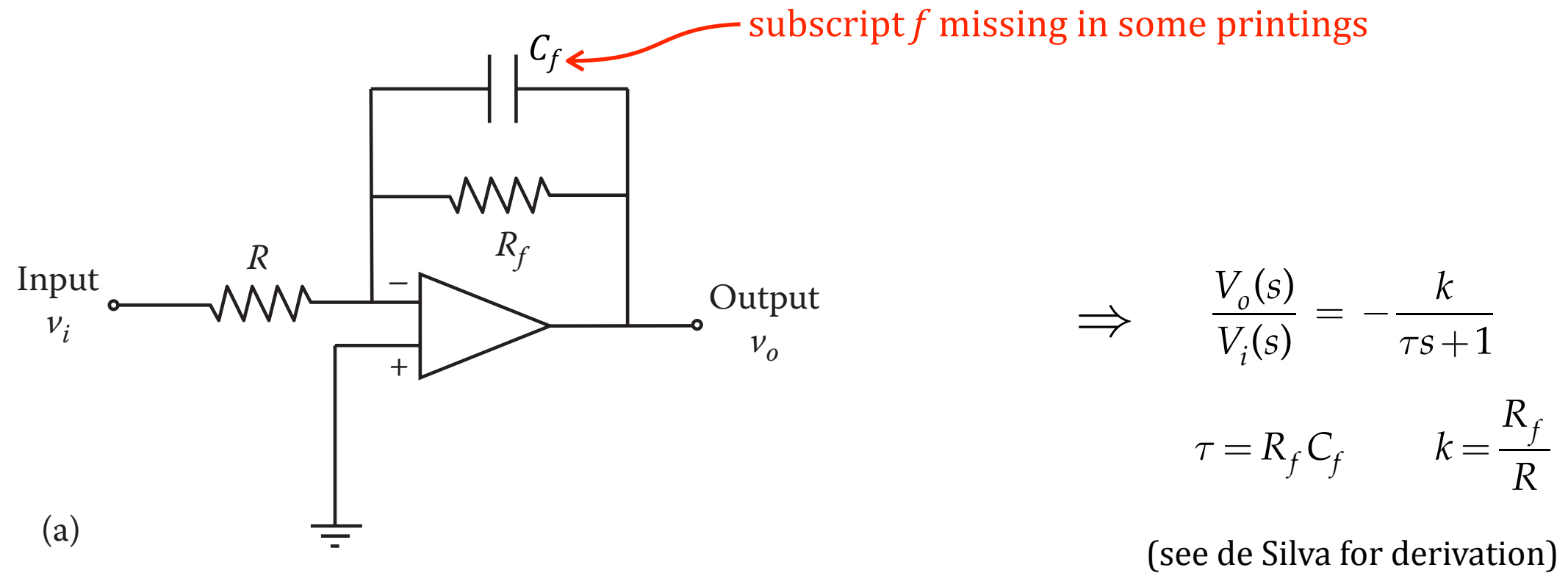


Figure 2.21 (a) A single-pole active low-pass filter (b) the frequency response characteristic.

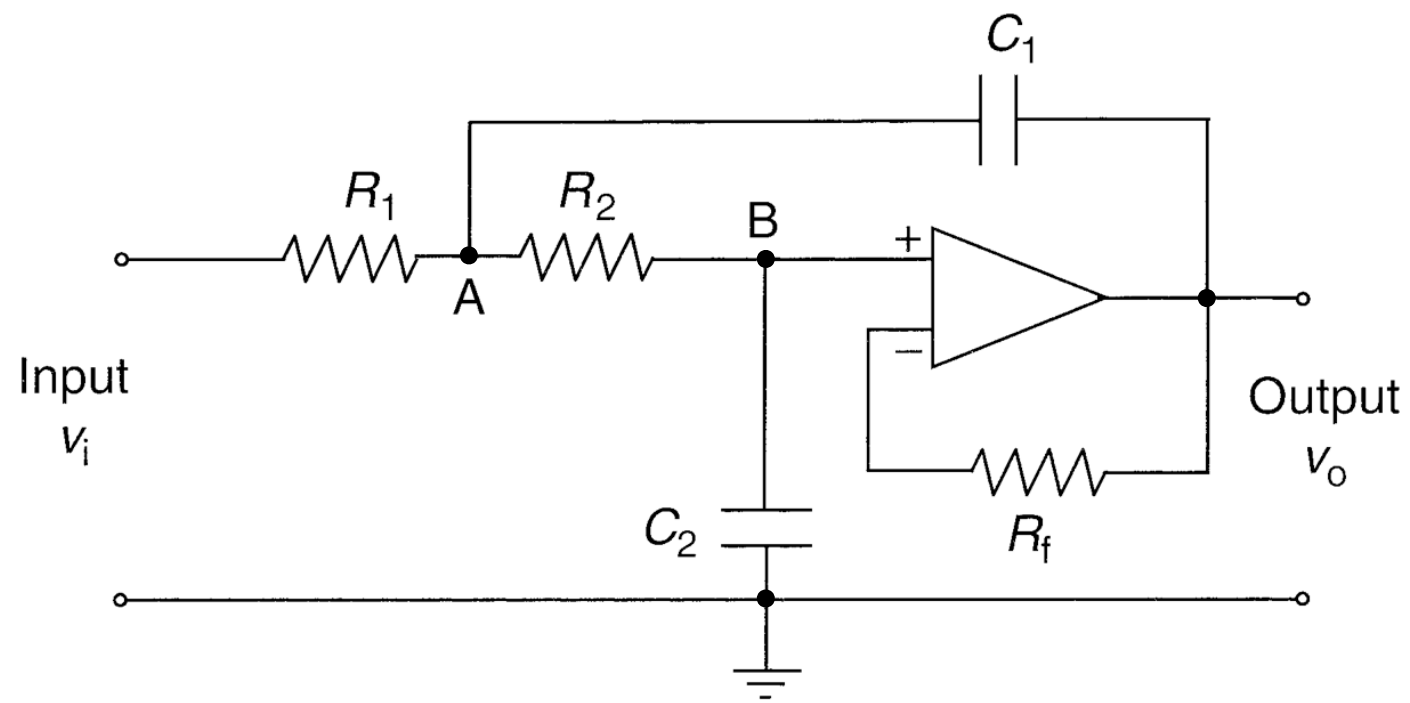



We will show that:

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{\tau_1 \tau_2 s^2 + (\tau_2 + \tau_3)s + 1}$$

$$= \frac{\omega_n^2}{s^2 + 2\zeta \omega_n s + \omega_n^2}$$

$$\tau_1 = R_1 C_1 \quad \tau_2 = R_2 C_2 \quad \tau_3 = R_1 C_2$$
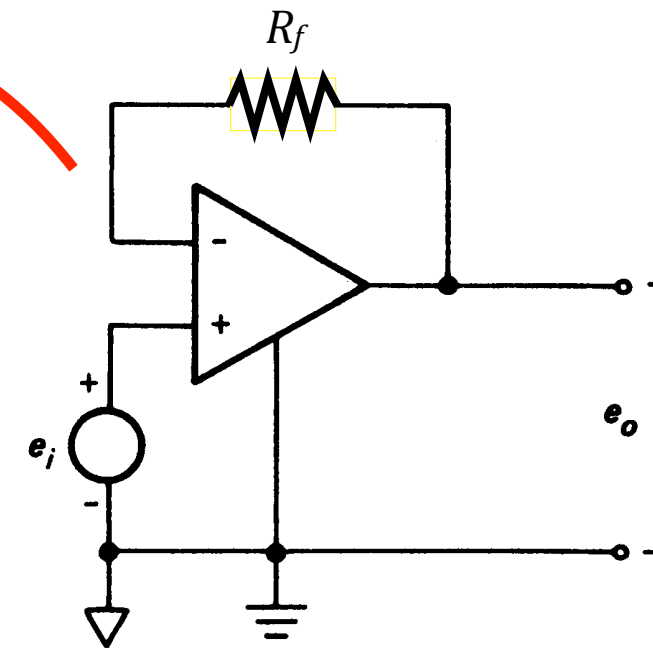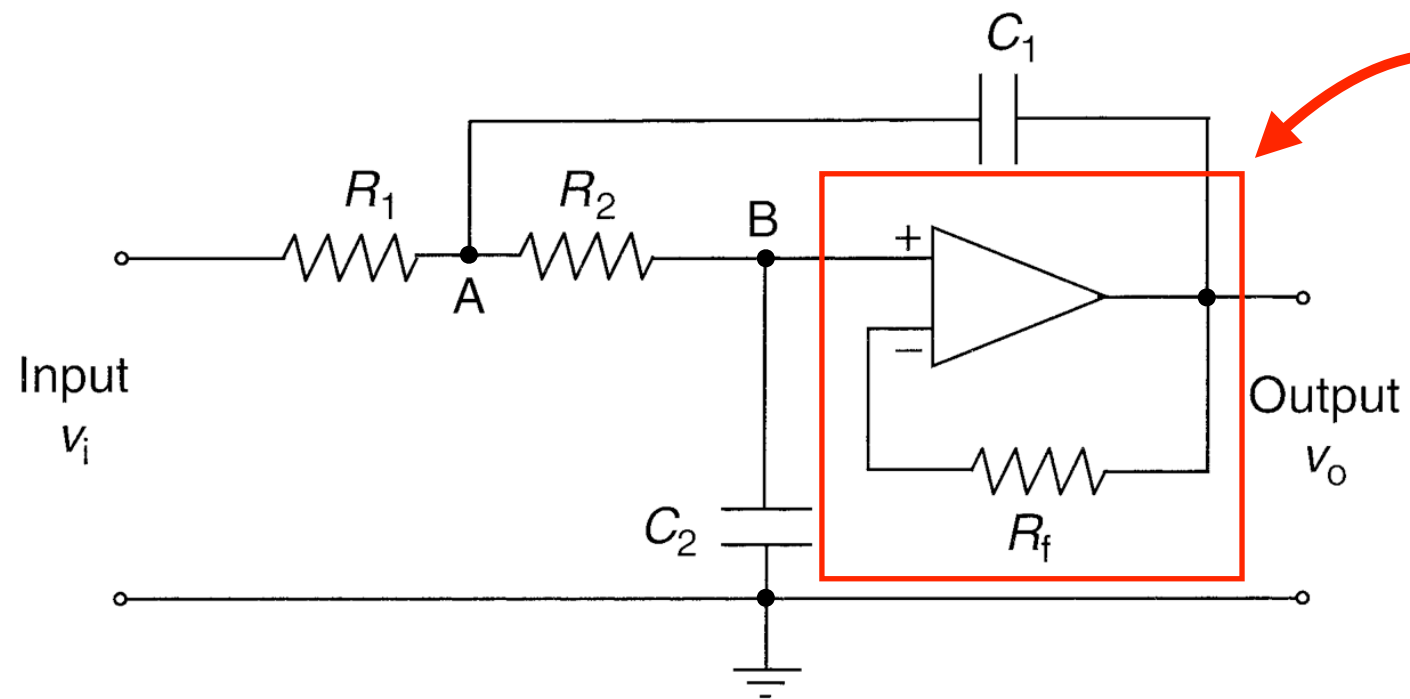
$$\omega_n = \frac{1}{\sqrt{\tau_1 \tau_2}} \quad \zeta = \frac{\tau_2 + \tau_3}{2\sqrt{\tau_1 \tau_2}}$$



Voltage Follower

Node equations for A and B yield:

$$\frac{v_i - v_A}{R_1} + C_1 \frac{d}{dt}(v_o - v_A) = \frac{v_A - v_B}{R_2} = C_2 \frac{dv_B}{dt} \quad (1)$$

Voltage follower yields:

$$v_B = v_o \quad (2)$$

From (1), using (2),

$$\frac{v_i - v_A}{R_1} + C_1 \frac{d}{dt}(v_o - v_A) = \frac{v_A - v_o}{R_2} = C_2 \frac{dv_o}{dt} \quad (3)$$

From the rightmost equation in (3)

$$v_A = R_2 C_2 \frac{dv_o}{dt} + v_o \quad (4)$$

From the leftmost equation in (3), using (4),

$$\left[v_i - \left(R_2 C_2 \frac{dv_0}{dt} + v_0 \right) \right] + R_1 C_1 \frac{d}{dt} \left[v_o - \left(R_2 C_2 \frac{dv_0}{dt} + v_0 \right) \right] = R_1 \frac{\left(R_2 C_2 \frac{dv_0}{dt} + v_0 \right) - v_0}{R_2} \quad (5)$$

Or

$$v_i = R_1 C_2 \frac{dv_0}{dt} + R_2 C_2 \frac{dv_0}{dt} + v_0 + R_1 C_1 R_2 C_2 \frac{d^2 v_0}{dt^2}$$

Or


$$v_i = \tau_3 \frac{dv_0}{dt} + \tau_2 \frac{dv_0}{dt} + v_0 + \tau_1 \tau_2 \frac{d^2 v_0}{dt^2}$$

$$\tau_1 = R_1 C_1 \quad \tau_2 = R_2 C_2 \quad \tau_3 = R_1 C_2$$

Or

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{\tau_1 \tau_2 s^2 + (\tau_2 + \tau_3) s + 1}$$

$$= \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} \quad \omega_n = \frac{1}{\sqrt{\tau_1 \tau_2}} \quad \zeta = \frac{\tau_2 + \tau_3}{2\sqrt{\tau_1 \tau_2}}$$

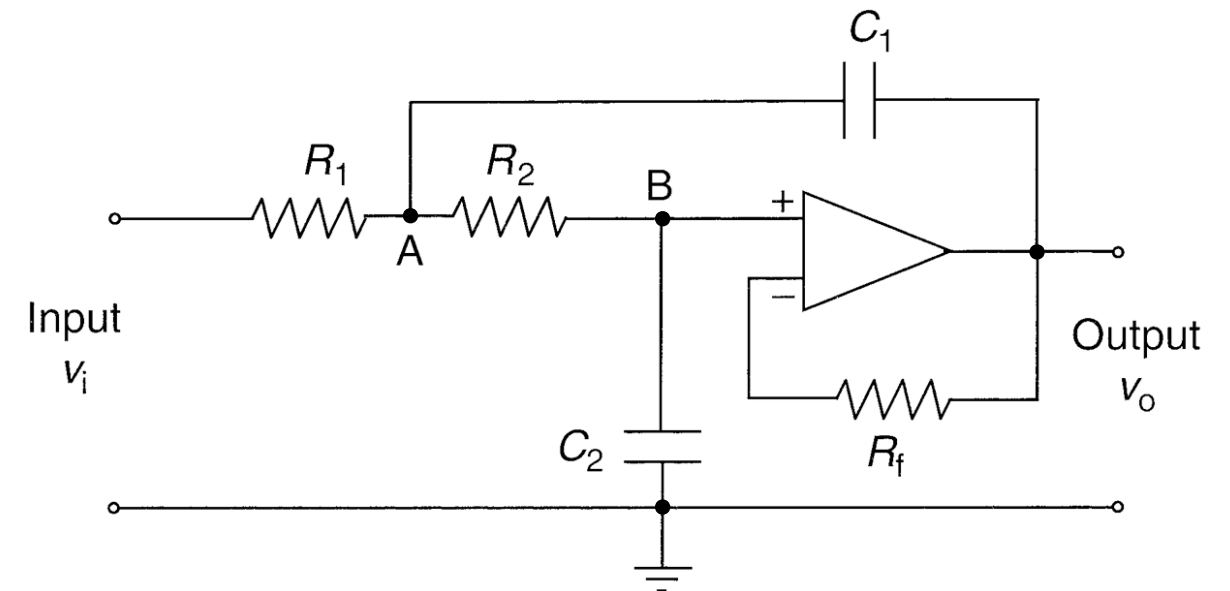

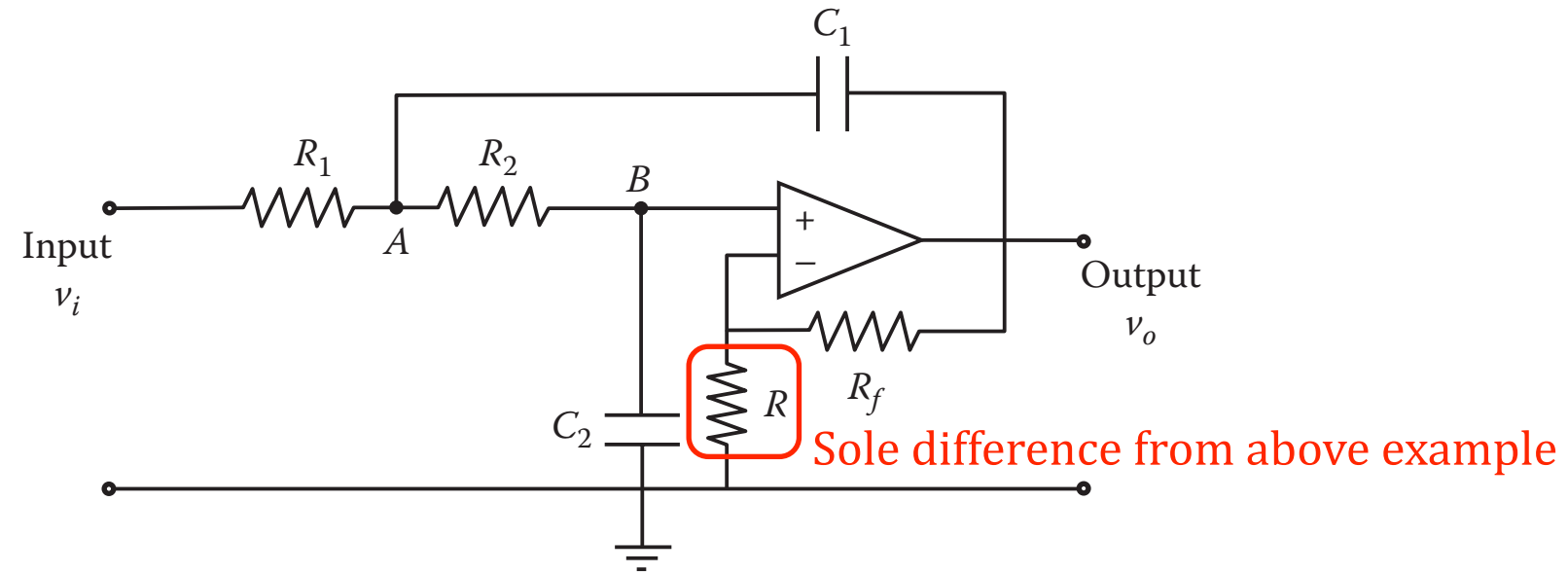



Figure 2.22 A two-pole low-pass Butterworth filter.

$$\Rightarrow \frac{V_o(s)}{V_i(s)} = \frac{1}{k[\tau_1\tau_2s^2 + ((1 - 1/k)\tau_1 + \tau_2 + \tau_3)s + 1]} = \frac{\omega_n^2}{k(s^2 + 2\zeta\omega_ns + \omega_n^2)}$$

$$\tau_1 = R_1C_1 \quad \tau_2 = R_2C_2 \quad \tau_3 = R_1C_2 \quad \omega_n = \frac{1}{\sqrt{\tau_1\tau_2}}$$

$$k = \frac{R}{R_f} \quad \zeta = \frac{(1 - 1/k)\tau_1 + \tau_2 + \tau_3}{2\sqrt{\tau_1\tau_2}}$$

(see de Silva for derivation)

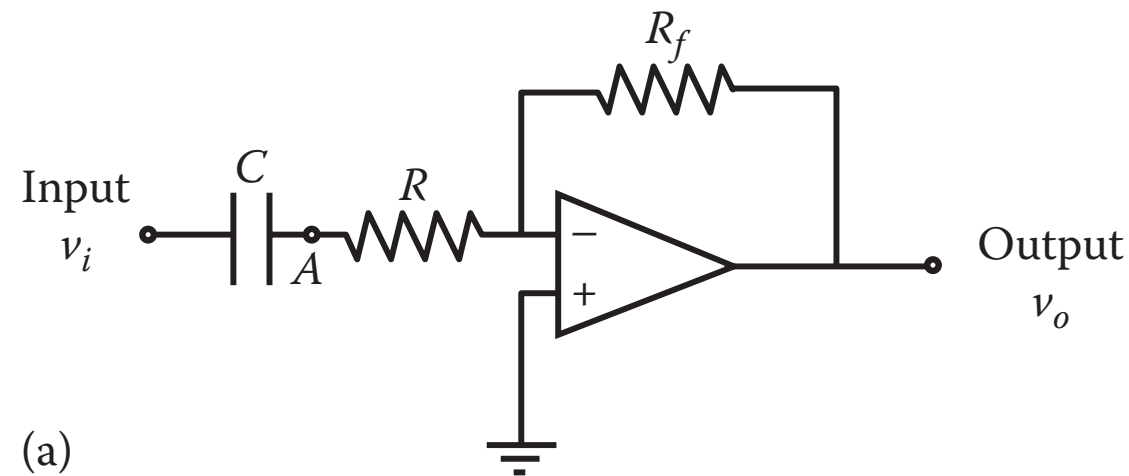


(a)

de Silva's Eq. 2.54 is incorrect
(sign error)

$$\Rightarrow \frac{V_o(s)}{V_i(s)} = -\frac{R_f}{R} \frac{\tau s}{\tau s + 1}$$


$$\tau = RC$$

(derived below)

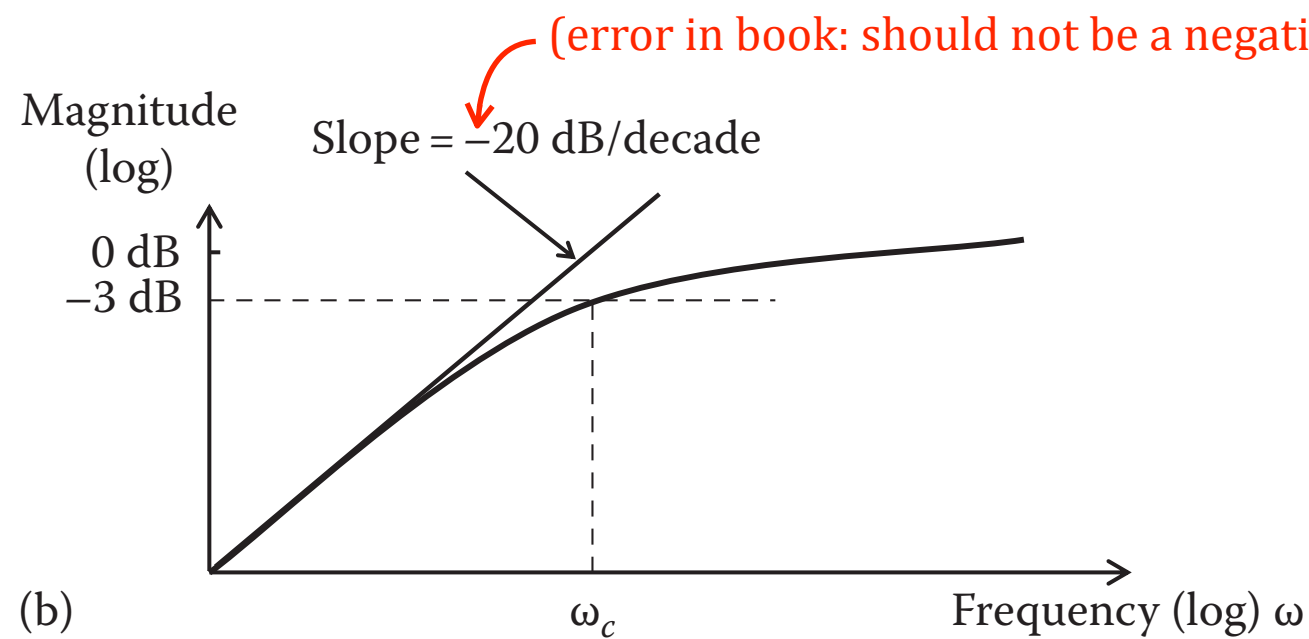

(b)

Figure 2.24 (a) A single-pole high-pass filter (b) frequency response characteristic

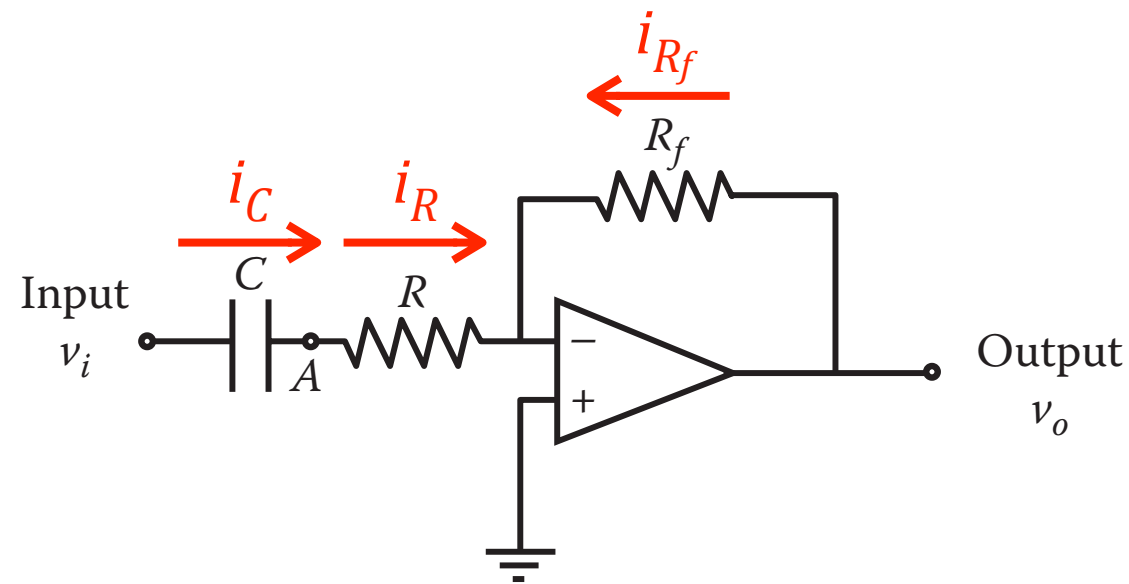

$$i_C = i_R = -i_{R_f}$$


$$\begin{aligned} \Rightarrow C \frac{d}{dt}(v_i - v_A) &= \frac{v_A}{R} = -\frac{v_o}{R_f} \\ \Rightarrow v_A &= -\frac{R}{R_f} v_o \end{aligned} \quad \left. \vphantom{\begin{aligned} \Rightarrow C \frac{d}{dt}(v_i - v_A) &= \frac{v_A}{R} = -\frac{v_o}{R_f} \\ \Rightarrow v_A &= -\frac{R}{R_f} v_o \end{aligned}} \right\} \Rightarrow C \frac{d}{dt}\left(v_i + \frac{R}{R_f} v_o\right) = -\frac{v_o}{R_f}$$

$$\Rightarrow C \frac{dv_i}{dt} = -\frac{RC}{R_f} \frac{dv_o}{dt} - \frac{v_o}{R_f}$$

$$\Rightarrow \frac{R_f}{R} RC \frac{dv_i}{dt} = -RC \frac{dv_o}{dt} - v_o$$

$$\Rightarrow \frac{V_o(s)}{V_i(s)} = -\frac{R_f}{R} \frac{\tau s}{\tau s + 1}$$

$$\tau = RC$$

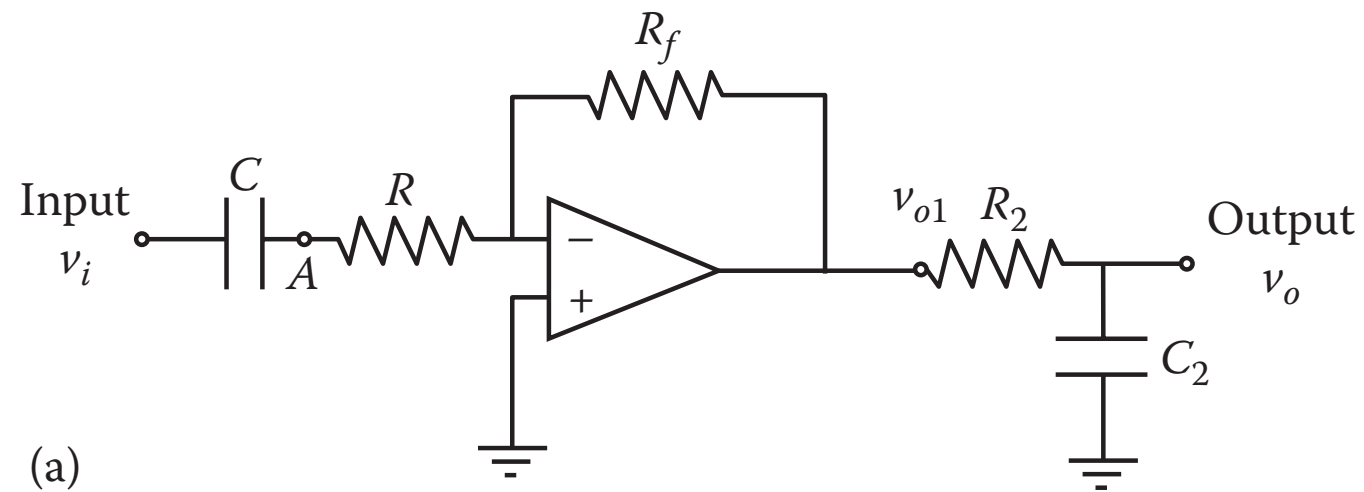

$$\Rightarrow \frac{V_o(s)}{V_i(s)} = \frac{\tau s}{(\tau s + 1)(\tau_2 s + 1)}$$

complex roots not possible

$$\tau = RC \quad \tau_2 = R_2 C_2$$

(see de Silva for derivation)


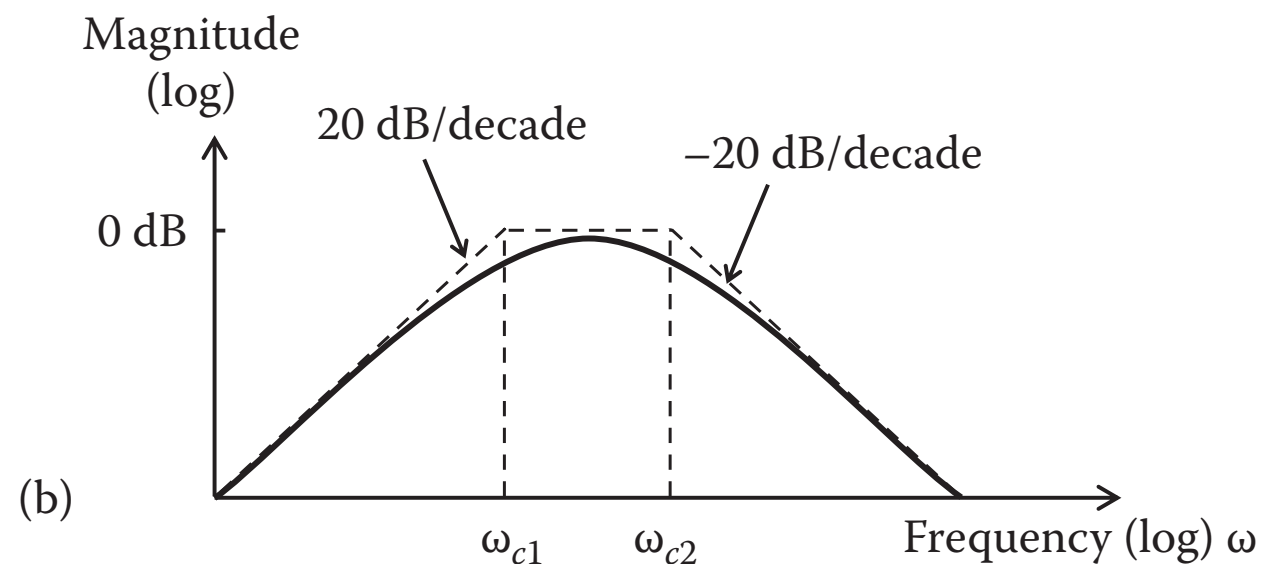


Figure 2.25 (a) An active band-pass filter
(b) Frequency response characteristic

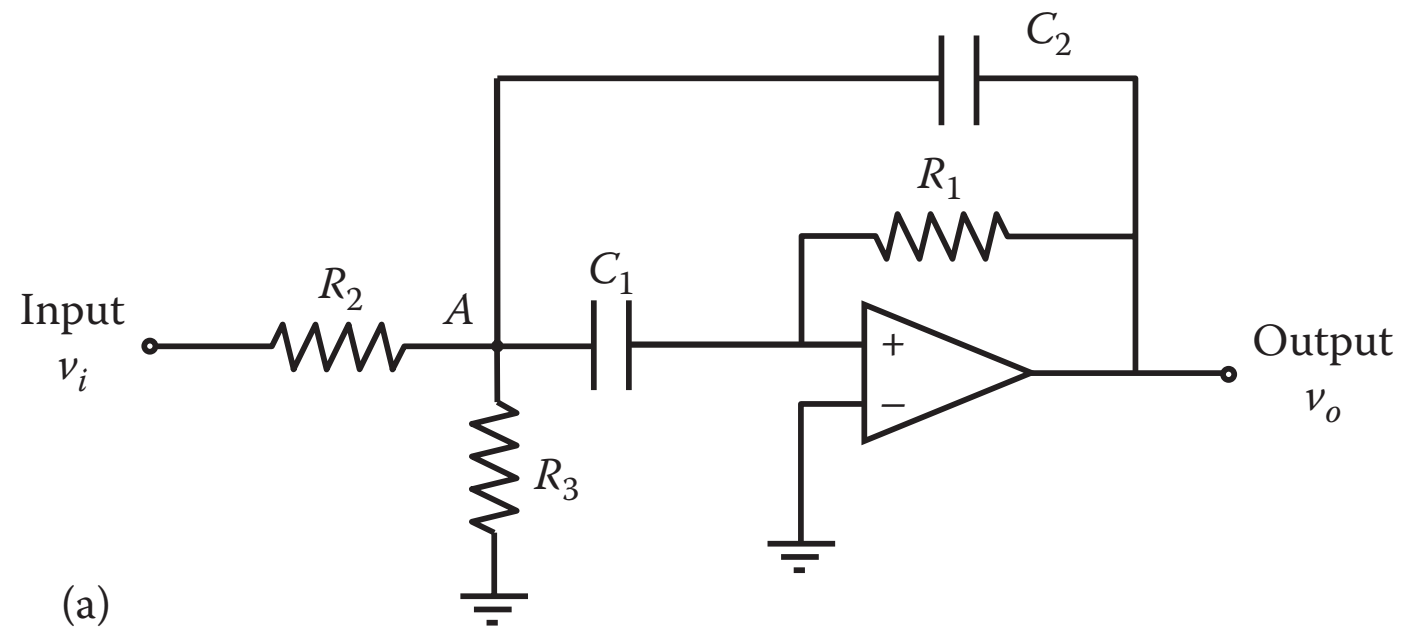

$$\Rightarrow \frac{V_o(s)}{V_i(s)} = - \frac{\tau_1 s}{\tau_1 \tau_2 s^2 + (k_1 \tau_1 + \tau_2) s + (1 + k_2)}$$

complex roots are possible

$$\tau_1 = R_1 C_1 \quad \tau_2 = R_2 C_2$$

$$k_1 = \frac{R_2}{R_1} \quad k_2 = \frac{R_2}{R_3}$$

(see de Silva for derivation)


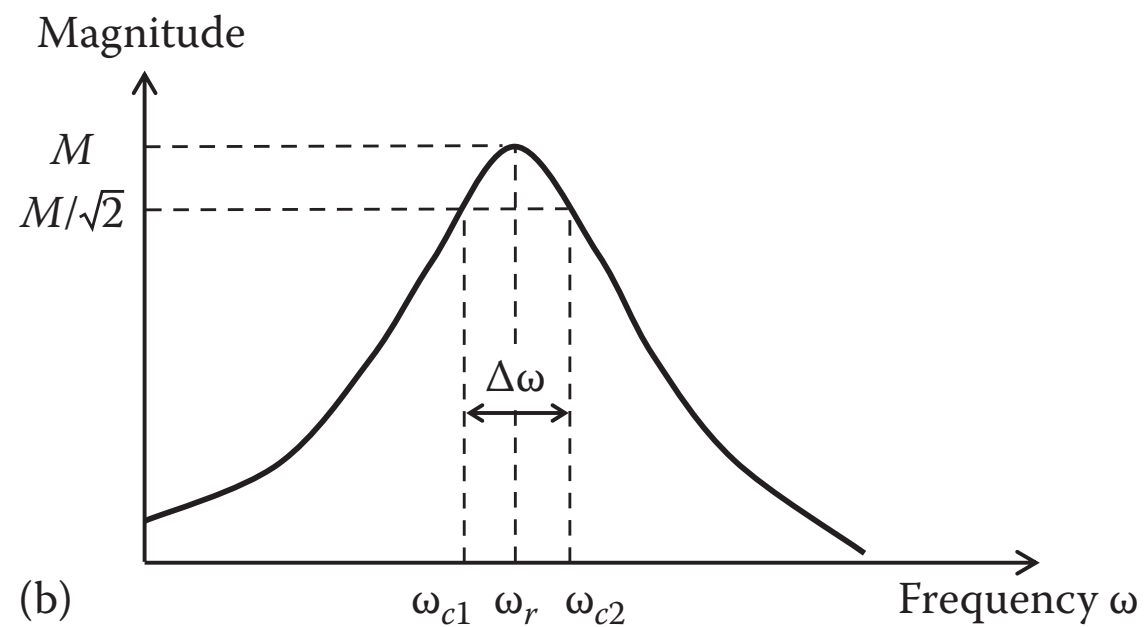



Figure 2.26 (a) A resonance-type narrow band-pass filter
(b) frequency response characteristic

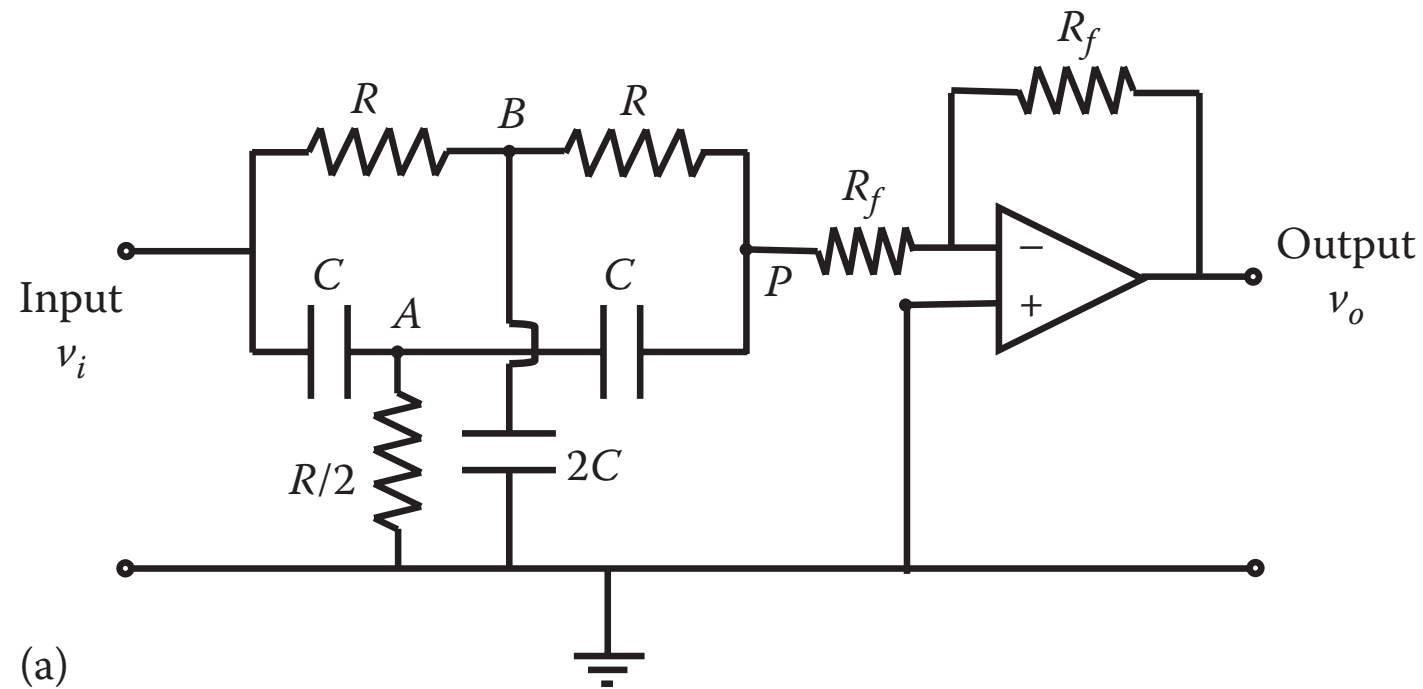

$$\Rightarrow \frac{V_o(s)}{V_i(s)} = - \frac{\tau^2 s^2 + 1}{\tau^2 s^2 + (4 + k)\tau s + (1 + 2k)}$$

$$\tau = RC \quad k = \frac{R}{R_f}$$

(see de Silva for derivation)

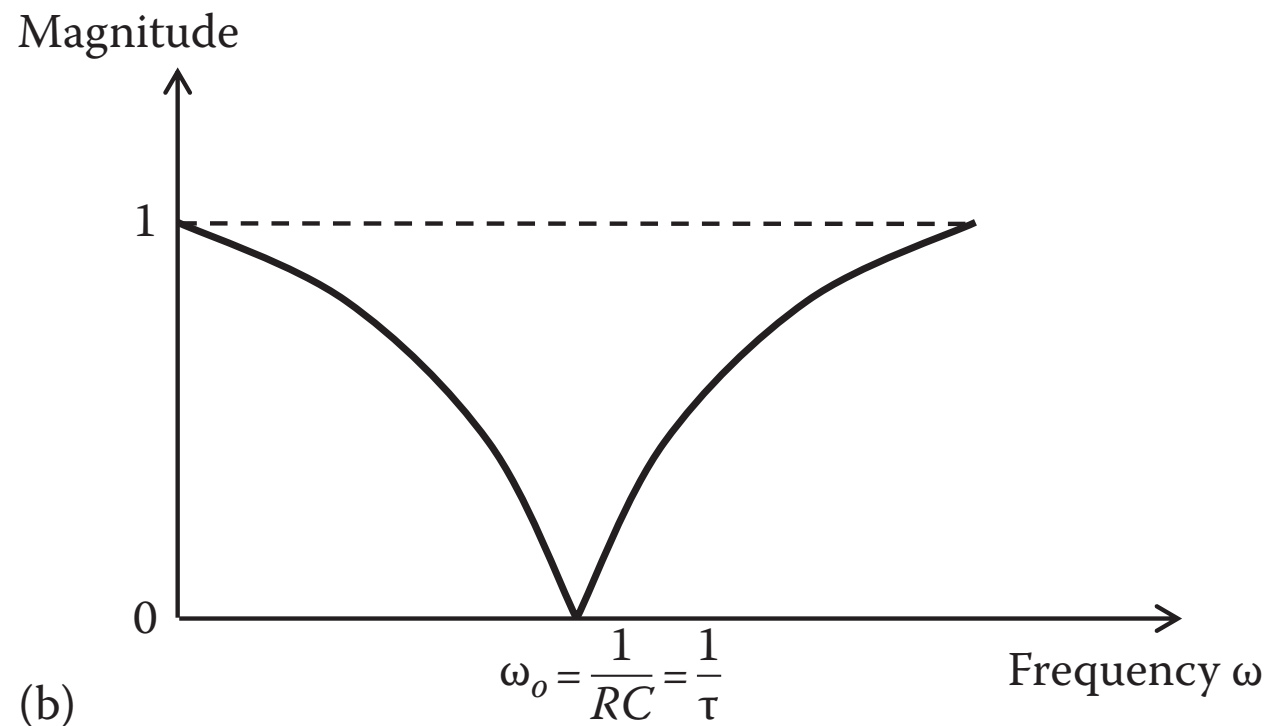

a.k.a. a *band-reject* or *notch* filter

Figure 2.27 (a) A twin T filter circuit

(b) Frequency response characteristic

Signal Modulation


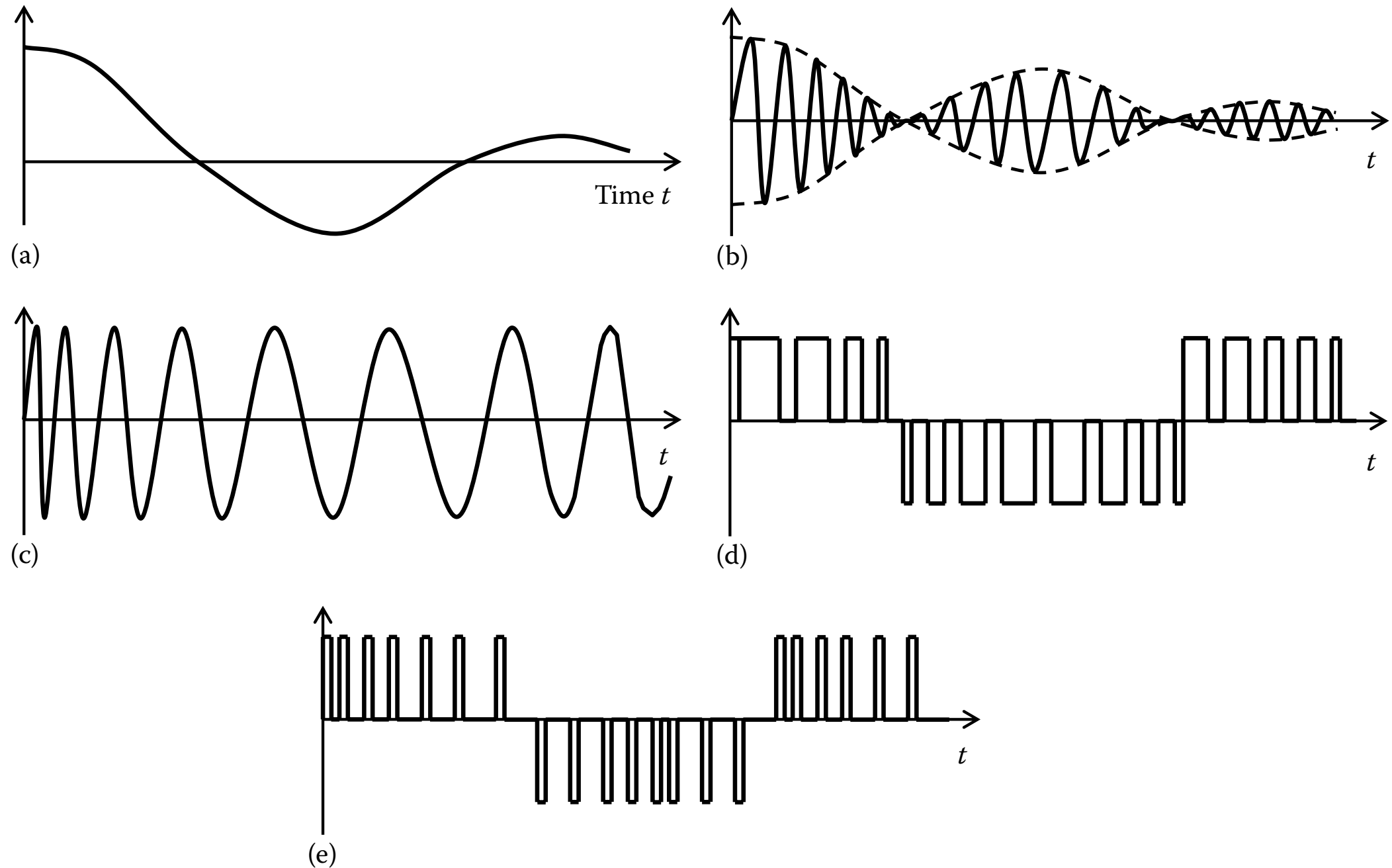


FIGURE 2.28 (a) Modulating signal (data signal), (b) amplitude-modulated (AM) signal, (c) frequency-modulated (FM) signal, (d) pulse-width-modulated (PWM) signal, and (e) pulse-frequency-modulated (PFM) signal.

AM Radio

Amplitude Modulation

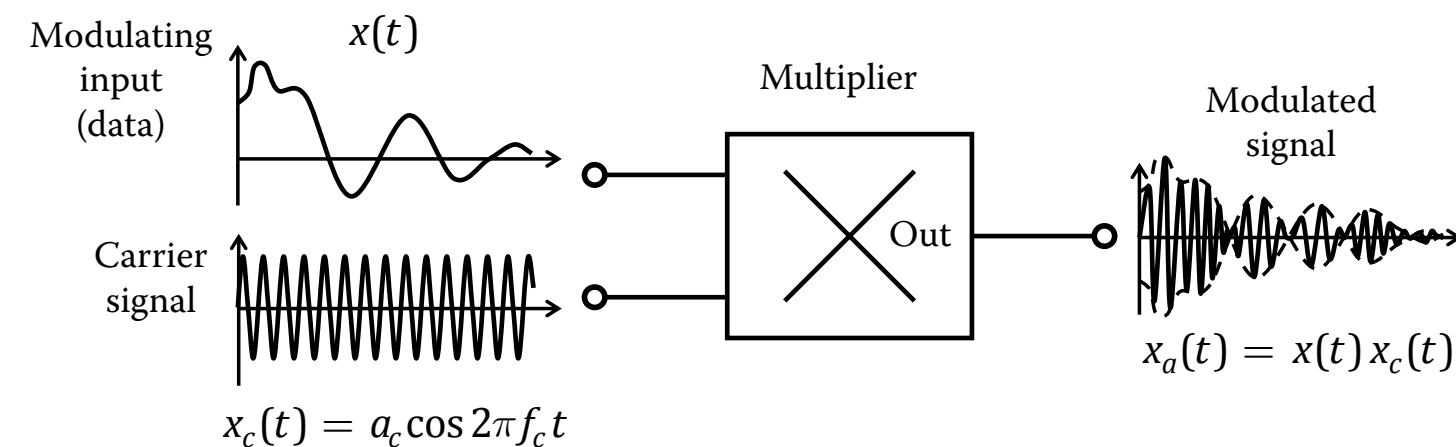


Why amplitude modulate radio signals?

1. The sum of the modulated signals from multiple radio stations can be broadcast over long distances.
2. It is relatively easy to recover one radio station's data signal, $x(t)$, from the sum of the modulated signals from multiple radio stations.

AM Radio

Amplitude Modulation

Demodulation

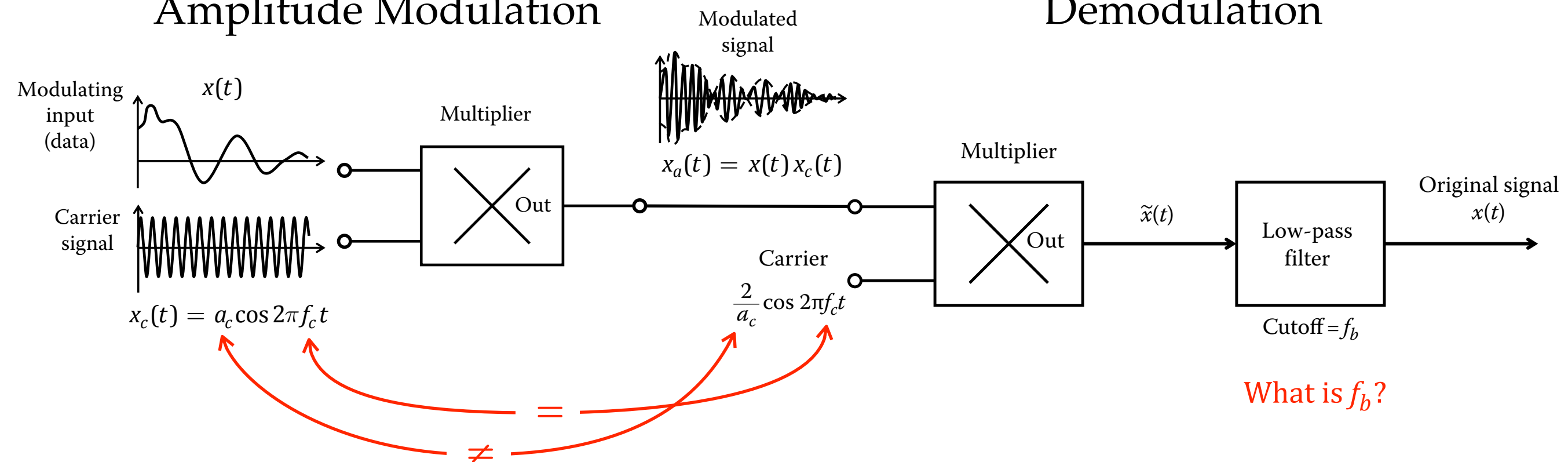


What conditions guarantee that above demodulation scheme recovers $x(t)$ exactly?

How did somebody come up with the above scheme?

What does $x_a(t) = x(t) x_c(t)$ look like, in the frequency domain?

AM Radio

Amplitude Modulation

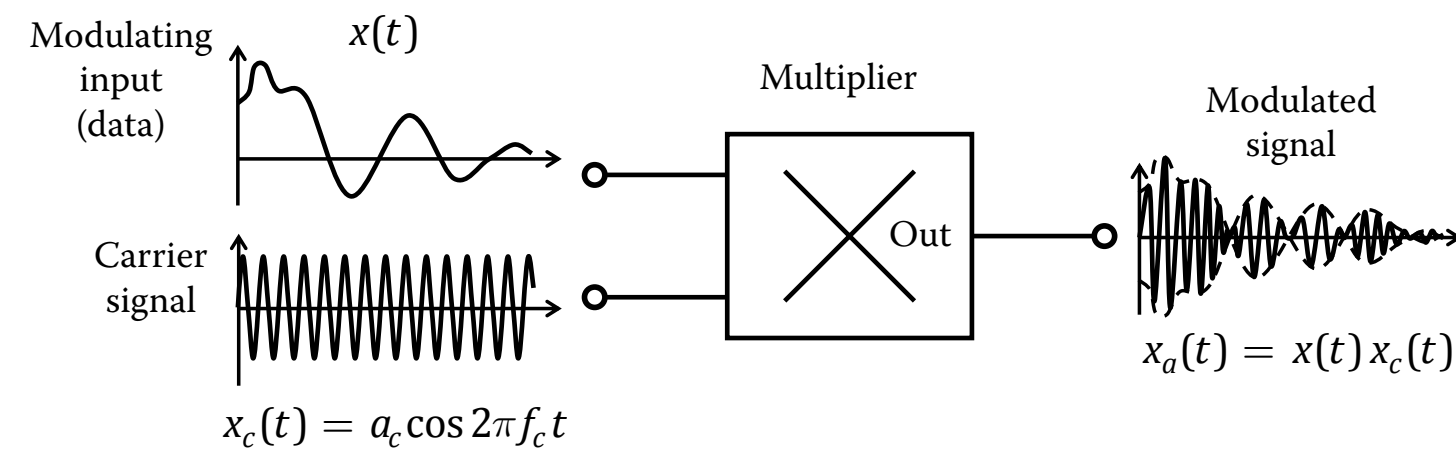

What does $x_a(t) = x(t) x_c(t)$ look like, in the frequency domain?

What does $x_a(t) = x(t) x_c(t)$ look like, in the frequency domain?

The Fourier transform, $X_a(j\omega)$, of $x_a(t)$, is:

$$X_a(j\omega) = \int_{-\infty}^{+\infty} x_a(t) e^{-j\omega t} dt$$

where ω is the frequency in radians/sec.


Or we can choose to measure frequency in cycles/sec, and write the above as

$$X_a(f) = \int_{-\infty}^{+\infty} x_a(t) e^{-j2\pi f t} dt$$

where f is the frequency in cycles/sec.

AM Radio

Amplitude Modulation

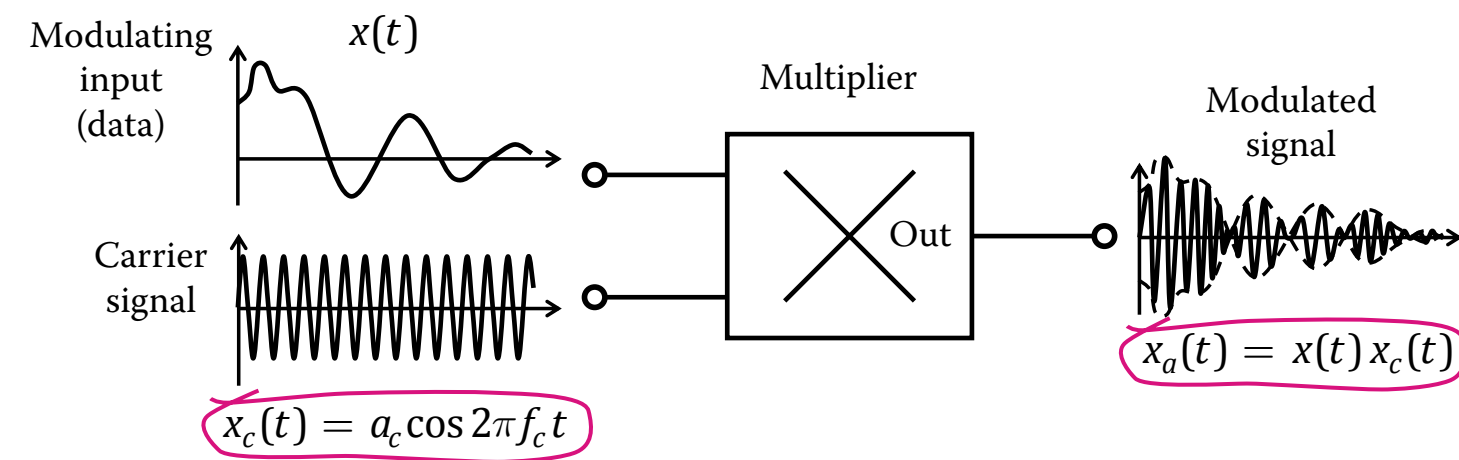

What does $x_a(t) = x(t) x_c(t)$ look like, in the frequency domain?

The Fourier transform, $X_a(j\omega)$, of $x_a(t)$, is:

$$X_a(j\omega) = \int_{-\infty}^{+\infty} x_a(t) e^{-j\omega t} dt$$

where ω is the frequency in radians/sec.

Or we can choose to measure frequency in cycles/sec, and write the above as

$$X_a(f) = \int_{-\infty}^{+\infty} x_a(t) e^{-j2\pi f t} dt$$

where f is the frequency in cycles/sec.

Here

$$x_a(t) = x(t) x_c(t) = x(t) a_c \cos(2\pi f_c t)$$

What does $x_a(t) = x(t) x_c(t)$ look like, in the frequency domain?

From Euler's formulas,

$$\cos(\omega_c t) = \frac{e^{j\omega_c t} + e^{-j\omega_c t}}{2}$$

where ω_c is the frequency in radians/sec.

Or we can choose to measure frequency in cycles/sec, and write the above as

$$\cos(2\pi f_c t) = \frac{e^{j2\pi f_c t} + e^{-j2\pi f_c t}}{2}$$

where f_c is the frequency in cycles/sec.

$$x_a(t) = x(t) x_c(t) = x(t) a_c \cos(2\pi f_c t)$$

What does $x_a(t) = x(t) x_c(t)$ look like, in the frequency domain?

The Fourier transform, $X_a(j\omega)$, of $x_a(t)$, is:

$$X_a(j\omega) = \int_{-\infty}^{+\infty} x_a(t) e^{-j\omega t} dt$$

where ω is the frequency in radians/sec.

Or we can choose to measure frequency in cycles/sec, and write the above as

$$X_a(f) = \int_{-\infty}^{+\infty} x_a(t) e^{-j2\pi f t} dt$$

where f is the frequency in cycles/sec.

Here

$$x_a(t) = x(t) x_c(t) = x(t) a_c \cos(2\pi f_c t)$$

What does $x_a(t) = x(t) x_c(t)$ look like, in the frequency domain?

Now from

$$X_a(f) = \int_{-\infty}^{+\infty} x_a(t) e^{-j2\pi f t} dt$$

using

$$x_a(t) = x(t) x_c(t) = x(t) a_c \cos(2\pi f_c t)$$

and

$$\cos(2\pi f_c t) = \frac{e^{j2\pi f_c t} + e^{-j2\pi f_c t}}{2}$$

we have that

$$\begin{aligned} X_a(f) &= \frac{1}{2} a_c \int_{-\infty}^{+\infty} x(t) \left[e^{j2\pi f_c t} + e^{-j2\pi f_c t} \right] e^{-j2\pi f t} dt \\ &= \frac{1}{2} a_c \int_{-\infty}^{+\infty} x(t) \left[e^{-j2\pi(f-f_c)t} + e^{-j2\pi(f+f_c)t} \right] dt \\ &= \frac{1}{2} a_c \int_{-\infty}^{+\infty} x(t) e^{-j2\pi(f-f_c)t} dt + \frac{1}{2} a_c \int_{-\infty}^{+\infty} x(t) e^{-j2\pi(f+f_c)t} dt \end{aligned}$$

What does $x_a(t) = x(t) x_c(t)$ look like, in the frequency domain?

Now from

$$X_a(f) = \int_{-\infty}^{+\infty} x_a(t) e^{-j2\pi f t} dt$$

using

$$x_a(t) = x(t) x_c(t) = x(t) a_c \cos(2\pi f_c t)$$

and

$$\cos(2\pi f_c t) = \frac{e^{j2\pi f_c t} + e^{-j2\pi f_c t}}{2}$$

we have that

$$\begin{aligned} X_a(f) &= \frac{1}{2} a_c \int_{-\infty}^{+\infty} x(t) \left[e^{j2\pi f_c t} + e^{-j2\pi f_c t} \right] e^{-j2\pi f t} dt \\ &= \frac{1}{2} a_c \int_{-\infty}^{+\infty} x(t) \left[e^{-j2\pi(f-f_c)t} + e^{-j2\pi(f+f_c)t} \right] dt \\ &= \frac{1}{2} a_c \int_{-\infty}^{+\infty} x(t) e^{-j2\pi(f-f_c)t} dt + \frac{1}{2} a_c \int_{-\infty}^{+\infty} x(t) e^{-j2\pi(f+f_c)t} dt \end{aligned}$$

What does $x_a(t) = x(t) x_c(t)$ look like, in the frequency domain?

Finally, using

$$X_a(f) = \frac{1}{2} a_c \int_{-\infty}^{+\infty} x(t) e^{-j2\pi(f-f_c)t} dt + \frac{1}{2} a_c \int_{-\infty}^{+\infty} x(t) e^{-j2\pi(f+f_c)t} dt$$

and

$$X(f) = \int_{-\infty}^{+\infty} x(t) e^{-j2\pi f t} dt$$

we have that

$$X_a(f) = \frac{1}{2} a_c \underbrace{X(f - f_c)}_{\substack{\text{Fourier} \\ \text{transfer} \\ \text{of } x(t) \\ \text{shifted } \textcolor{red}{\textit{right}} \\ \text{in frequency} \\ \text{by } f_c}} + \frac{1}{2} a_c \underbrace{X(f + f_c)}_{\substack{\text{Fourier} \\ \text{transfer} \\ \text{of } x(t) \\ \text{shifted } \textcolor{blue}{\textit{left}} \\ \text{in frequency} \\ \text{by } f_c}} \quad (\text{de Silva's Equation 2.76})$$



What does $x_a(t) = x(t) x_c(t)$ look like, in the frequency domain?

From

$$X_a(f) = \frac{1}{2}a_c X(f - f_c) + \frac{1}{2}a_c X(f + f_c) \quad (\text{de Silva's Equation 2.76})$$

if

$$x(t) = a \cos 2\pi f_0 t$$

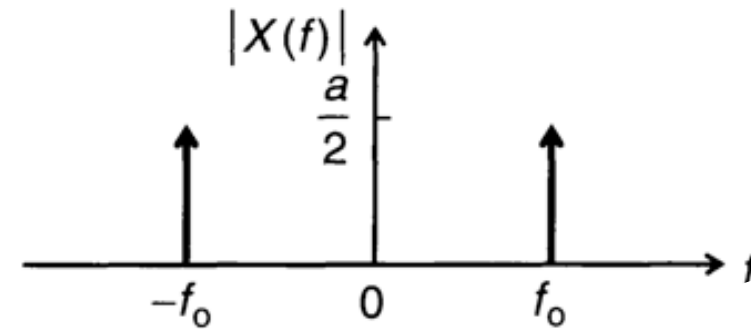
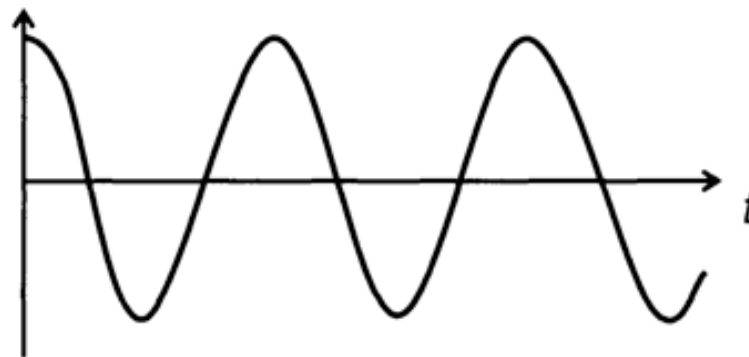


multiply by $a_c/2$
and
shift left by f_c

multiply by $a_c/2$
and
shift right by f_c

then
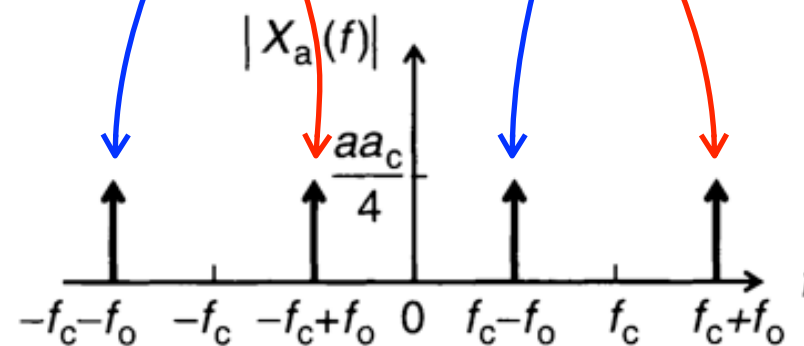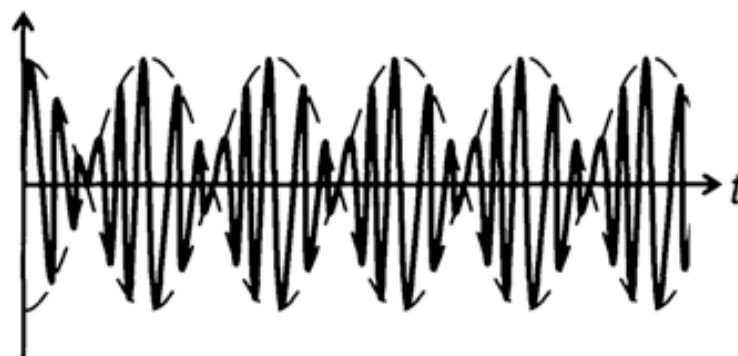
$$x_a(t) = aa_c \cos 2\pi f_0 t \cos 2\pi f_c t$$




What does $x_a(t) = x(t) x_c(t)$ look like, in the frequency domain?


From

$$X_a(f) = \frac{1}{2}a_c X(f - f_c) + \frac{1}{2}a_c X(f + f_c) \quad (\text{de Silva's Equation 2.76})$$

if

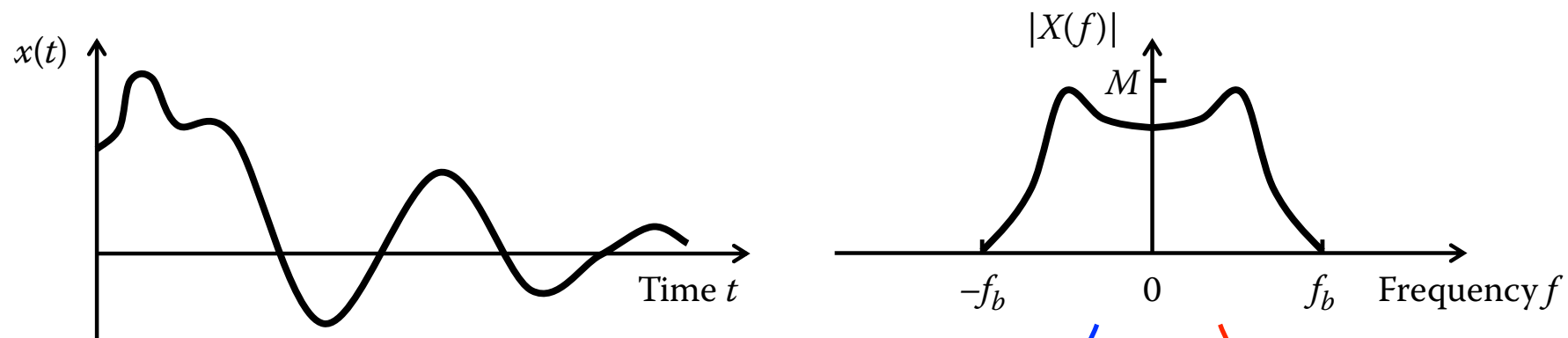


then

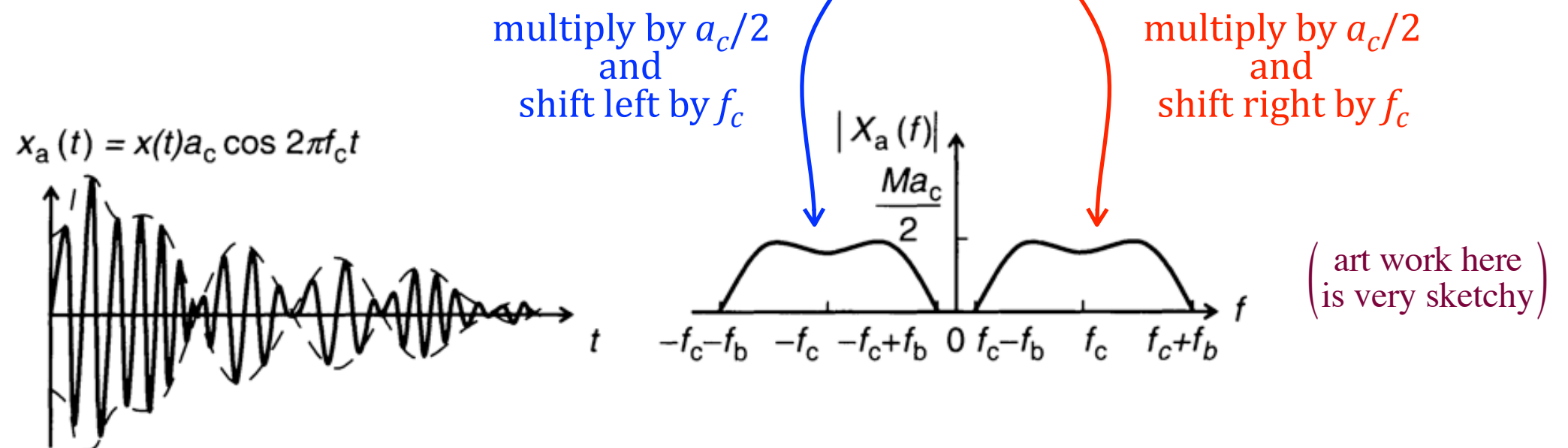


About Demodulation

If we take

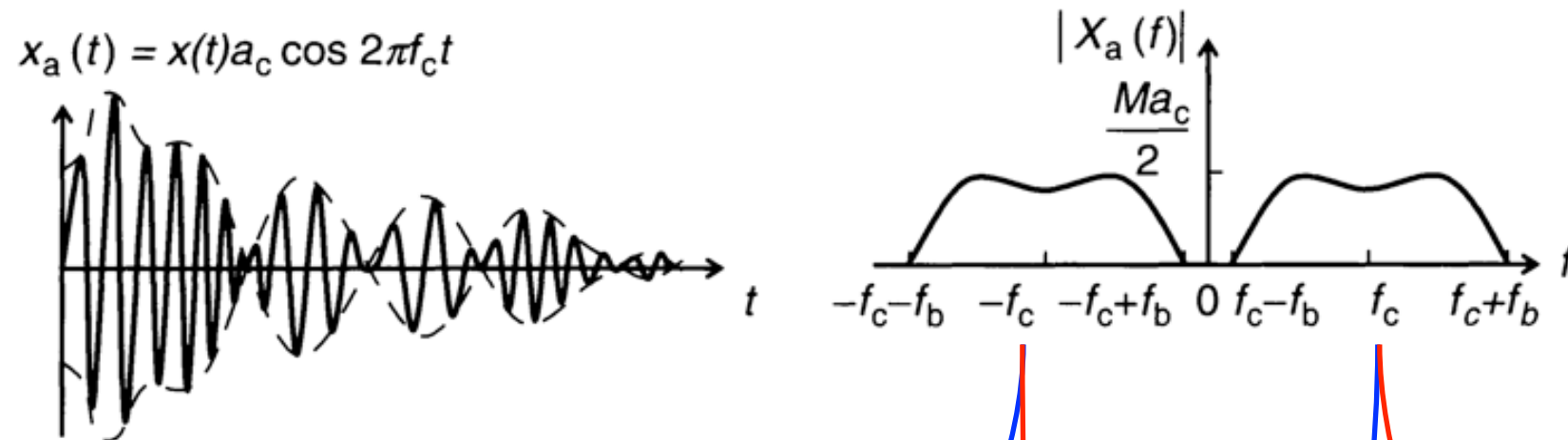


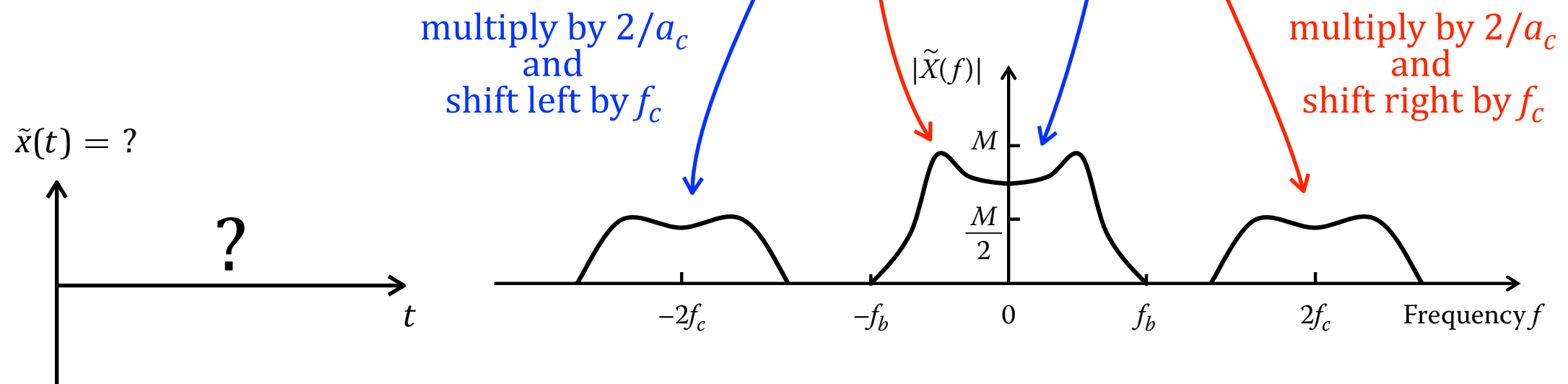and multiply it by $2/a_c$, and then sum the **left-shifted-by- f_c** and **right-shifted by f_c** versions of the multiplied signal, the resulting signal will be




About Demodulation

If we take

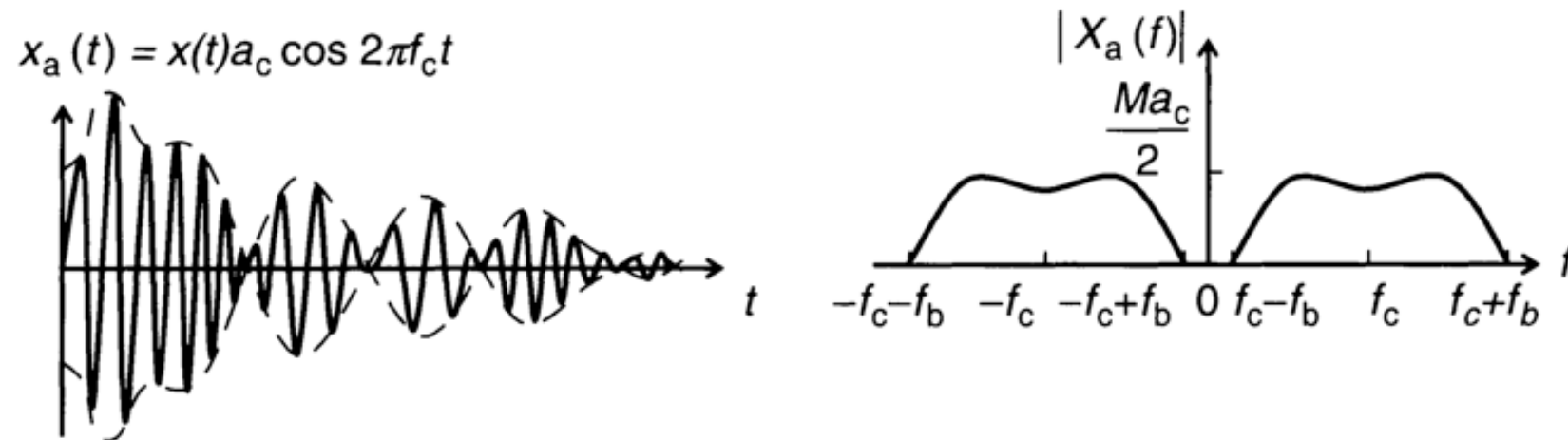


How to do this?

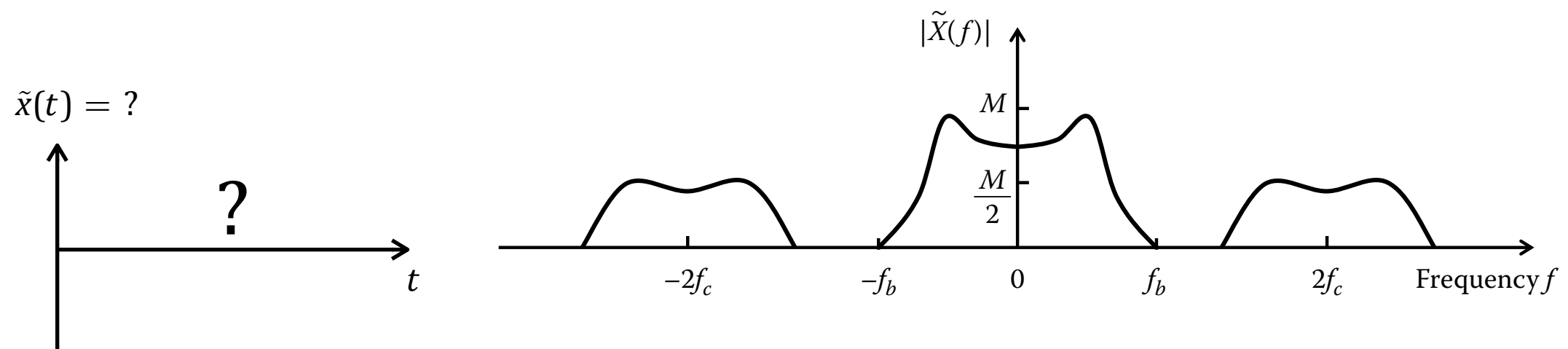and multiply it by $2/a_c$, and then sum the **left-shifted-by- f_c** and **right-shifted by f_c** versions of the multiplied signal the resulting signal will be





Amplitude Modulation

Demodulation

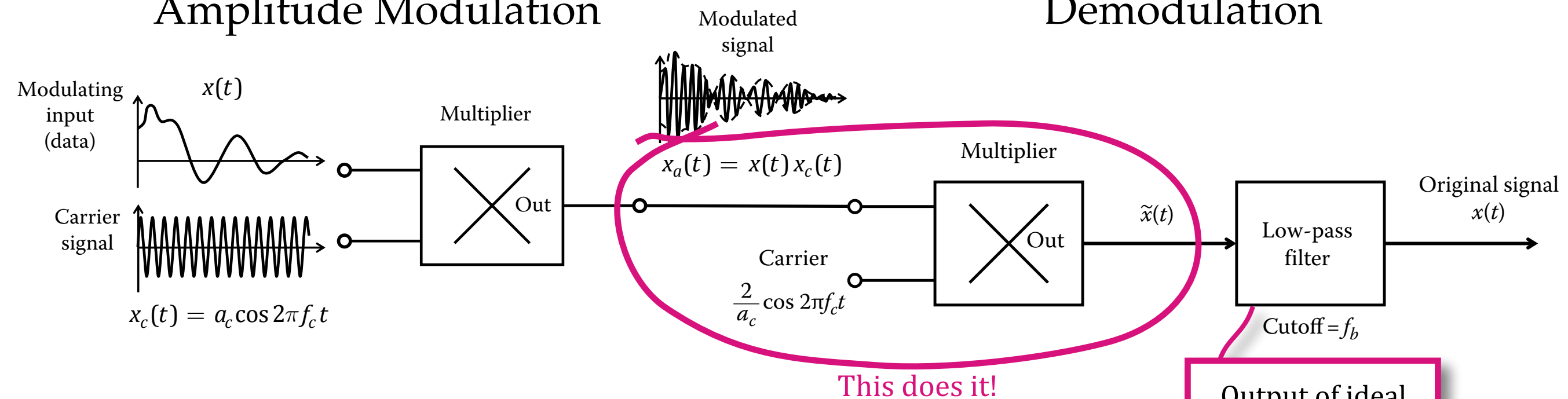

Recall that:

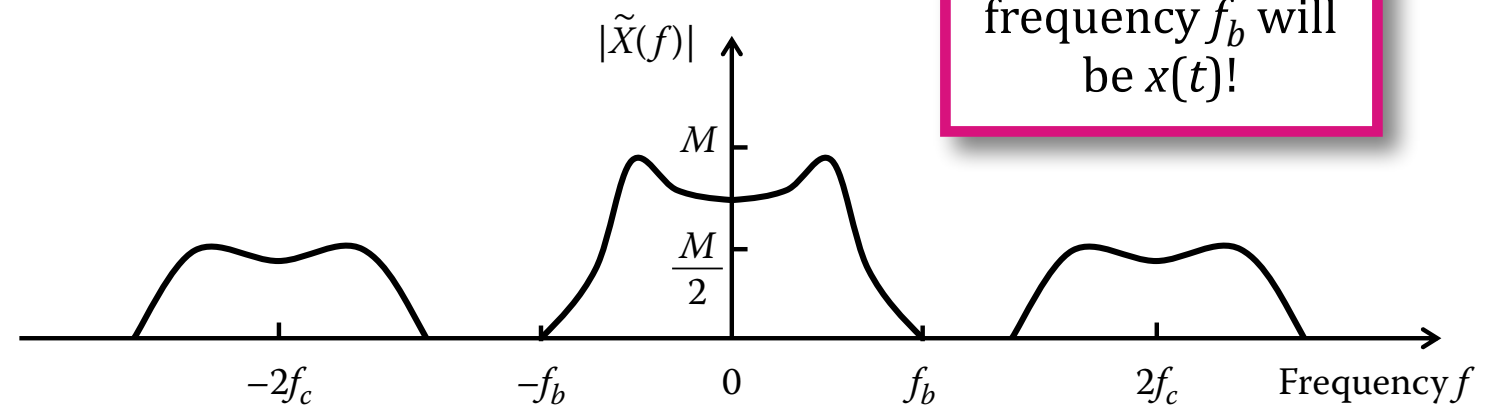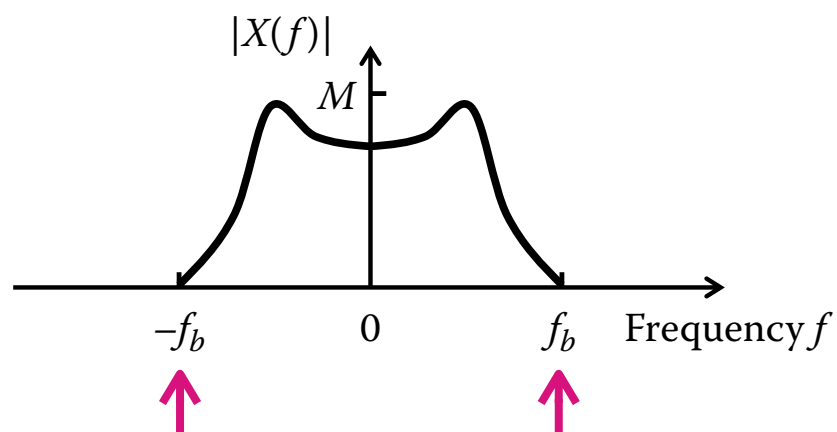


Output of ideal low-pass filter with cutoff frequency f_b will be $x(t)$!

AM Radio

Amplitude Modulation

Demodulation

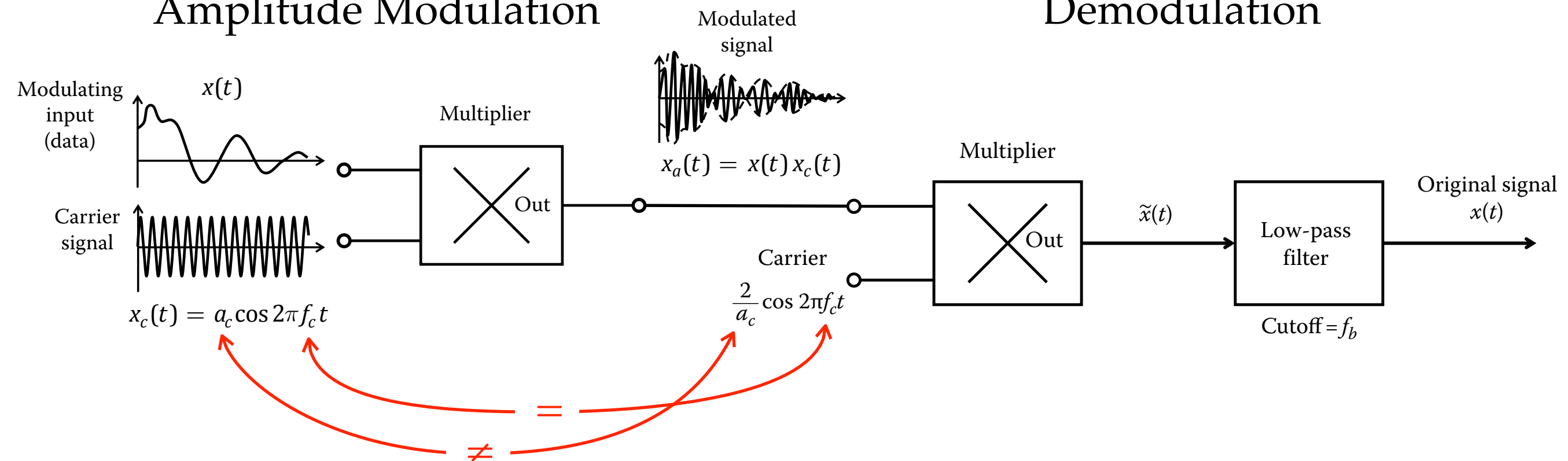

What conditions guarantee that the above demodulation scheme will recover $x(t)$ exactly?

f_b is the highest frequency in $x(t)$.

$$f_c > f_b$$

The low-pass filter is an ideal low pass filter.