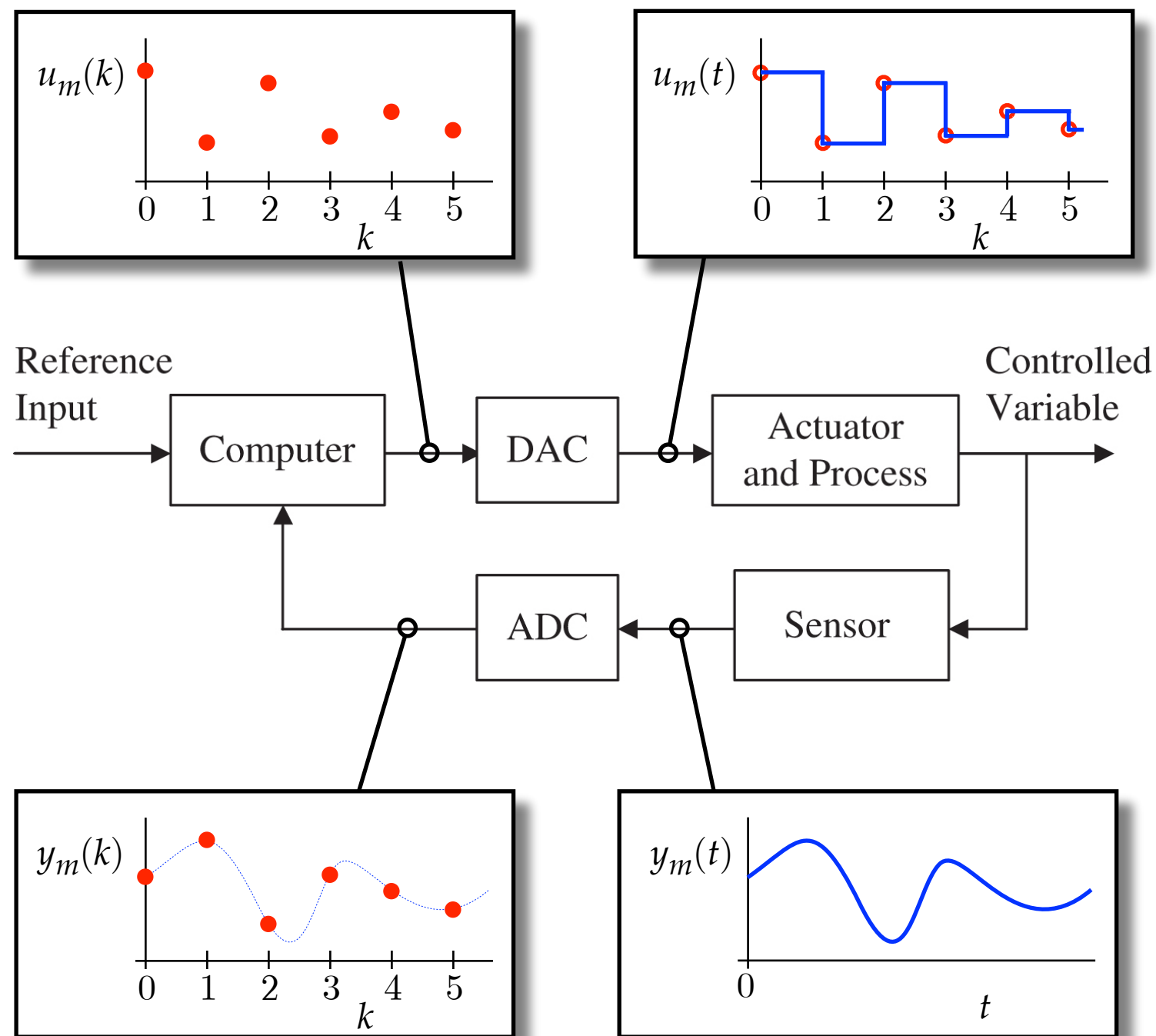



# Digital to analog converters (DAC), analog to digital converters (ADC)




$$y_m(k) \triangleq y_m(k \Delta T), \quad k = 0, 1, 2, \dots$$

- Resolution: given in number of bits (e.g. 10 or 16 bits, corresponding to dividing the voltage range into  $2^{10}=1024$  or  $2^{16}=65536$  intervals)
- speed (bandwidth): minimum interval  $\Delta T$

# Digital to Analog Conversion

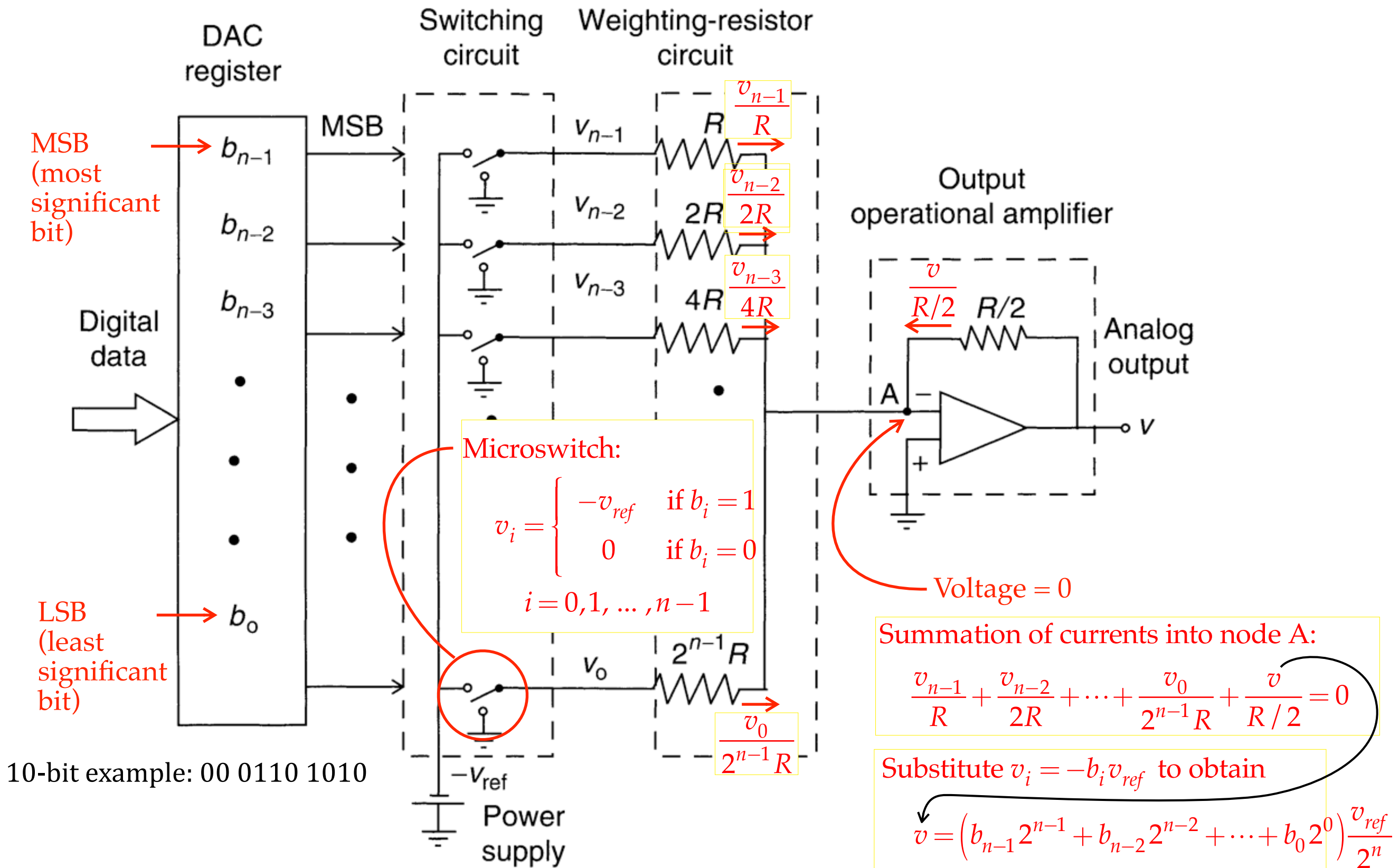

# Digital to Analog Conversion

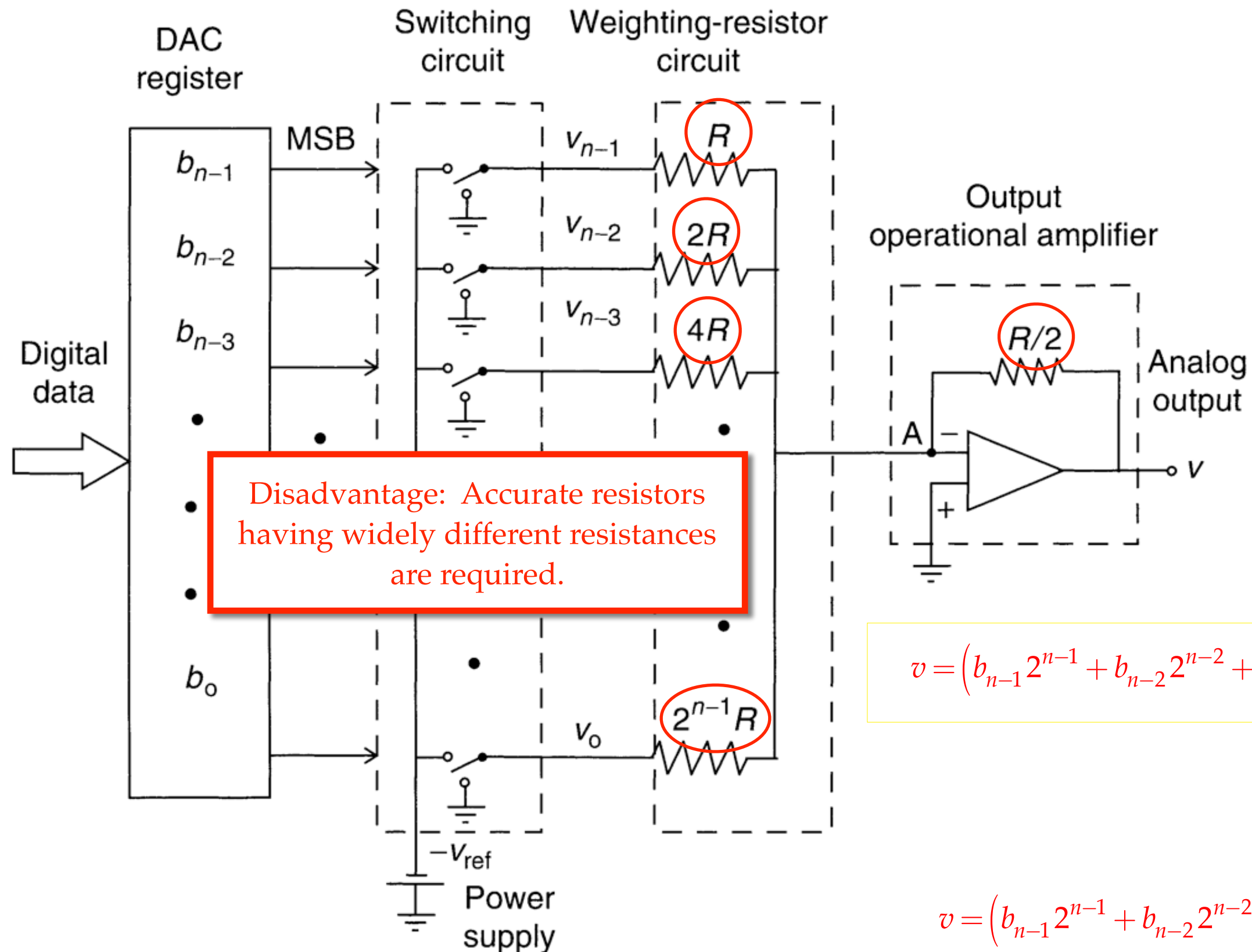

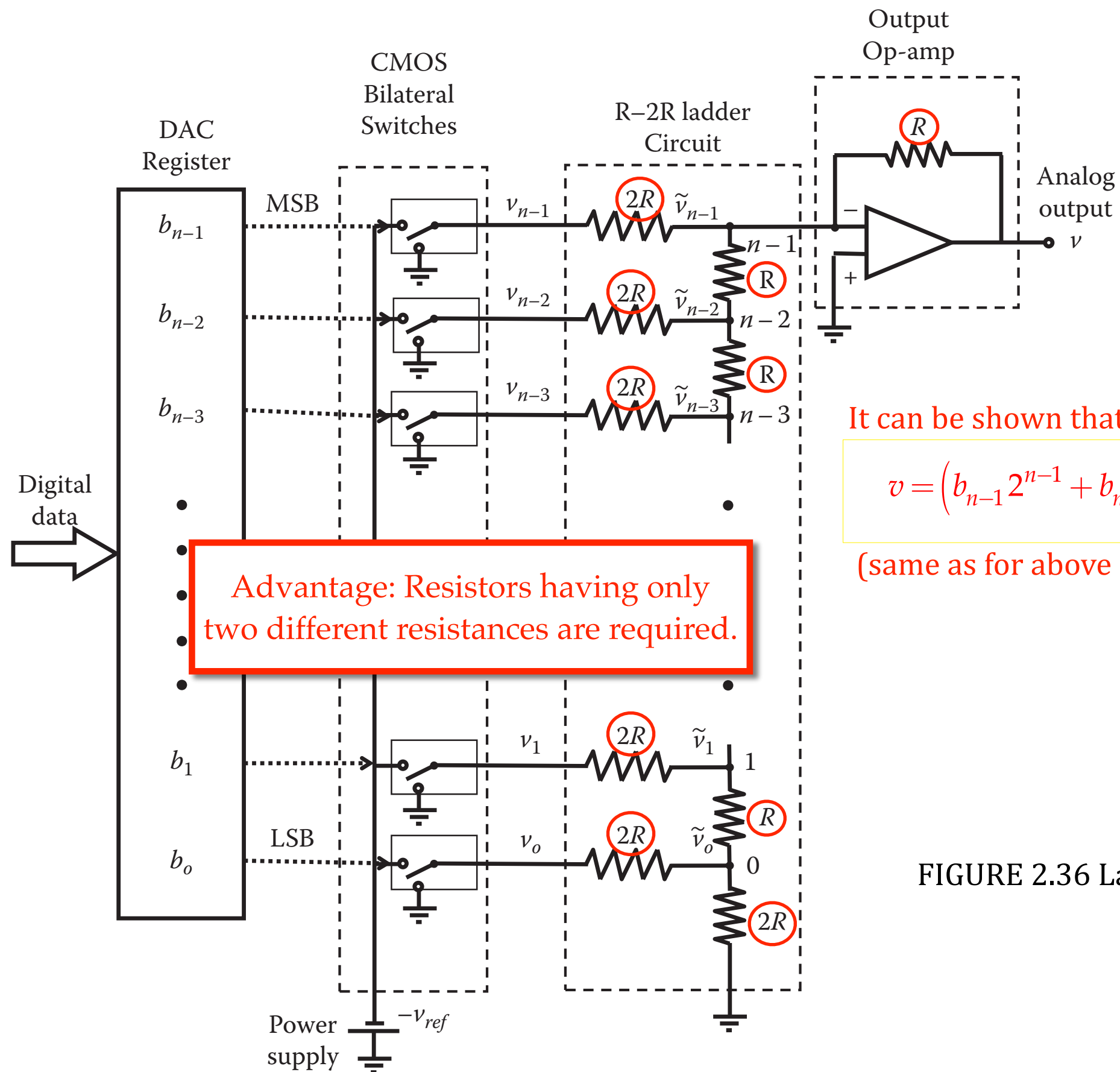


FIGURE 2.36 Ladder DAC circuit.

# analog to digital converters (ADC)

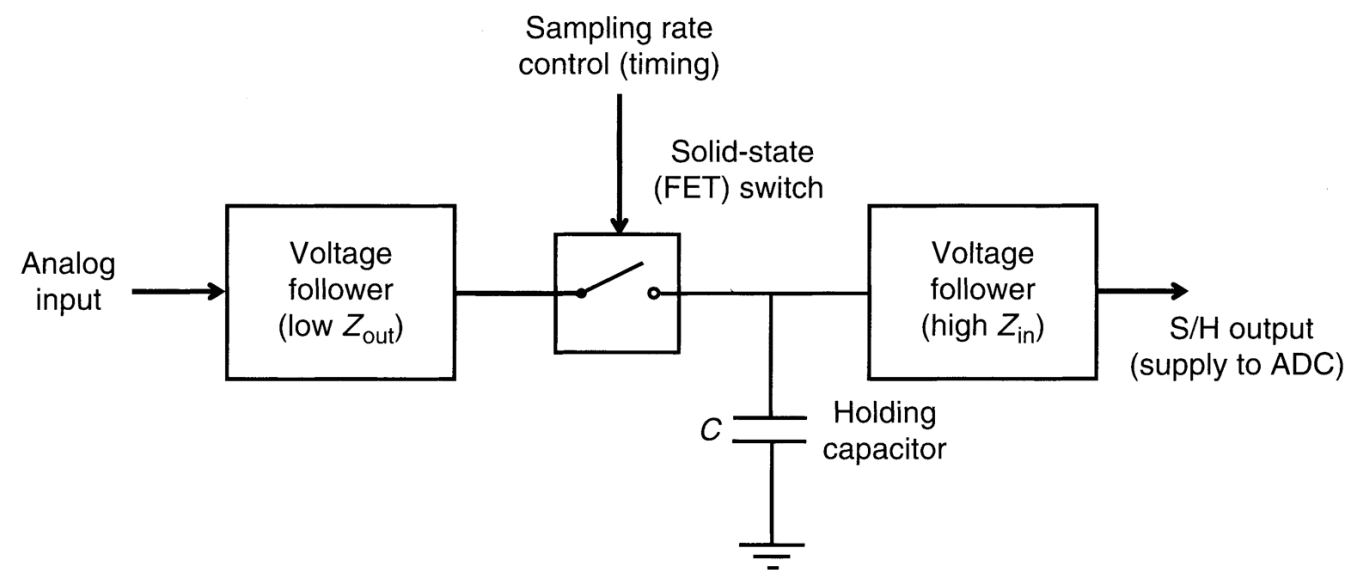


Figure 2.40 The circuit of a sample-and-hold chip.

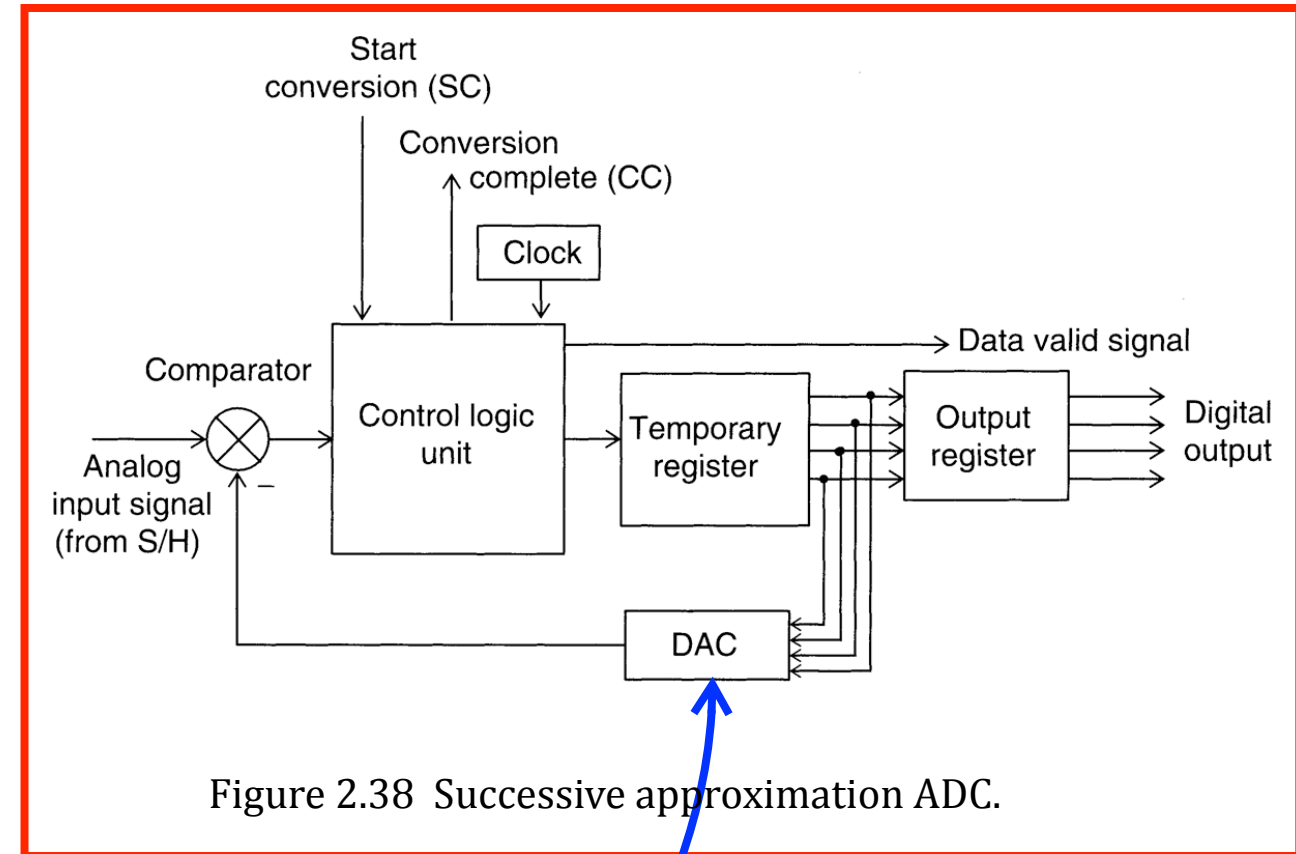


Figure 2.38 Successive approximation ADC.

For example, a weighted-resistance or ladder DAC

## Example: 4-bit ADC with Signal Range 0-5v

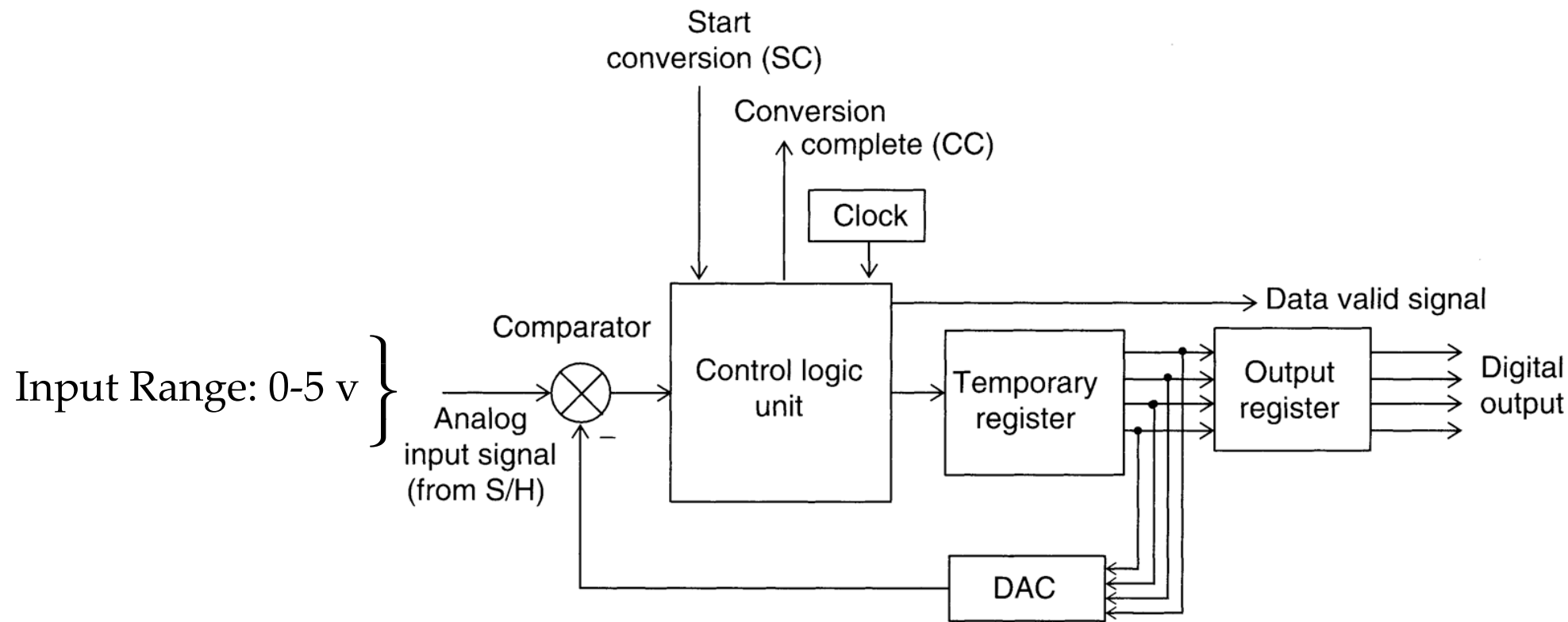


Figure 2.38 Successive approximation ADC.

| Base 2 | Base 10            | Volts |
|--------|--------------------|-------|
| 0000   | = 0                | 0     |
| 0001   | = 1 <sub>10</sub>  | 1/3   |
| 0010   | = 2 <sub>10</sub>  | 2/3   |
| 0011   | = 3 <sub>10</sub>  | 1     |
| 0100   | = 4 <sub>10</sub>  | 1 1/3 |
| 0101   | = 5 <sub>10</sub>  | 1 2/3 |
| 0110   | = 6 <sub>10</sub>  | 2     |
| 0111   | = 7 <sub>10</sub>  | 2 1/3 |
| 1000   | = 8 <sub>10</sub>  | 2 2/3 |
| 1001   | = 9 <sub>10</sub>  | 3     |
| 1010   | = 10 <sub>10</sub> | 3 1/3 |
| 1011   | = 11 <sub>10</sub> | 3 2/3 |
| 1100   | = 12 <sub>10</sub> | 4     |
| 1101   | = 13 <sub>10</sub> | 4 1/3 |
| 1110   | = 14 <sub>10</sub> | 4 2/3 |
| 1111   | = 15 <sub>10</sub> | 5     |

Suppose: Analog Input = 3 1/6 v

Targeted functionality:

$0\text{ V} \leq \text{Analog Input} < 1/3\text{ V} \Rightarrow \text{Digital Output} = 0000$

$1/3\text{ V} \leq \text{Analog Input} < 2/3\text{ V} \Rightarrow \text{Digital Output} = 0001$

$2/3\text{ V} \leq \text{Analog Input} < 1\text{ V} \Rightarrow \text{Digital Output} = 0010$

⋮

⋮

## Example: 4-bit ADC with Signal Range 0-5v

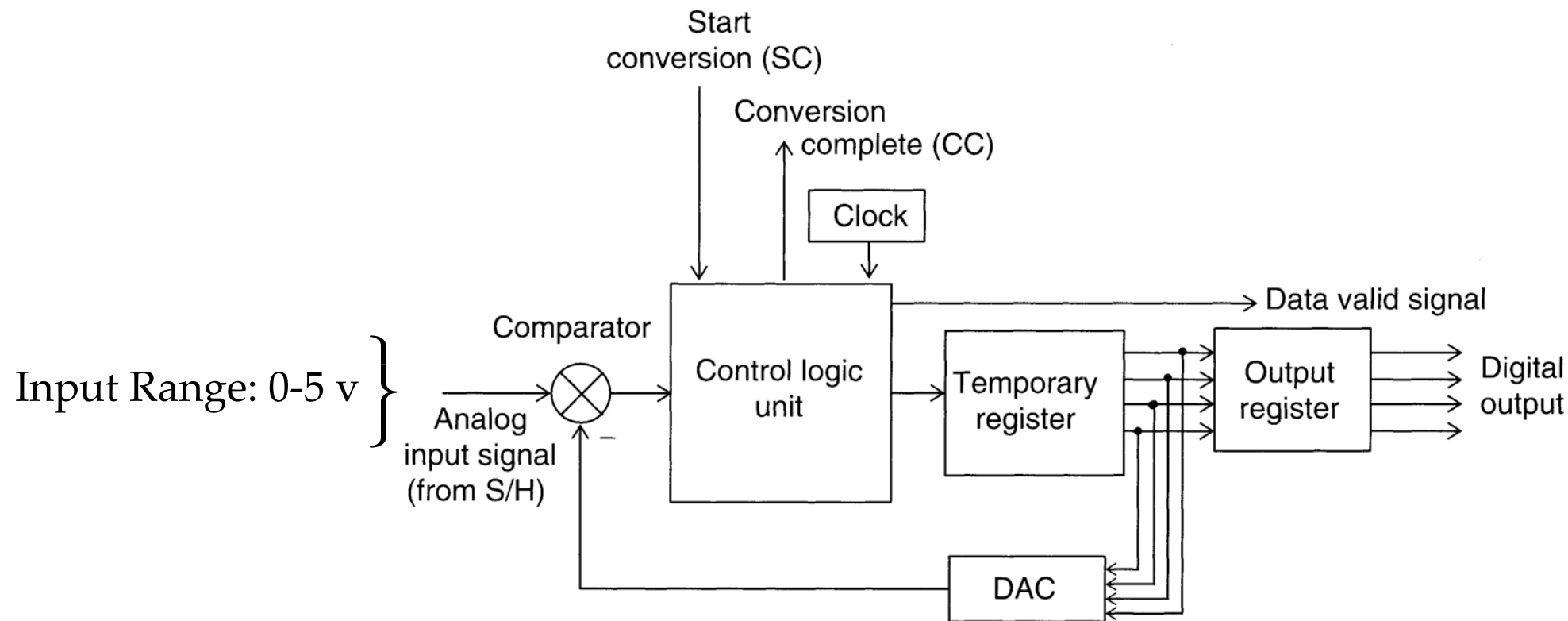


Figure 2.38 Successive approximation ADC.

| Base 2 | Base 10            | Volts |
|--------|--------------------|-------|
| 0000   | = 0                | 0     |
| 0001   | = 1 <sub>10</sub>  | 1/3   |
| 0010   | = 2 <sub>10</sub>  | 2/3   |
| 0011   | = 3 <sub>10</sub>  | 1     |
| 0100   | = 4 <sub>10</sub>  | 1 1/3 |
| 0101   | = 5 <sub>10</sub>  | 1 2/3 |
| 0110   | = 6 <sub>10</sub>  | 2     |
| 0111   | = 7 <sub>10</sub>  | 2 1/3 |
| 1000   | = 8 <sub>10</sub>  | 2 2/3 |
| 1001   | = 9 <sub>10</sub>  | 3     |
| 1010   | = 10 <sub>10</sub> | 3 1/3 |
| 1011   | = 11 <sub>10</sub> | 3 2/3 |
| 1100   | = 12 <sub>10</sub> | 4     |
| 1101   | = 13 <sub>10</sub> | 4 1/3 |
| 1110   | = 14 <sub>10</sub> | 4 2/3 |
| 1111   | = 15 <sub>10</sub> | 5     |

Analog Input = 3 1/6 v

Bit 3: Temporary Register = 1000  
(first guess is always 1000)

⇒ DAC Output = 2 2/3 v

⇒ Analog Input – DAC Output = Positive

⇒ Bit 3 = 1

Bit 2: Temporary Register = 1100

⇒ DAC Output = 4 v

⇒ Analog Input – DAC Output = Negative

⇒ Bit 2 = 0



## Example: 4-bit ADC with Signal Range 0-5v

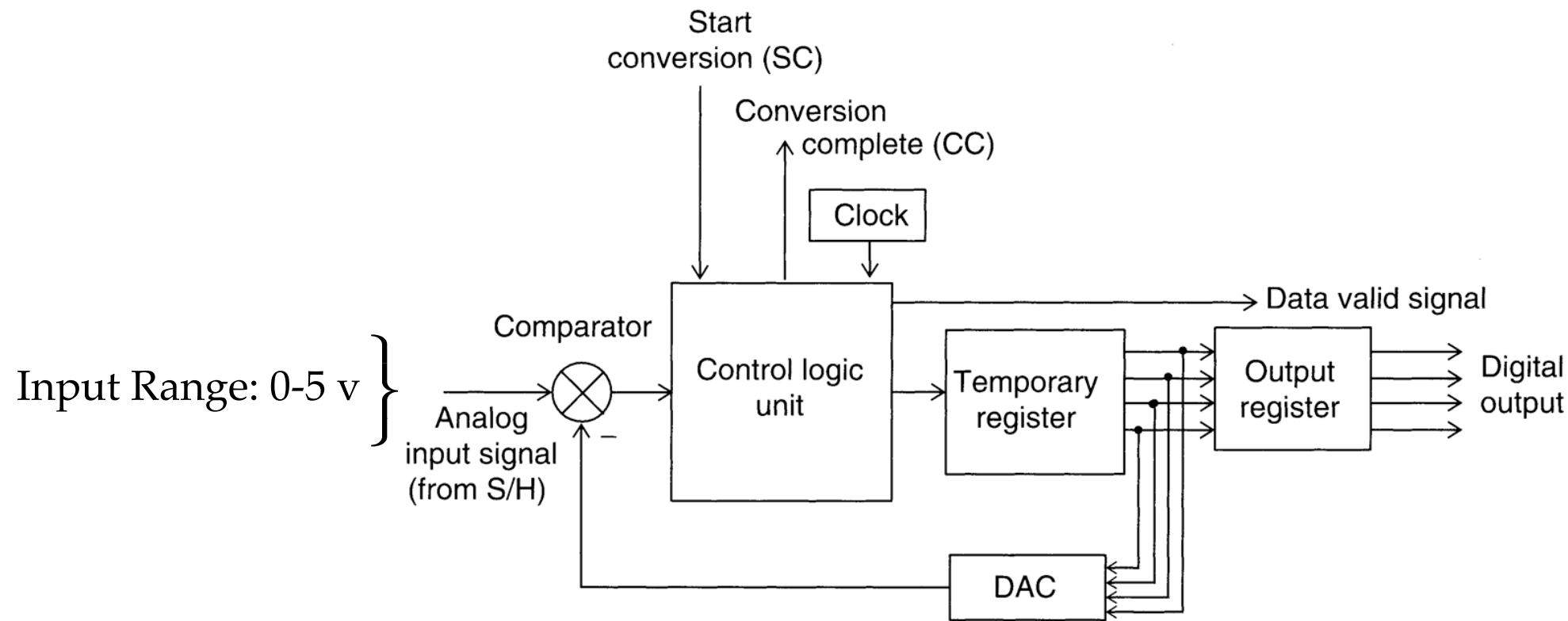


Figure 2.38 Successive approximation ADC.

| Base 2 | Base 10            | Volts |
|--------|--------------------|-------|
| 0000   | = 0                | 0     |
| 0001   | = 1 <sub>10</sub>  | 1/3   |
| 0010   | = 2 <sub>10</sub>  | 2/3   |
| 0011   | = 3 <sub>10</sub>  | 1     |
| 0100   | = 4 <sub>10</sub>  | 1 1/3 |
| 0101   | = 5 <sub>10</sub>  | 1 2/3 |
| 0110   | = 6 <sub>10</sub>  | 2     |
| 0111   | = 7 <sub>10</sub>  | 2 1/3 |
| 1000   | = 8 <sub>10</sub>  | 2 2/3 |
| 1001   | = 9 <sub>10</sub>  | 3     |
| 1010   | = 10 <sub>10</sub> | 3 1/3 |
| 1011   | = 11 <sub>10</sub> | 3 2/3 |
| 1100   | = 12 <sub>10</sub> | 4     |
| 1101   | = 13 <sub>10</sub> | 4 1/3 |
| 1110   | = 14 <sub>10</sub> | 4 2/3 |
| 1111   | = 15 <sub>10</sub> | 5     |

Analog Input = 3 1/6 v

Bit 1: Temporary Register = 1010

⇒ DAC Output = 3 1/3 v

⇒ Analog Input – DAC Output = Negative

⇒ Bit 1 = 0

Bit 0: Temporary Register = 1001

⇒ DAC Output = 3 v

⇒ Analog Input – DAC Output = Positive

⇒ Bit 0 = 1



## Example: 4-bit ADC with Signal Range 0-5v

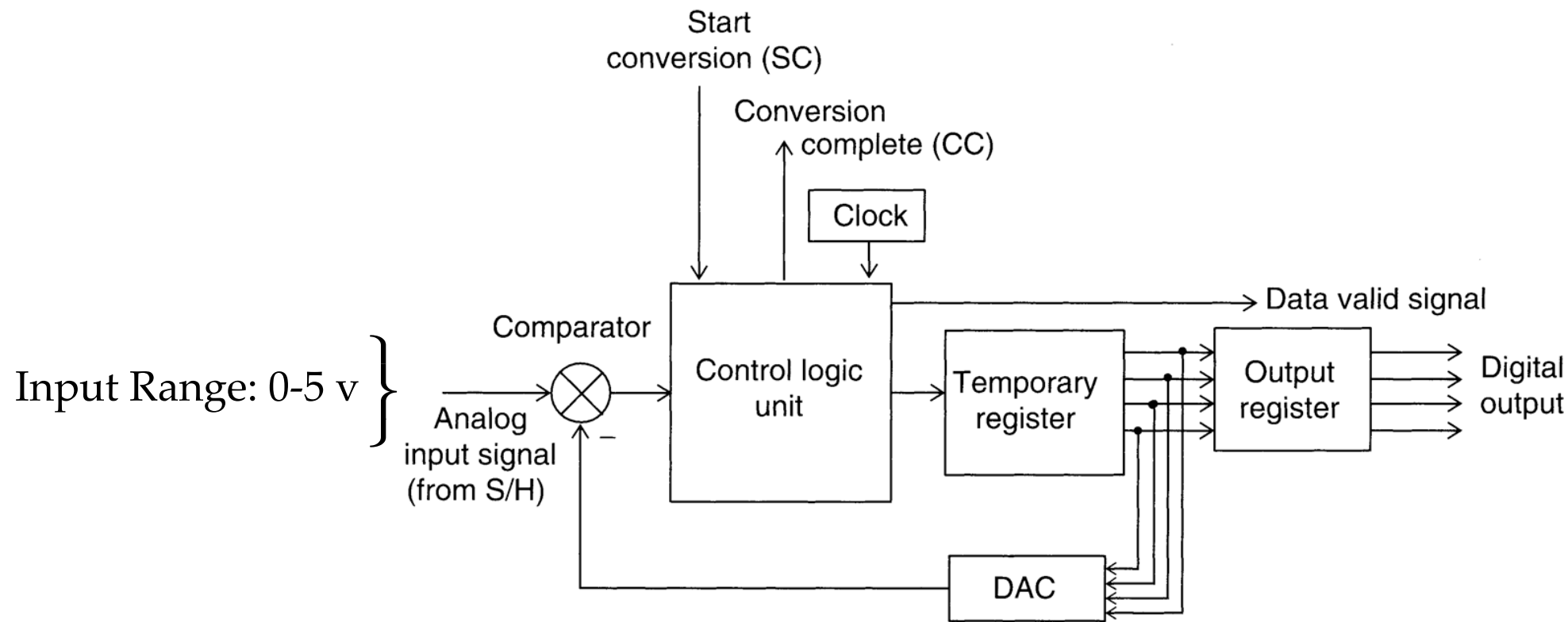


Figure 2.38 Successive approximation ADC.

| Base 2 | Base 10            | Volts |
|--------|--------------------|-------|
| 0000   | = 0                | 0     |
| 0001   | = 1 <sub>10</sub>  | 1/3   |
| 0010   | = 2 <sub>10</sub>  | 2/3   |
| 0011   | = 3 <sub>10</sub>  | 1     |
| 0100   | = 4 <sub>10</sub>  | 1 1/3 |
| 0101   | = 5 <sub>10</sub>  | 1 2/3 |
| 0110   | = 6 <sub>10</sub>  | 2     |
| 0111   | = 7 <sub>10</sub>  | 2 1/3 |
| 1000   | = 8 <sub>10</sub>  | 2 2/3 |
| 1001   | = 9 <sub>10</sub>  | 3     |
| 1010   | = 10 <sub>10</sub> | 3 1/3 |
| 1011   | = 11 <sub>10</sub> | 3 2/3 |
| 1100   | = 12 <sub>10</sub> | 4     |
| 1101   | = 13 <sub>10</sub> | 4 1/3 |
| 1110   | = 14 <sub>10</sub> | 4 2/3 |
| 1111   | = 15 <sub>10</sub> | 5     |


Analog Input = 3 1/6 v

Finish: Temporary Register = 1001


⇒ Output Register = 1001

Conversion Complete!


# Constant-Voltage Resistance Bridge

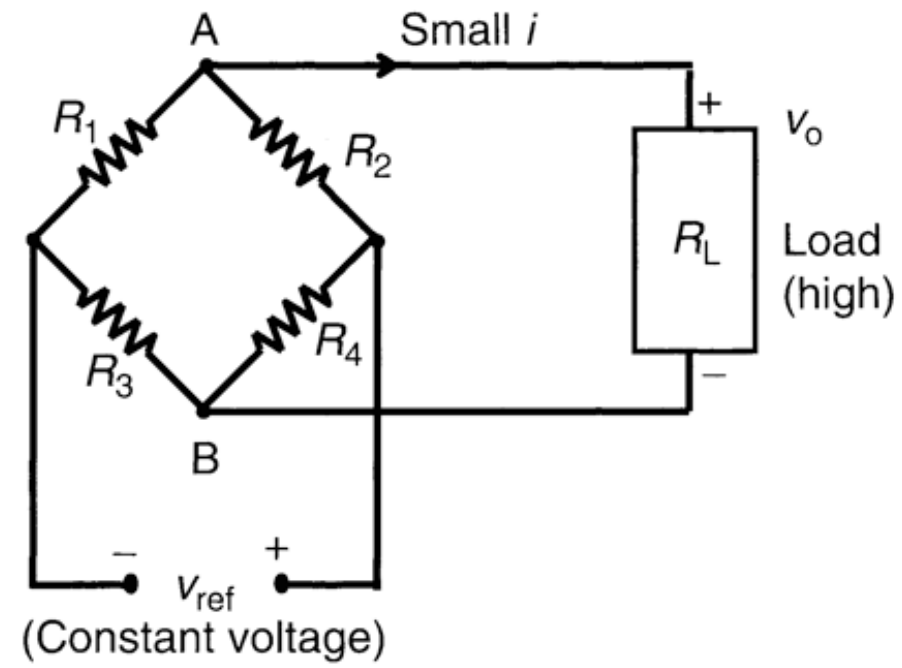
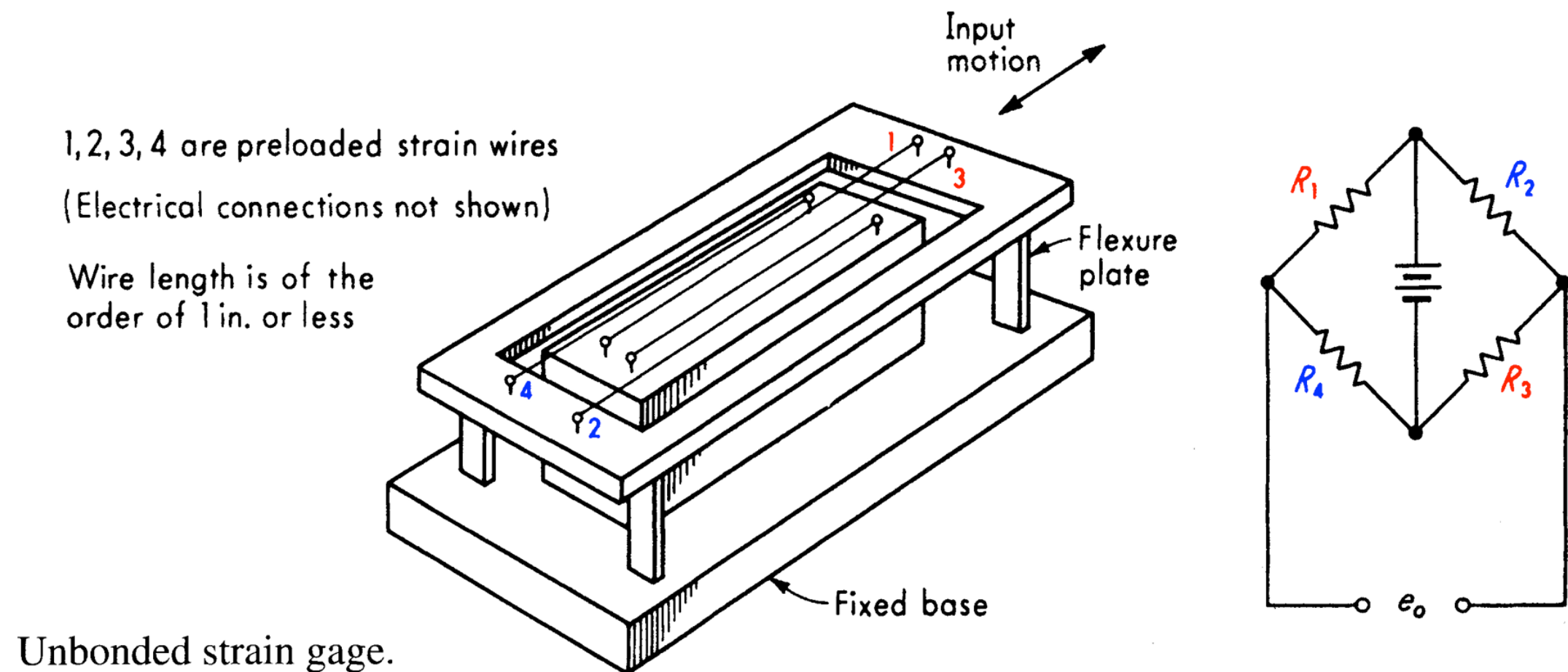
## Example Application: An Unbonded Strain Gage



# Constant-Voltage Resistance Bridge

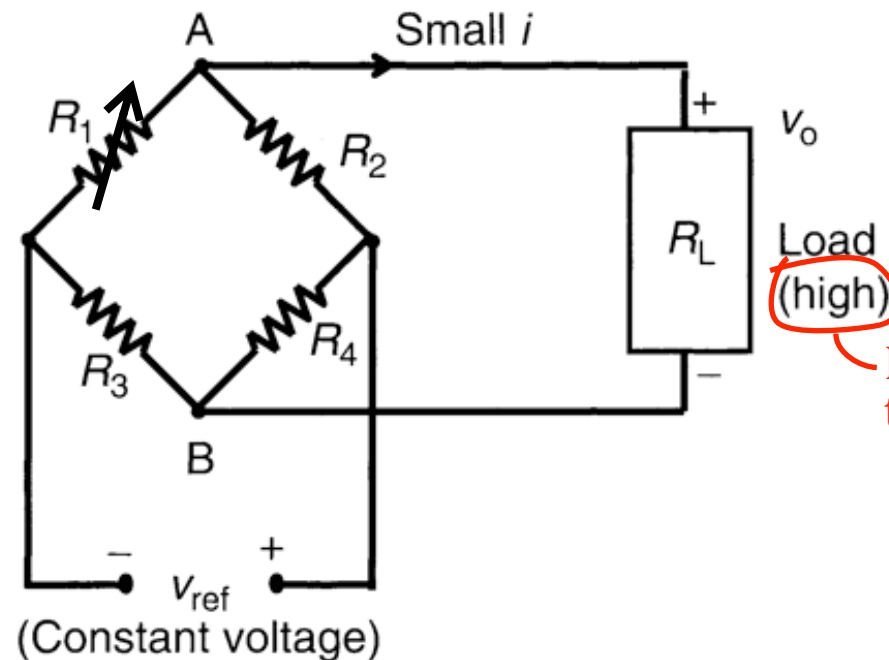

If  $R_L \gg R_i$ , then negligible current flows through the load.

$$v_o = v_A - v_B = \left[ \frac{R_1}{R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right] v_{ref} = \left[ \frac{R_1 R_4 - R_2 R_3}{(R_1 + R_2)(R_3 + R_4)} \right] v_{ref}$$


$$= 0 \text{ when } \frac{R_1}{R_2} = \frac{R_3}{R_4} \quad \leftarrow \text{Balanced Bridge Condition}$$

With  $R_2 = R_3 = R_4 = R$  and  $R_1 = R + \delta R$ :

$$\delta v_o = v_o \Big|_{\substack{R_1=R+\delta R \\ R_2=R_3=R_4=R}} - v_o \Big|_{R_1=R_2=R_3=R_4=R} = \left[ \frac{(R + \delta R)(R) - (R)(R)}{(R + \delta R + R)(R + R)} \right] v_{ref} = \left[ \frac{R(\delta R)}{4R^2 + 2R(\delta R)} \right] v_{ref}$$

$$= \left( \frac{\delta R/R}{4 + 2\delta R/R} \right) v_{ref} \quad \leftarrow \delta v_o \text{ due to } \delta R \text{ is a nonlinear function of } \delta R$$

# Constant-Voltage Resistance Bridge

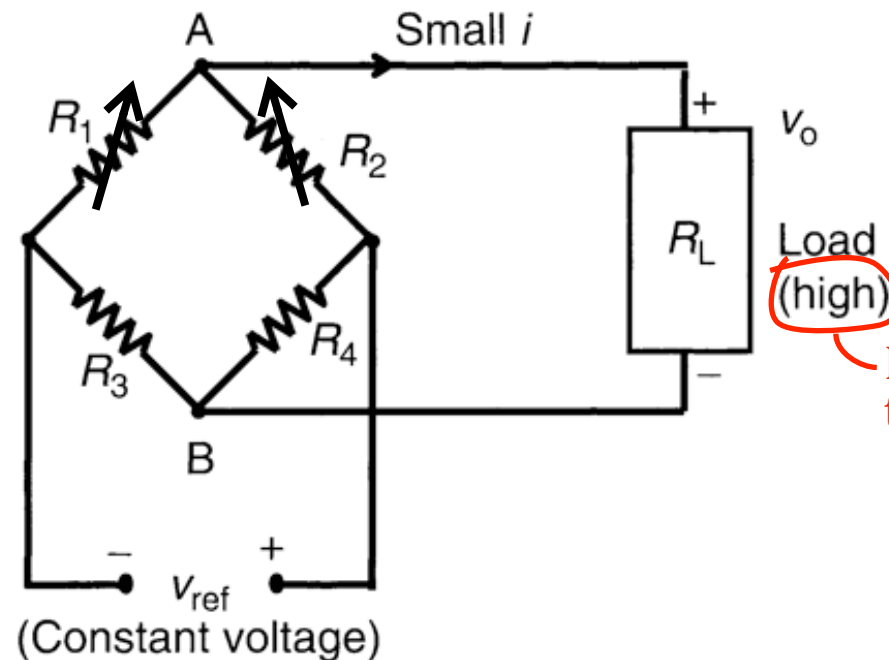

If  $R_L \gg R_i$ , then negligible current flows through the load.

$$v_o = v_A - v_B = \left[ \frac{R_1}{R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right] v_{ref} = \left[ \frac{R_1 R_4 - R_2 R_3}{(R_1 + R_2)(R_3 + R_4)} \right] v_{ref}$$

$$= 0 \text{ when } \frac{R_1}{R_2} = \frac{R_3}{R_4} \quad \leftarrow \text{Balanced Bridge Condition}$$


With  $R_3 = R_4 = R$  and  $R_1 = R + \delta R$  and  $R_2 = R - \delta R$ :

$$\delta v_o = v_o \bigg|_{\substack{R_1=R+\delta R \\ R_2=R-\delta R \\ R_3=R_4=R}} - v_o \bigg|_{R_1=R_2=R_3=R_4=R} = \left[ \frac{(R + \delta R)(R) - (R - \delta R)(R)}{(R + \delta R + R - \delta R)(R + R)} \right] v_{ref} = \left[ \frac{2R(\delta R)}{4R^2} \right] v_{ref}$$

$$= \left( \frac{v_{ref}}{2R} \right) \delta R \quad \leftarrow \delta v_o \text{ proportional to } \delta R!!$$

Example 2.11 in de Silva treats this same example and gets a wrong result!

# Constant-Current Resistance Bridge

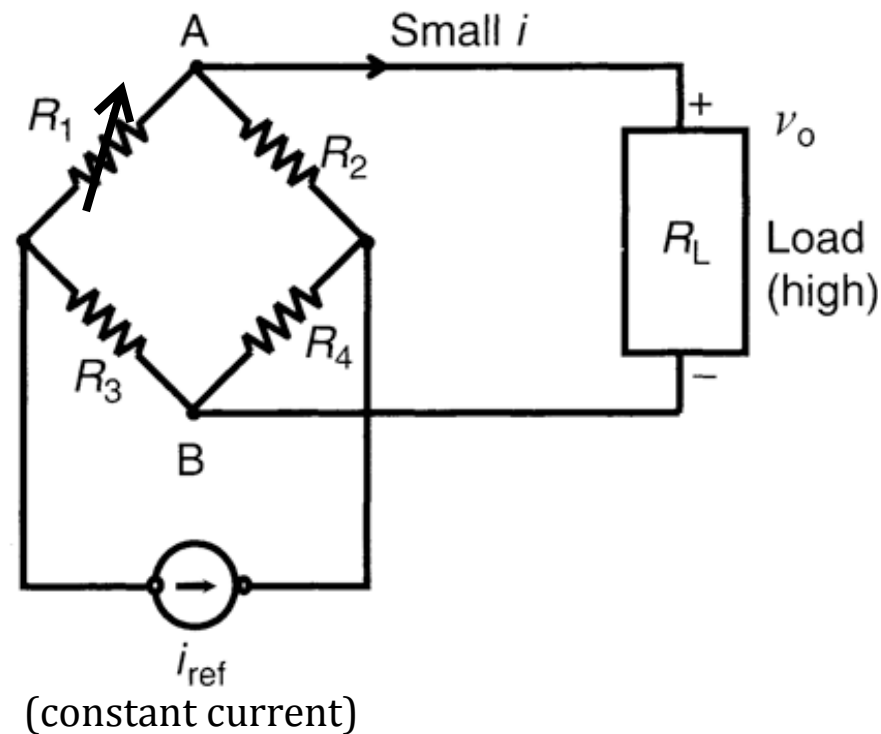

With  $R_2 = R_3 = R_4 = R$  and  $R_1 = R + \delta R$ :


$$\delta v_o = v_o \bigg|_{\substack{R_1=R+\delta R \\ R_2=R_3=R_4=R}} - v_o \bigg|_{R_1=R_2=R_3=R_4=R}$$

For constant-voltage bridge this was  $\frac{\delta R/R}{4 + 2\delta R/R}$

$$= \left( \frac{\delta R/R}{4 + \delta R/R} \right) R i_{\text{ref}} \quad \leftarrow \delta v_o \text{ due to } \delta R \text{ is a nonlinear function of } \delta R$$

(Derivation in Sec. 2.8.2)

# Constant-Current Resistance Bridge

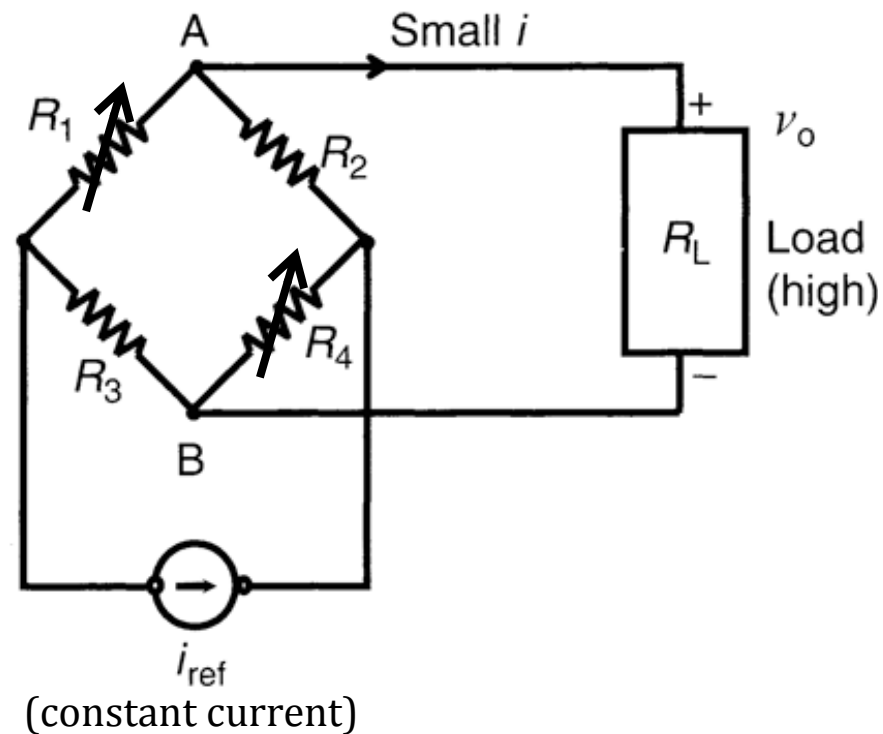


With  $R_2 = R_3 = R$  and  $R_1 = R + \delta R$  and  $R_4 = R + \delta R$ :

$$\delta v_o = v_o \left| \begin{array}{l} R_1 = R + \delta R \\ R_4 = R + \delta R \\ R_2 = R_3 = R \end{array} \right| - v_o \left| \begin{array}{l} R_1 = R_2 = R_3 = R_4 = R \end{array} \right| = \left( \frac{\delta R / R}{2} \right) R i_{\text{ref}} \quad \leftarrow \delta v_o \text{ proportional to } \delta R!!$$


(Derivation in Example 2.12)


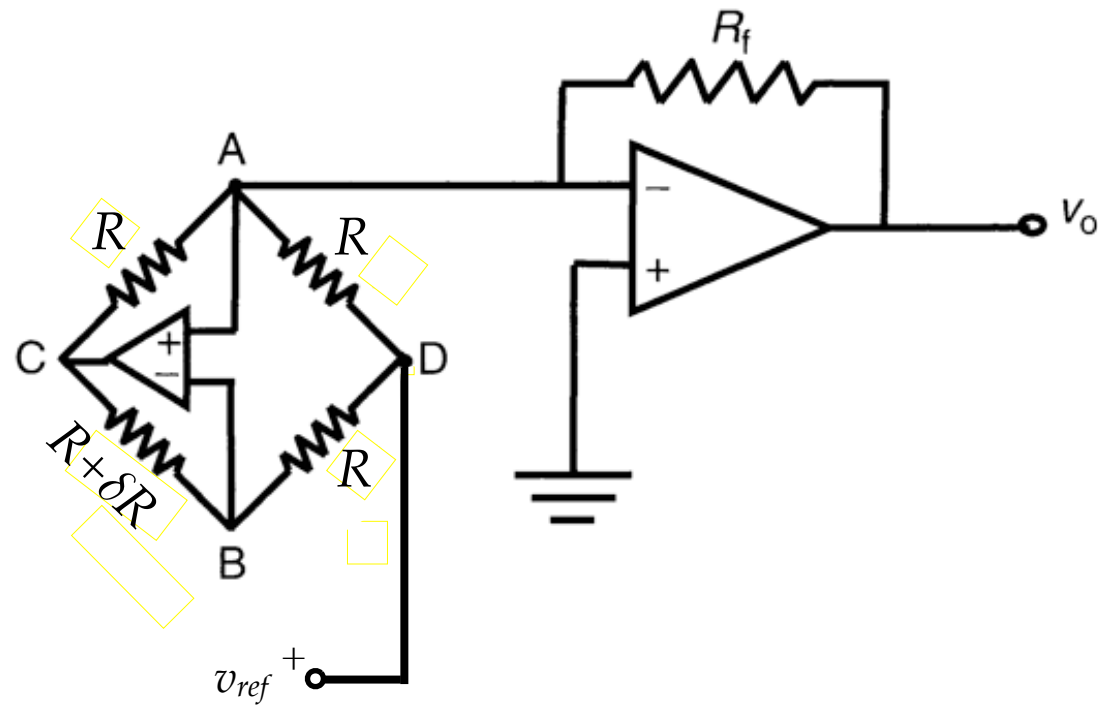
# Another Constant-Voltage Resistance Bridge




Or, equivalently:

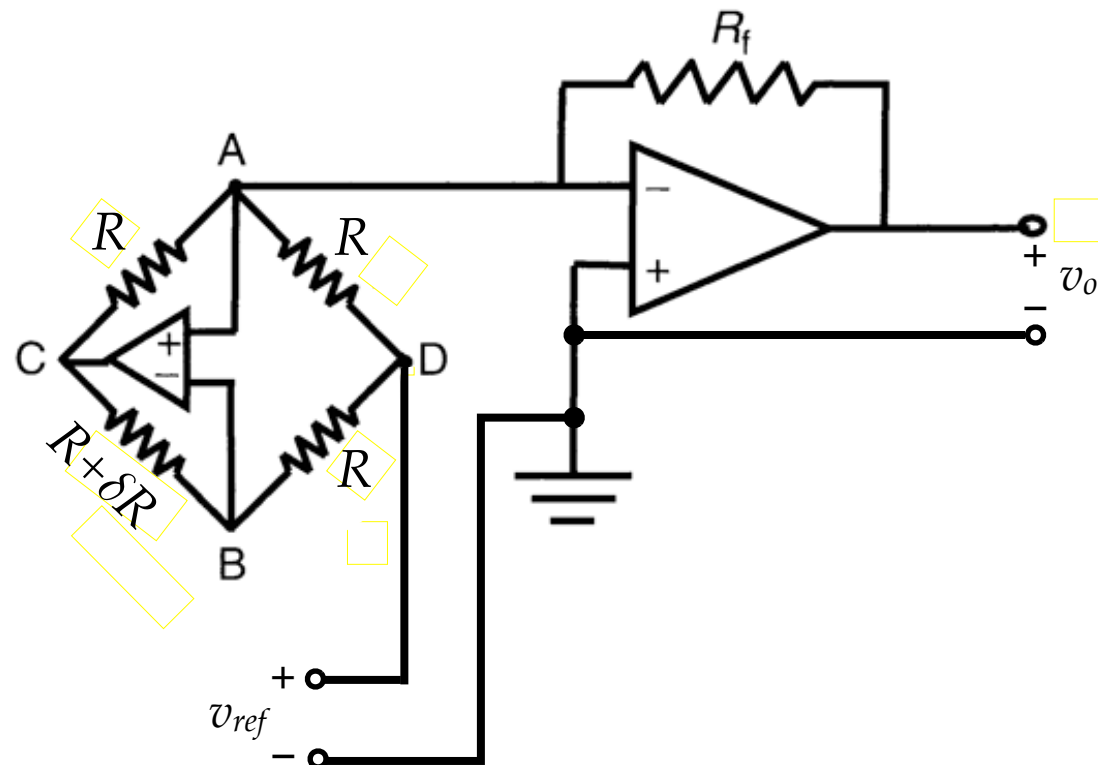



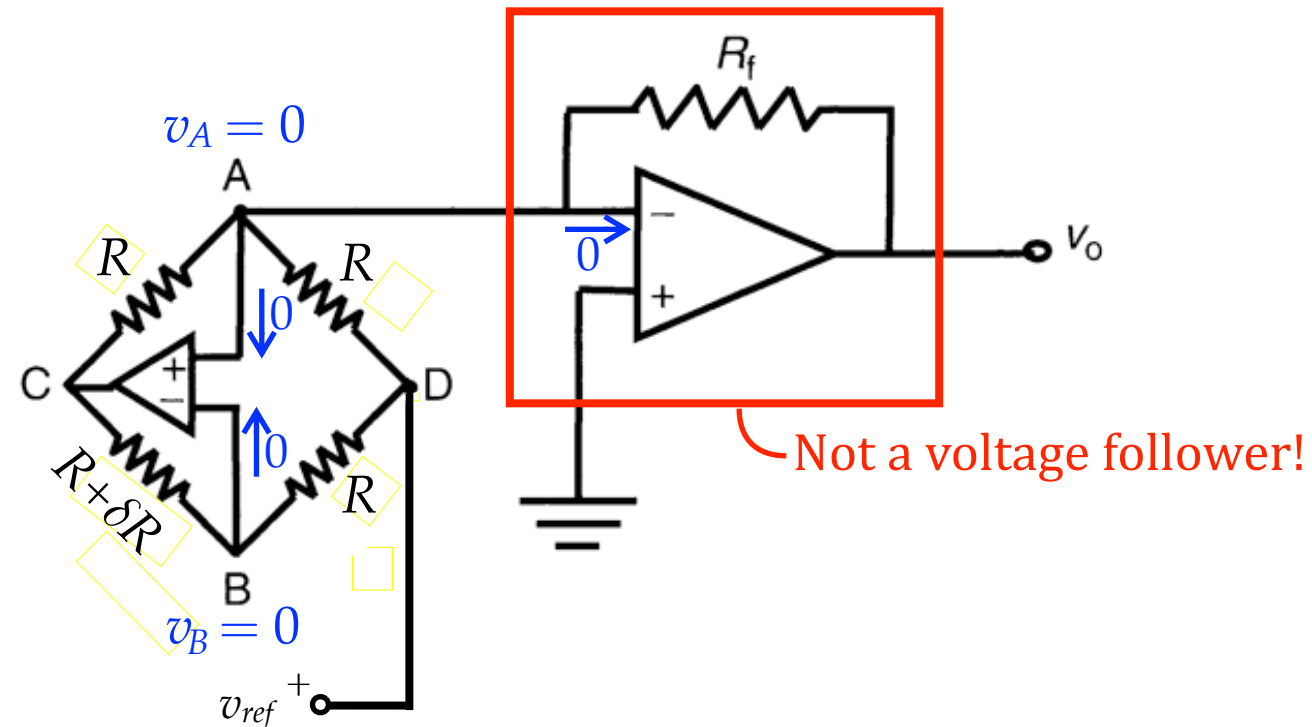
# Another Constant-Voltage Resistance Bridge



$$\begin{aligned}
 \text{Node A: } & \frac{v_C}{R} + \frac{v_{ref}}{R} + \frac{v_0}{R_f} = 0 \\
 \text{Node B: } & \frac{v_{ref}}{R} + \frac{v_C}{R + \delta R} = 0 \Rightarrow v_C = -v_{ref} \frac{R + \delta R}{R}
 \end{aligned}
 \left. \vphantom{\begin{aligned} \text{Node A:} \\ \text{Node B:} \end{aligned}} \right\} \Rightarrow -v_{ref} \frac{R + \delta R}{R^2} + \frac{v_{ref}}{R} + \frac{v_0}{R_f} = 0$$

$$\begin{aligned}
 \Rightarrow \frac{v_0}{R_f} &= v_{ref} \frac{R + \delta R}{R^2} - \frac{v_{ref}}{R} \Rightarrow v_0 = v_{ref} R_f \left( \frac{R + \delta R}{R^2} - \frac{1}{R} \right) = v_{ref} R_f \left( \frac{R + \delta R}{R^2} - \frac{R}{R^2} \right) \\
 &= v_{ref} R_f \left( \frac{\delta R}{R^2} \right) \\
 &= v_{ref} \frac{R_f}{R^2} \delta R \leftarrow v_o \text{ proportional to } \delta R!!
 \end{aligned}$$

# Impedance Bridge

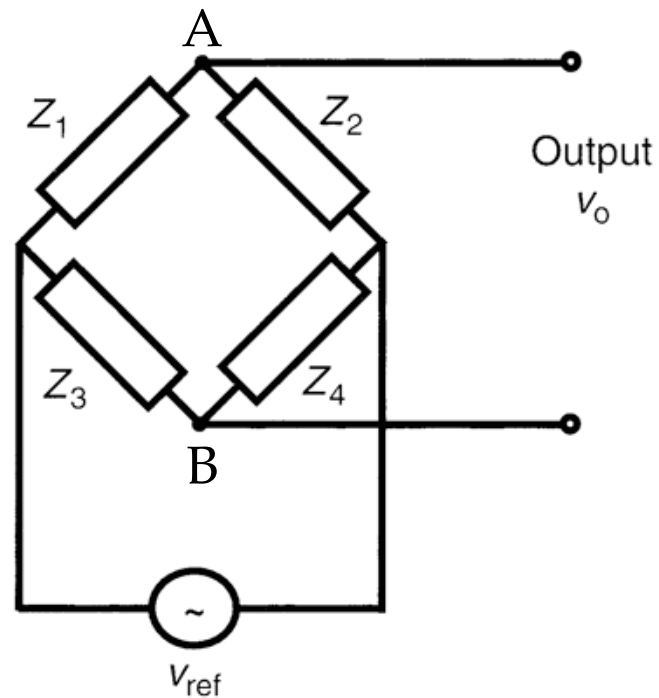


$$V_o(s) = V_A(s) - V_B(s) = \left[ \frac{Z_1}{Z_1 + Z_2} - \frac{Z_3}{Z_3 + Z_4} \right] V_{ref}(s) = \left[ \frac{Z_1 Z_4 - Z_2 Z_3}{(Z_1 + Z_2)(Z_3 + Z_4)} \right] V_{ref}(s)$$

$$= 0 \text{ when } \frac{Z_1}{Z_2} = \frac{Z_3}{Z_4} \quad \leftarrow \text{Balanced Bridge Condition}$$

An Owen Bridge is a practical example of an Impedance Bridge

# Owen Bridge

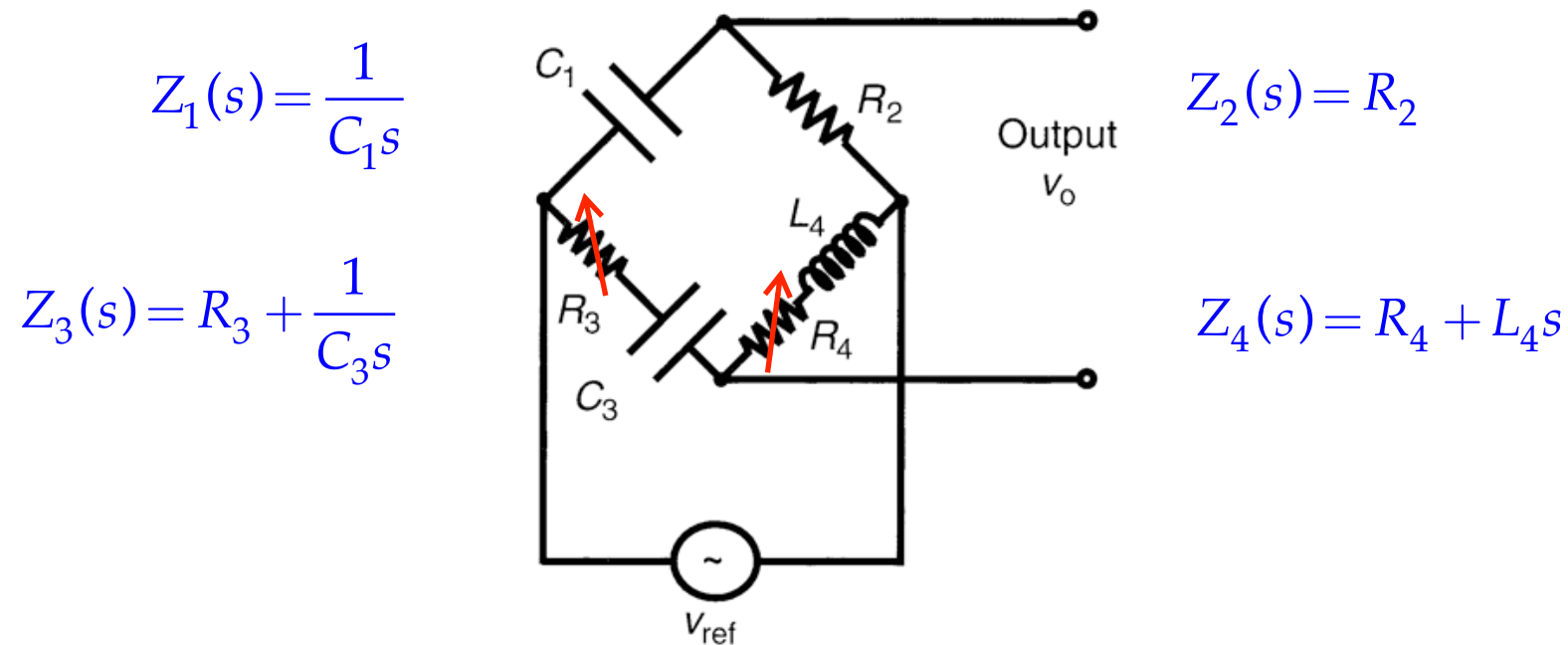

With  $v_{ref}(t) = \sin(\omega t)$ , balance the bridge (i.e., make  $v_o = 0$ ) by varying  $R_3$  and  $R_4$ , then:

$$\frac{Z_1(j\omega)}{Z_2(j\omega)} = \frac{Z_3(j\omega)}{Z_4(j\omega)} \Rightarrow Z_1(j\omega)Z_4(j\omega) = Z_2(j\omega)Z_3(j\omega)$$

$$\Rightarrow \frac{1}{C_1 j\omega} [R_4 + L_4 j\omega] = R_2 \left[ R_3 + \frac{1}{C_3 j\omega} \right]$$

$$\Rightarrow \frac{L_4}{C_1} = R_2 R_3 \quad \text{and} \quad \frac{R_4}{C_1} = \frac{R_2}{C_3}$$

$$\Rightarrow L_4 = C_1 R_2 R_3 \quad \text{and} \quad C_3 = \frac{R_2 C_1}{R_4}$$

$\Rightarrow L_4$  and  $C_3$  can be determined if  $C_1$ ,  $R_2$ ,  $R_3$  and  $R_4$  are known